

EE-612: Lecture 24: CMOS Circuits: Part 1


Mark Lundstrom

Electrical and Computer Engineering

Purdue University

West Lafayette, IN USA

Fall 2006

 

NCN

www.nanohub.org


Outline

- 1) Review
- 2) CMOS circuits
- 3) The CMOS inverter
- 4) Speed

MOSFETs

PMOS


NMOS

 

output conductance


$$r_o = \left(\partial I_D / \partial V_{DS} \right)^{-1}$$

$$I_D = I_{DSAT} (1 + \lambda V_{DS})$$

 

channel length modulation
'DIBL above threshold'

small signal gain

 


$$A_V = -g_m (R_D \parallel r_o)$$

$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DS}}$$


Outline

- 1) Review
- 2) CMOS circuits**
- 3) The CMOS inverter
- 4) Speed
- 5) Power
- 6) Circuit performance


ideal CMOS inverter

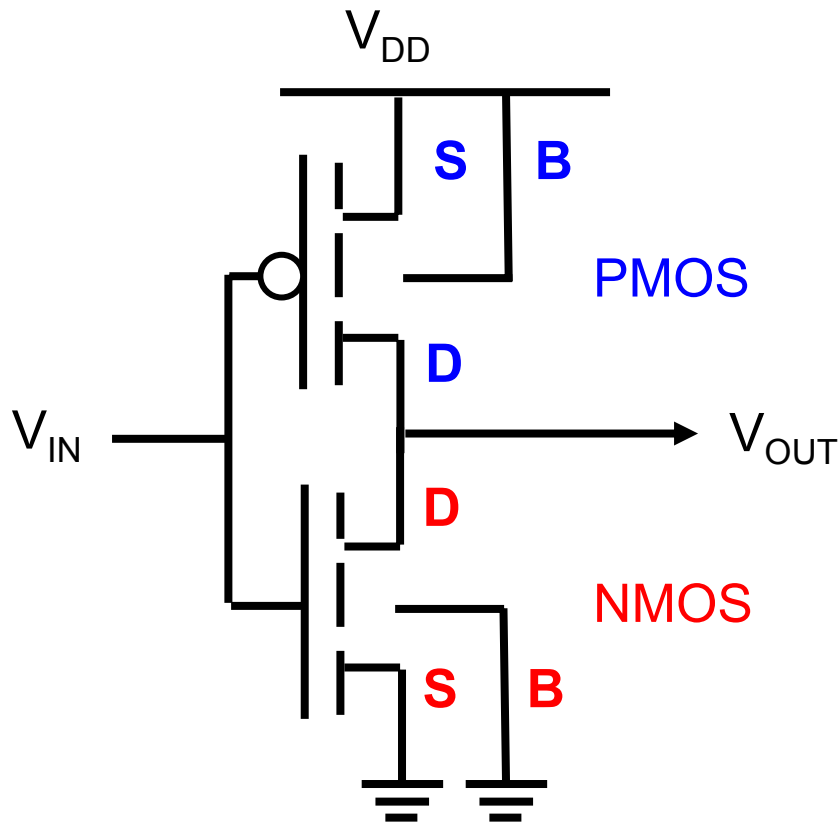

transfer characteristic


 


CMOS inverter (cross-section)

 


Courtesy of Dr. Lynn Fuller of Rochester Institute of Technology.
<http://www.rit.edu/~lffeee/AdvCmos2003.pdf>

CMOS inverter (top view)

  


technology-independent design rules

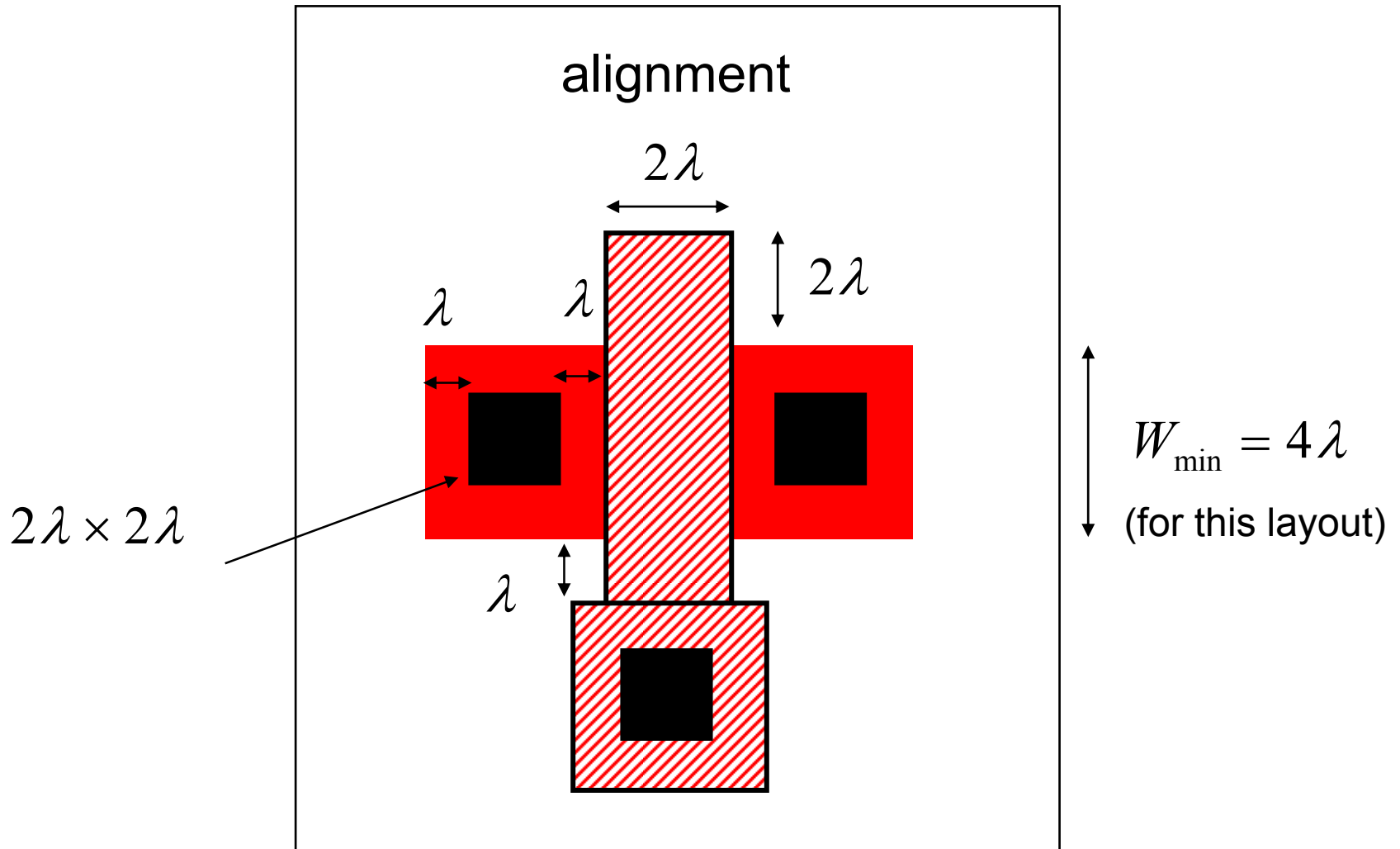


2-input NAND gate

AND		
A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

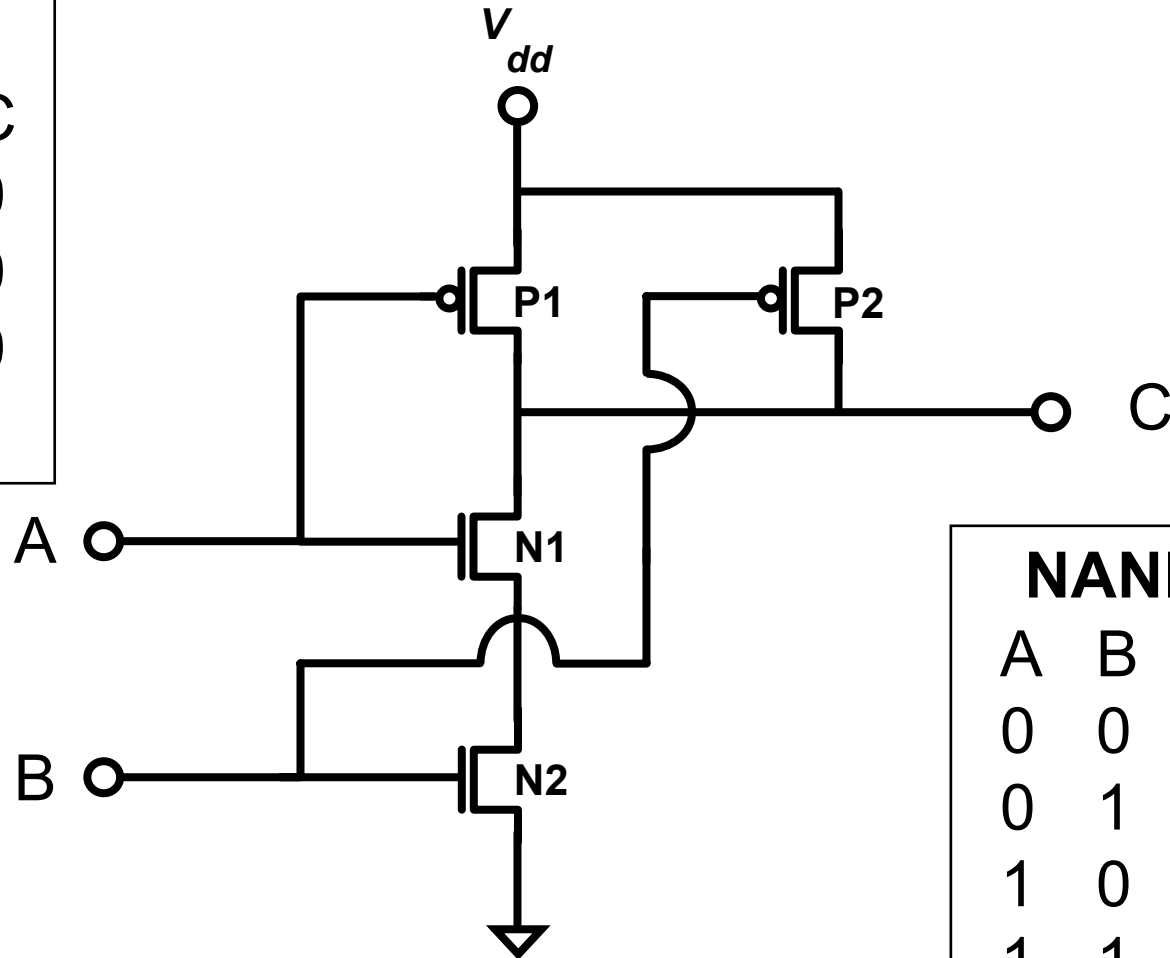


NAND		
A	B	C
0	0	1
0	1	1
1	0	1
1	1	0


dynamic logic: NOR gate

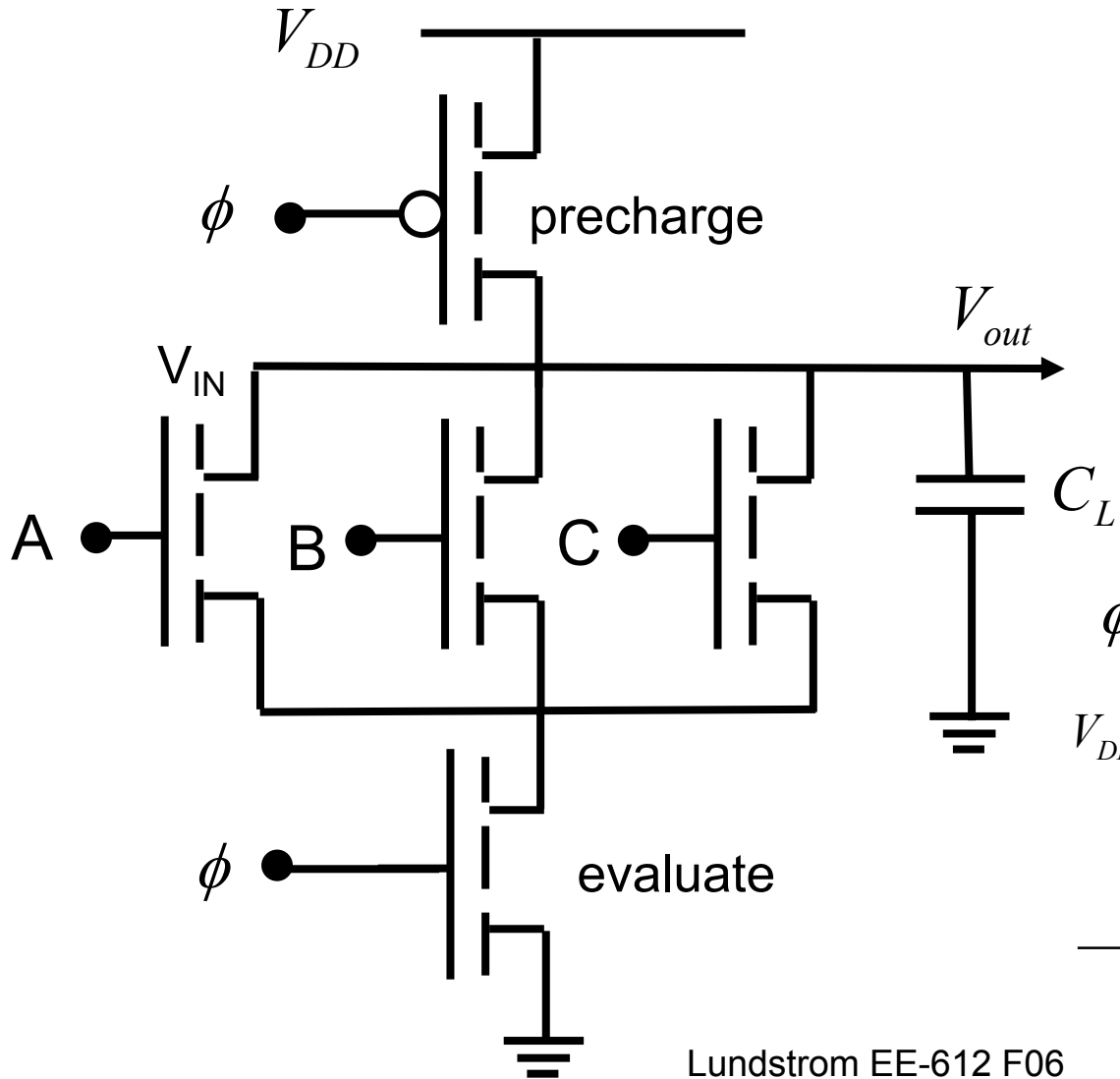

A	B	C	OUT
0	0	0	1
0	1	0	0


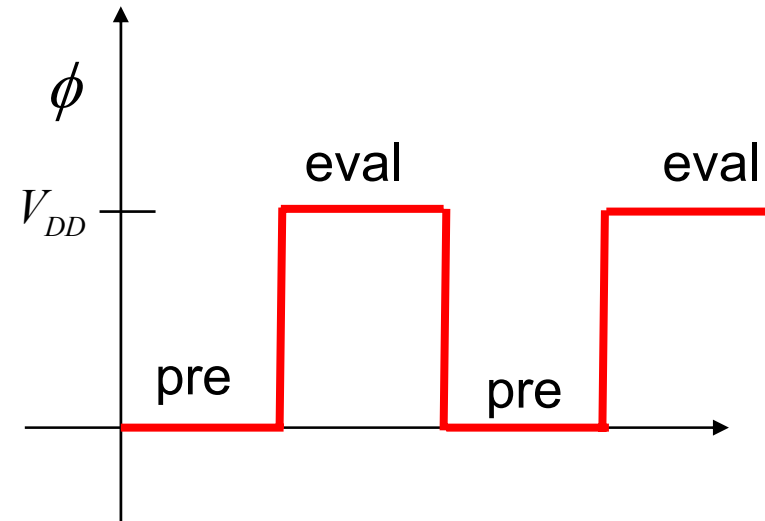


dynamic logic

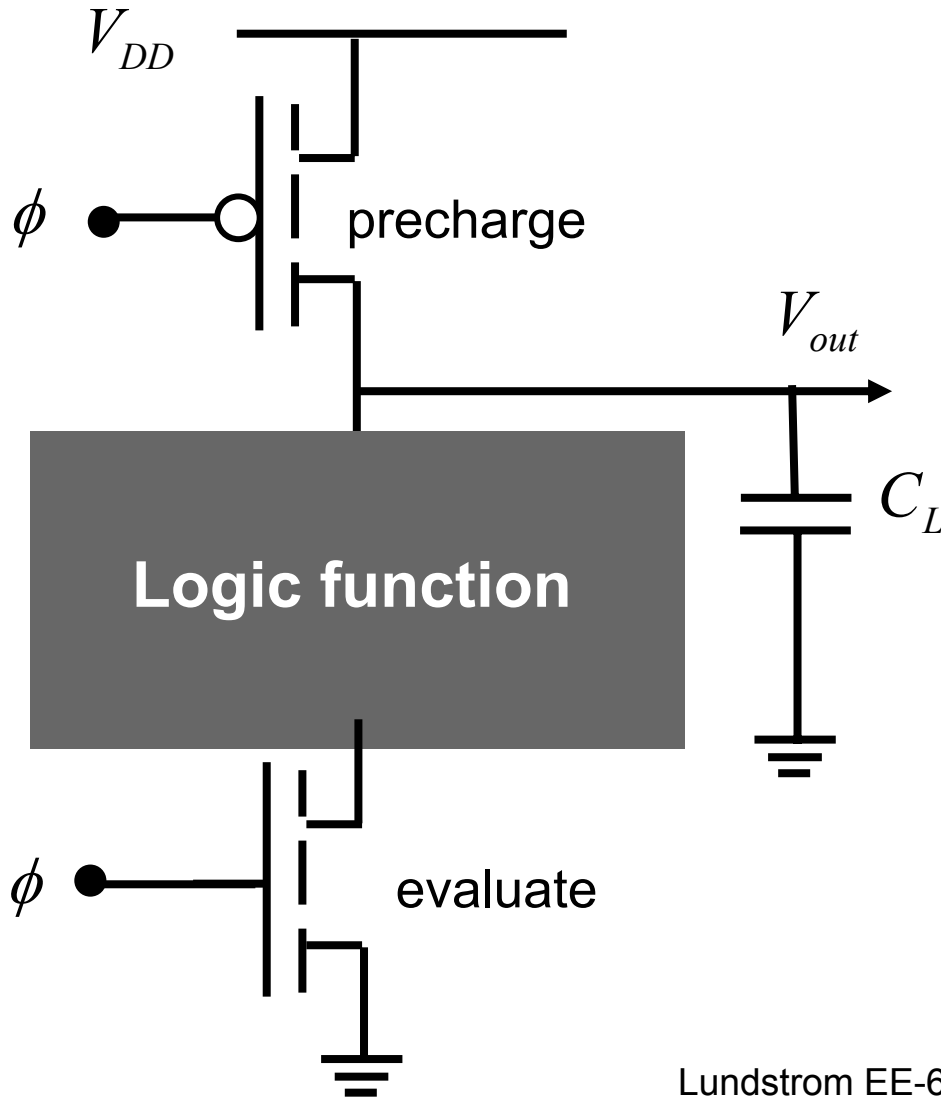


- M-input logic needs M+2 transistors (2M for CMOS)
- 'no' standby power
- minimum frequency

transmission gates

  


transmission gates: high to low

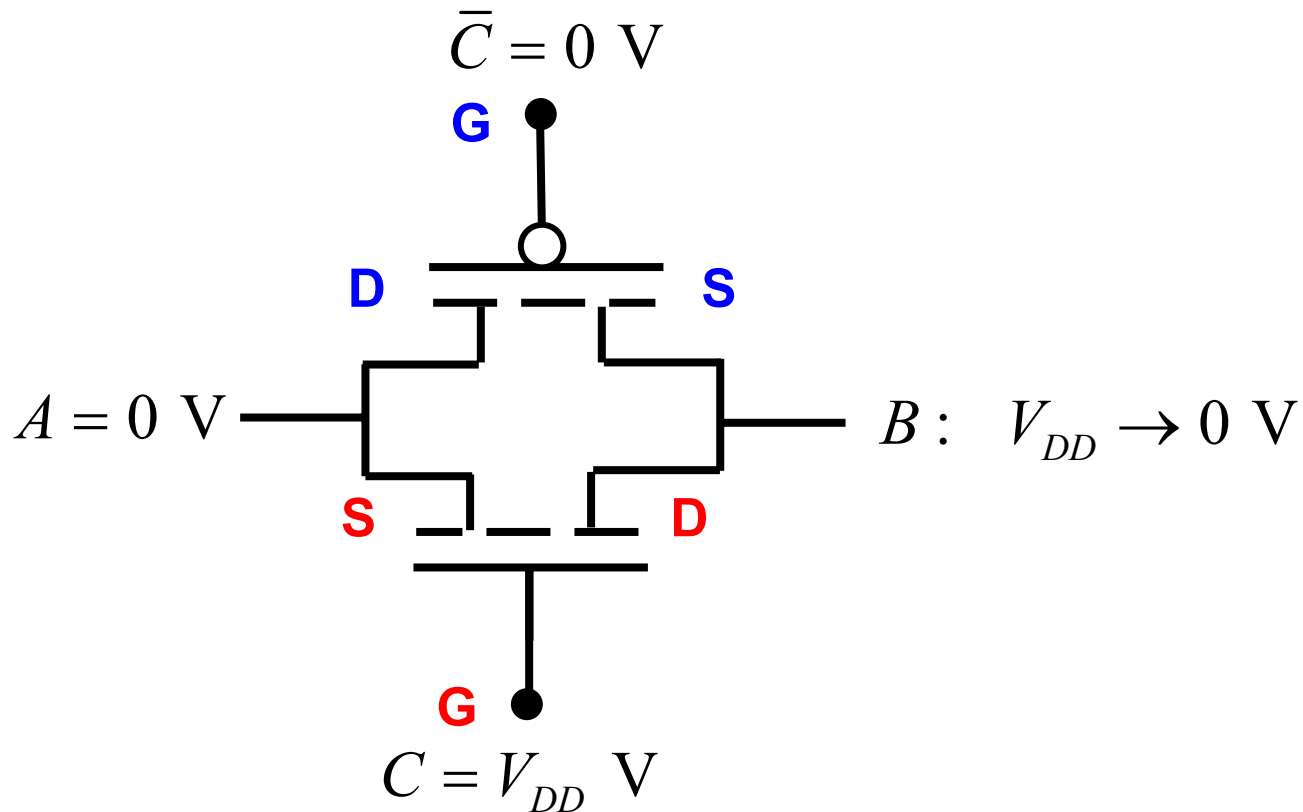


NMOS can discharge the output all the way to 0V;
PMOS can't.

transmission gates: low to high

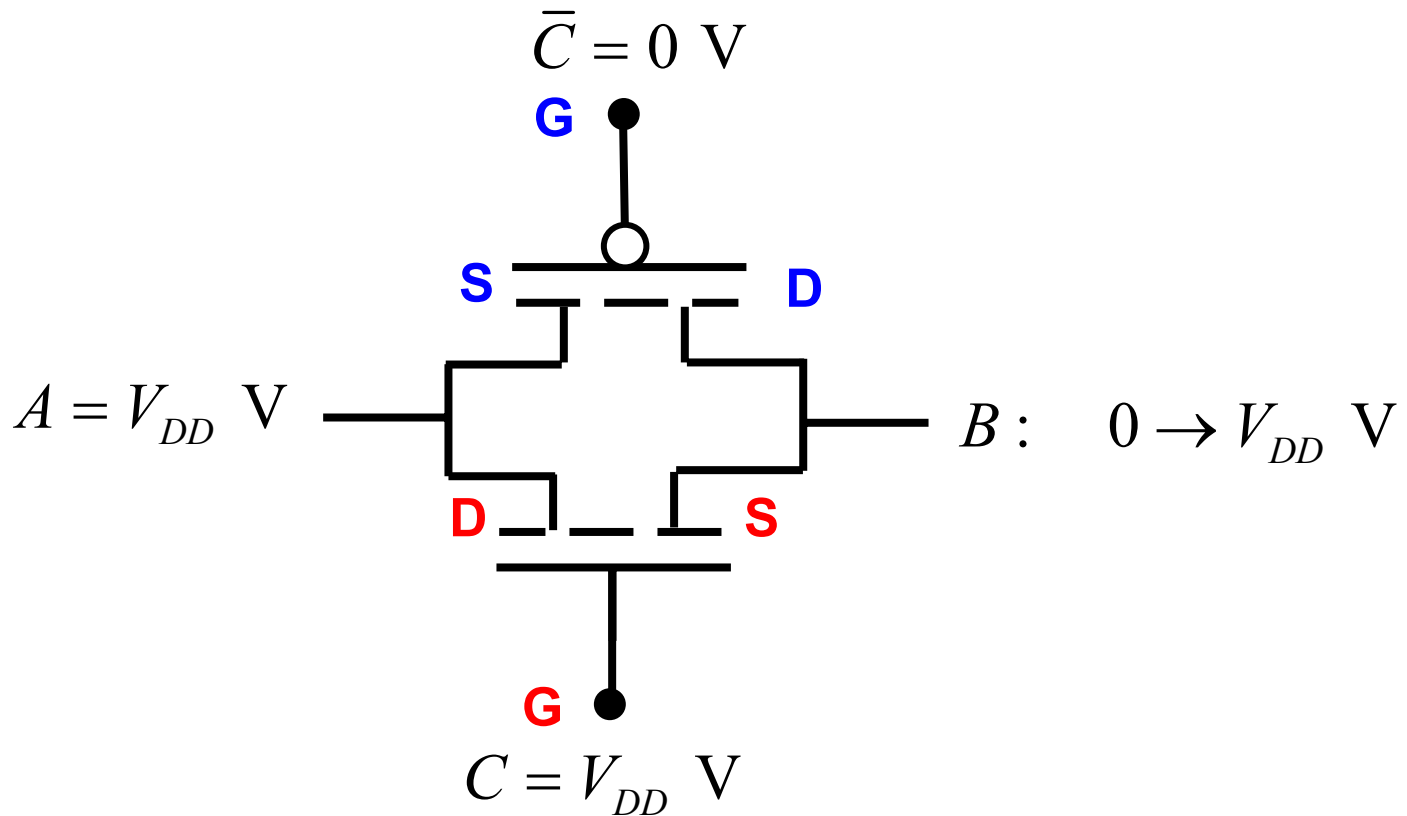


PMOS can charge the output all the way to V_{DD} V;
NMOS can't.

multiplexer with transmission gates

 


From Hodges, Jackson, and Saleh, *Analysis and Design of Digital Integrated Circuits, 3rd Ed.*, McGraw-Hill, 2004.

memories

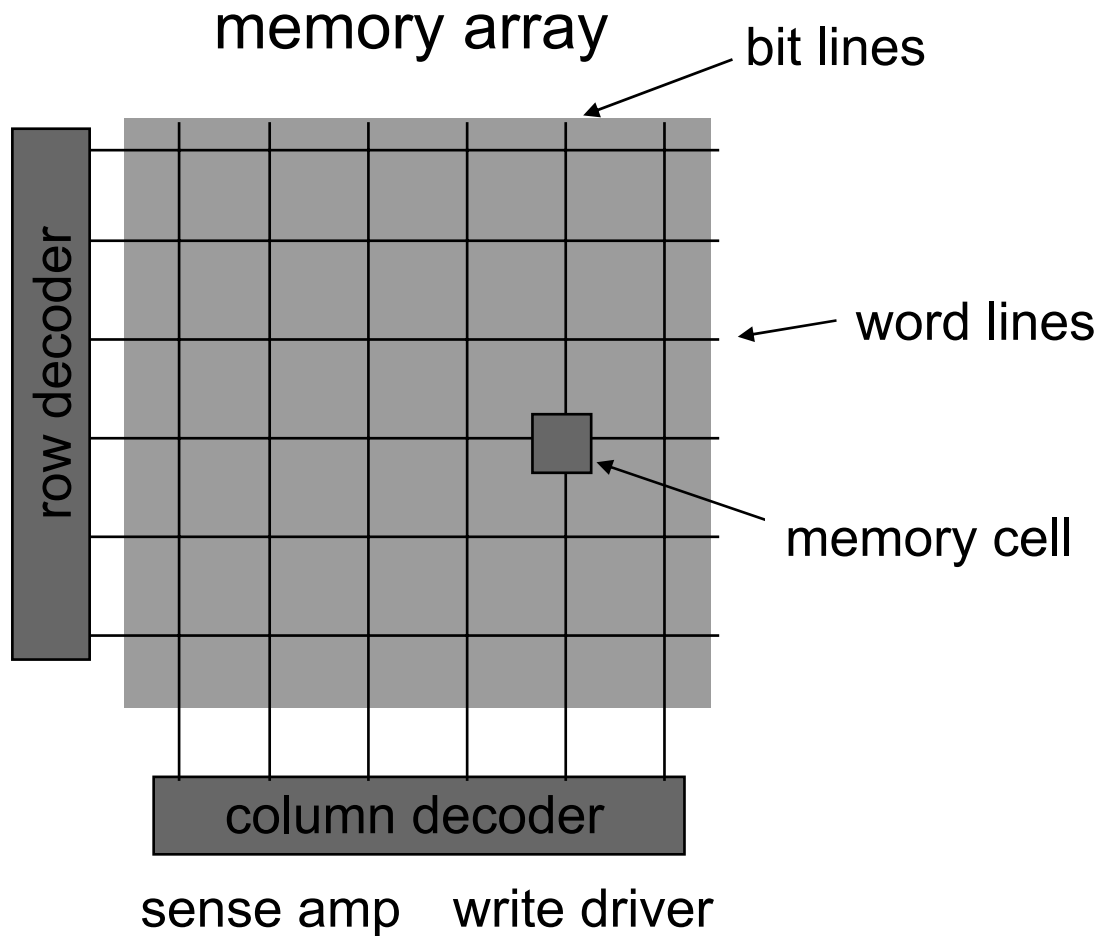


SRAM
DRAM
Flash, etc.

SRAM cell

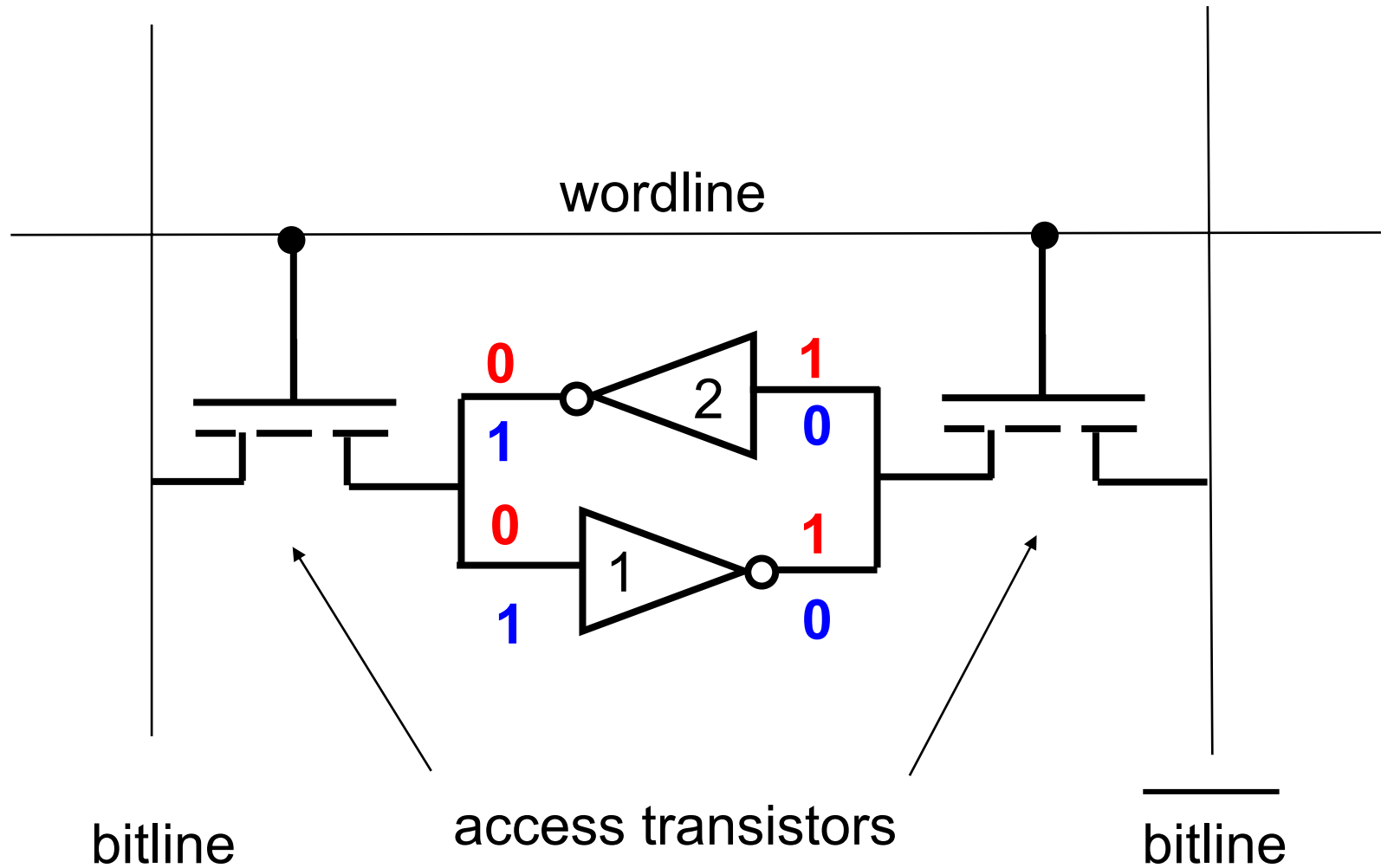

6 transistor SRAM cell

 

6 transistor SRAM cell (ii)

- SRAM consumes most of the area on a CPU chip
- steady state power determined by leakage (use high V_T)
- small area with optimized layout
- minimum W/L - sensitive to variations


for more information on CMOS circuits

Hodges, Jackson, and Saleh,
Analysis and Design of Digital Integrated Circuits, 3rd Ed.,
McGraw-Hill, 2004.


Outline

- 1) Review
- 2) CMOS circuits
- 3) The CMOS inverter**
- 4) Speed


CMOS inverter

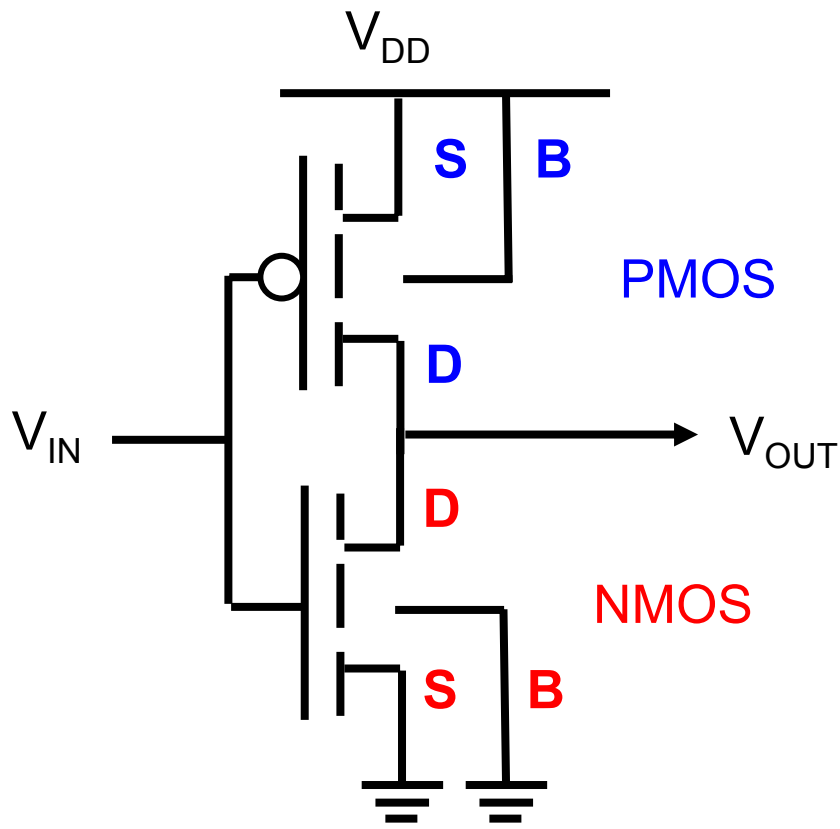

transfer characteristic

 

CMOS inverter: voltages

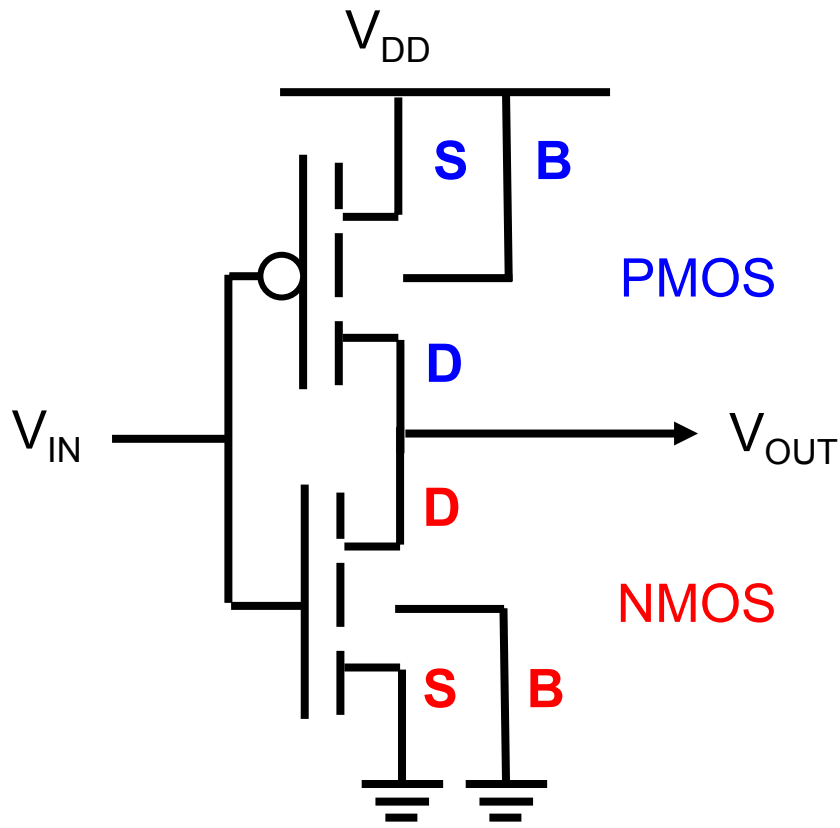

$$V_{gs} = V_{in} - V_{DD}$$

$$V_{ds} = V_{out} - V_{DD}$$

$$V_{gs} = V_{in}$$

$$V_{ds} = V_{out}$$

CMOS inverter: transfer characteristic


$$V_{gs} = V_{in} - V_{DD}$$

$$V_{ds} = V_{out} - V_{DD}$$

$$V_{in} : 0 \rightarrow V_{DD}$$


$$V_{gs} = V_{in}$$

$$V_{ds} = V_{out}$$

 

sizing the P-MOSFET

130 nm technology ($L_G = 60$ nm)

 


I-V curves for low V_T device

Intel Technical J., Vol. 6, May 16, 2002.


CMOS inverter: V_{out} vs. V_{in}

$$V_{DD} = 1.0 \text{ V}$$


$$V_{TN} = -V_{TP} = 0.15 \text{ V}$$

 


CMOS VTC

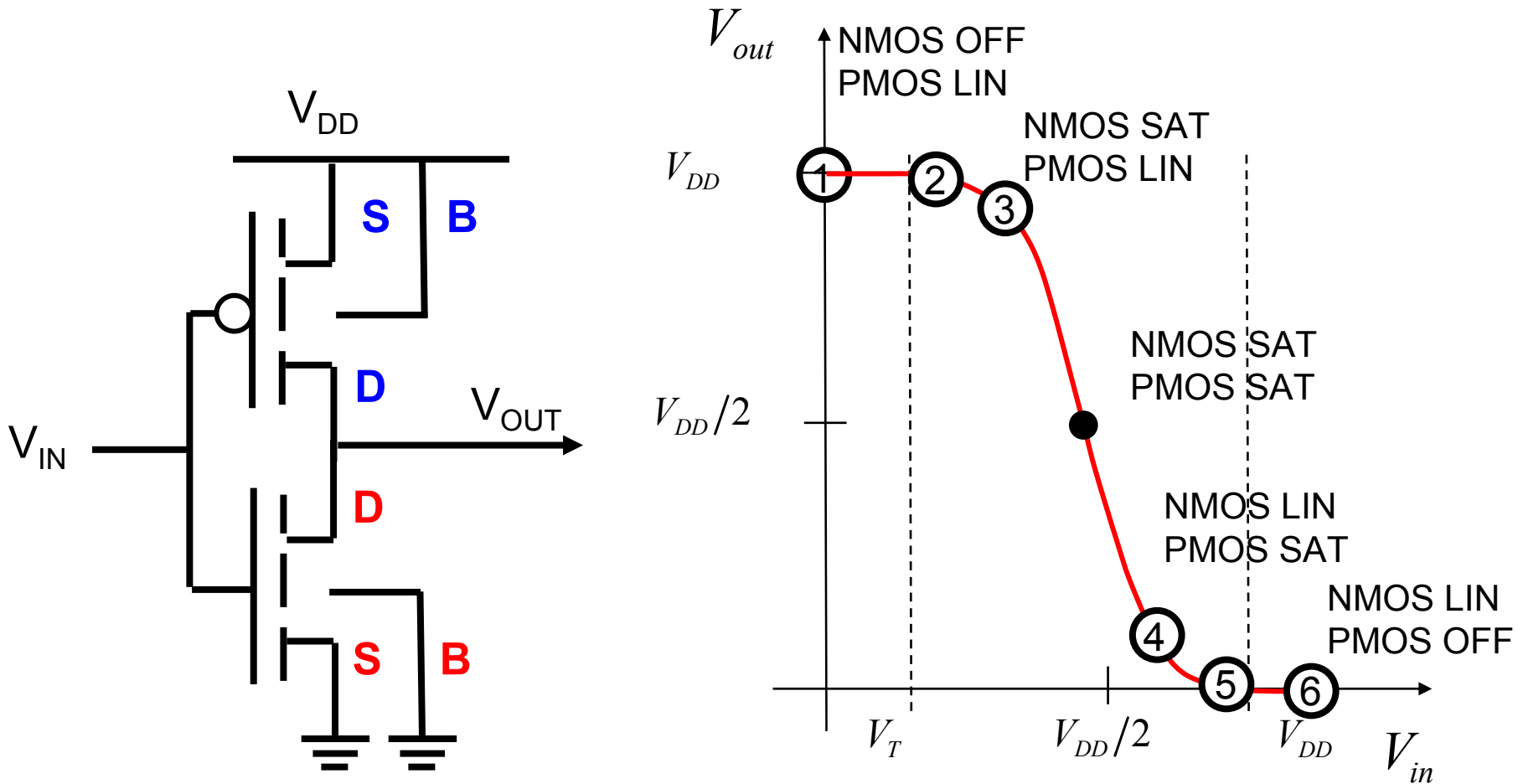


CMOS inverter: current

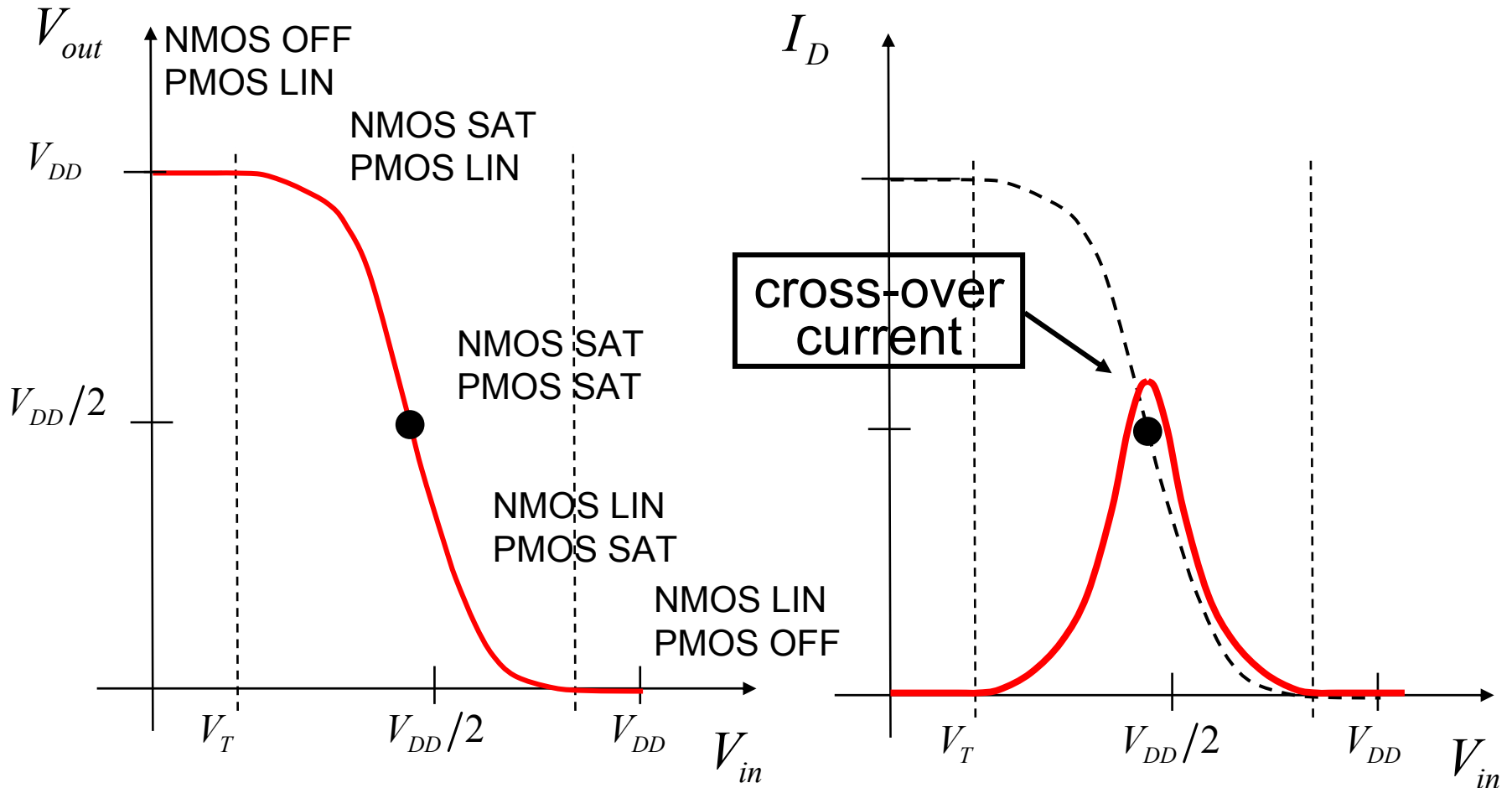


CMOS inverter: noise margins

 

importance of gain

 


approximate noise margins

 

CMOS inverter: summary

'pull up'
transistor

V_{DD}

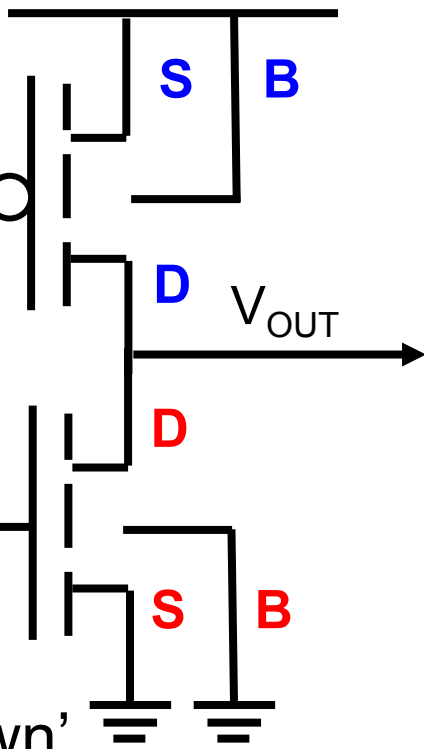

'pull down'
transistor




- 1) little current flow (power dissipation) unless switching
- 2) good noise margins if device has high R_{OUT} (high gain)

next: understand speed and power



Outline

- 1) Review
- 2) CMOS circuits
- 3) The CMOS inverter
- 4) **Speed**

CMOS inverter

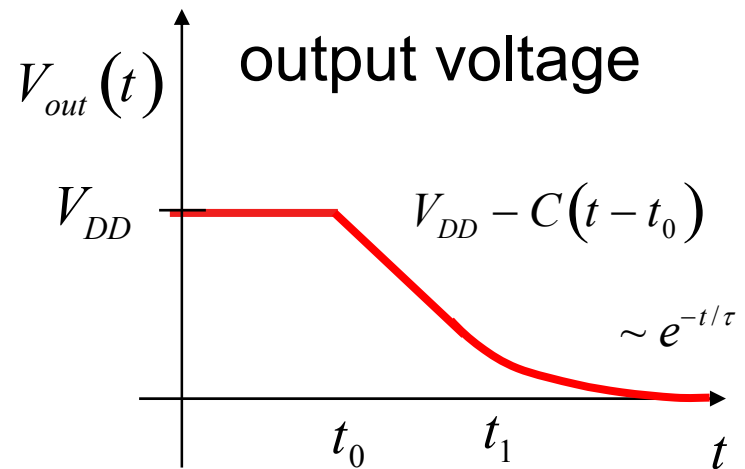  

discharging time

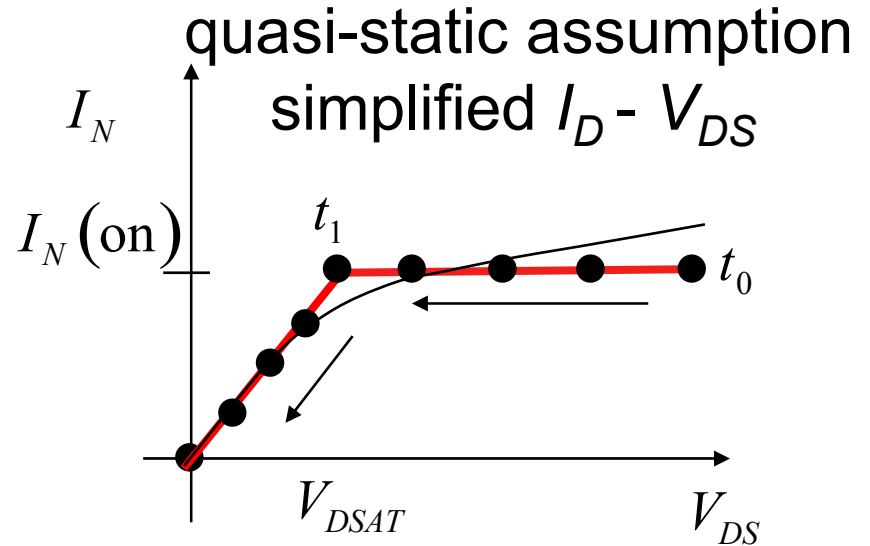 

$$I_d(t) = -C_{TOT} \frac{dV_{out}(t)}{dt}$$

$$V_{out}(t) = V_{DD} - \frac{I_N(\text{on})}{C_T} (t - t_0)$$



$$t_0 < t < t_1$$

$$\tau = R_{CH} C_{TOT} \quad R_{CH} = V_{DSAT} / I_N(\text{on})$$

$$V_{out}(t) = V_{out}(t_1) e^{-t/\tau}$$

$$t_0 < t < t_1$$

propagation delay (H-L)

  


$$V_{out}(t) = V_{DD} - \frac{I_N(\text{on})}{C_T} (t - t_0) \quad t_0 < t < t_1$$

$$V_{DD} / 2 = V_{DD} - \frac{I_N(\text{on})}{C_{TOT}} \tau_n$$

$$\tau_n = \frac{C_{TOT} V_{DD}}{2 I_N(\text{on})} \equiv R_{sw} C_{TOT}$$

$$R_{sw} = k_n \frac{V_{DD}}{I_N(\text{on})} \quad k_n = \frac{1}{2}$$

loaded propagation delay

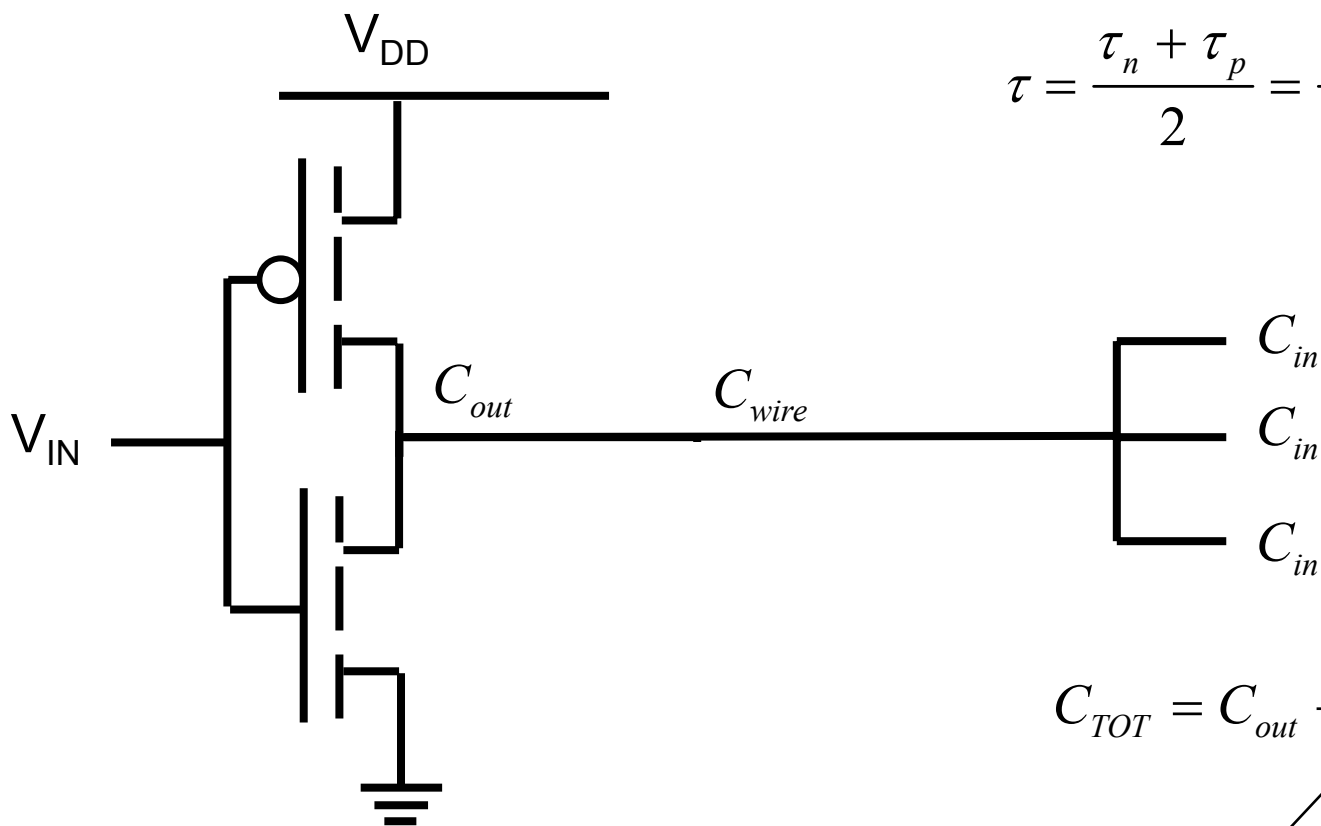


$$\tau = \frac{\tau_n + \tau_p}{2} = \frac{(R_{sw_n} + R_{sw_p})}{2} C_{TOT}$$

$$C_{TOT} = C_{out} + C_L + FO \times C_{in}$$

interconnect C

use of buffers

 


$$\tau = R_{sw} (C_{out} + C_L)$$

Can we do better?

$$C_{TOT} \gg C_{in}$$

delay with buffers

 

$$\tau = R_{sw} (C_{out} + C_L)$$

$$\tau_{buf} = \tau_1 + \tau_2$$

$$\tau_1 = R_{sw} (C_{out} + kC_{in2})$$

$$\tau_2 = \frac{R_{sw}}{k} (kC_{out} + C_L)$$

delay with buffers (ii)

$$\tau = R_{sw} (C_{out} + C_L)$$

$$\tau_{buf} = \tau_1 + \tau_2$$

$$\tau_1 = R_{sw} (C_{out} + kC_{in2})$$

$$\tau_2 = \frac{R_{sw}}{k} (kC_{out} + C_L)$$

$$\tau_{buf} = R_{sw} (C_{out} + kC_{in}) + \frac{R_{sw}}{k} (kC_{out} + C_L)$$

$$\tau_{buf} = R_{sw} \left(2C_{out} + kC_{in} + \frac{C_L}{k} \right)$$

$$\frac{d\tau_{buf}}{dk} = 0 \Rightarrow k_{min} = \sqrt{\frac{C_L}{C_{in}}}$$

$$\tau_{buf}(\min) = R_{sw} \left(2C_{out} + 2\sqrt{C_{in} C_L} \right)$$


$$C_L \gg C_{in}, C_{out}$$

$$\tau_{buf} / \tau = 2\sqrt{C_{in} / C_L} \ll 1$$

For very heavy loads, use multi-stage buffers.
See Taur and Ning, HW probs. 5.7 - 5.10


delay vs. load C
 
$$\tau = \frac{(R_{swi} + R_{swp})}{2} C_{TOT} = R_{sw} (C_{out} + FO \times C_{in} + C_{wire})$$



(see Fig. 5.29
Taur and Ning)

C_{in} and C_{out}


 


$$C_{in} = [C_G + C_{OV} + C_{OV}]_N + [C_G + C_{OV} + C_{OV}]_P$$

$$C_{GN} = C_{OX}W_NL$$

$$C_{out} = [C_J + C_{OV}]_N + [C_J + C_{OV}]_P$$

Miller C

  

capacitors connected between input and output require a special treatment

Outline

- 1) Review
- 2) CMOS circuits
- 3) The CMOS inverter
- 4) Speed

to be continued.....