 


# **EE-612:**

# **Lecture 25:**

# **CMOS Circuits: Part 2**

**Mark Lundstrom**  
Electrical and Computer Engineering  
Purdue University  
West Lafayette, IN USA  
Fall 2006



[www.nanohub.org](http://www.nanohub.org)

Lundstrom EE-612 F06


**PURDUE**  
UNIVERSITY

# Outline


---

- 1) Review
- 2) Speed (continued)
- 3) Power
- 4) Circuit performance


# CMOS inverter

 

transfer characteristic

 

# importance of gain

 


# outline

---

- 1) Review
- 2) Speed (continued)**
- 3) Power
- 4) Circuit performance

# CMOS inverter speed

 


$$\tau = \frac{1}{2} \left( \frac{C_{TOT} V_{DD}}{2I_N(\text{on})} + \frac{C_{TOT} V_{DD}}{2I_P(\text{on})} \right)$$

$$\tau = \frac{(R_{swN} + R_{swP})}{2} C_{TOT}$$



$$\tau = R_{sw} C_{TOT}$$

$$R_{swn} = k_n \frac{V_{DD}}{I_N(\text{on})} \quad k_n > \frac{1}{2}$$

# loaded propagation delay

 



# Miller C

  

$$\left. \begin{array}{l} V_c(t \ll 0) = -V_{DD} \\ V_c(t \gg 0) = +V_{DD} \end{array} \right\} \quad \begin{array}{l} \Delta V_c = 2V_{DD} \\ \Delta Q_c = \Delta V_c C_{OV} = 2V_{DD} C_{OV} = C_M V_{DD} \end{array}$$
  
# on-current determines circuit speed

$$\tau = R_{sw} C_{TOT} \quad R_{sw} \sim V_{DD} / I_D(\text{ON})$$



- 1) quasi-static assumption
- 2) simplified  $I_D - V_{DS}$

# metrics for circuit speed

---

K.K. Ng, et al., “Effective On-Current of MOSFETs for Large-Signal Speed Consideration,” IEDM, Dec., 2001.

M.H. Na, et al., “The Effective Drive Current in CMOS Inverters,” IEDM, Dec., 2002.

J. Deng and H.S.P. Wong, “Metrics for Performance Benchmarking of Nanoscale Si and Carbon Nanotube FETs Including Device Nonidealities,” *IEEE Trans. Electron Dev.*, **53**, pp. 1317-1366, 2006.


R. Venugopal, et al., “Design of CMOS Transistors to Maximize Circuit FOM Using a Coupled Process and Mixed Mode Simulation Methodology,” *IEEE Electron Dev. Lett.*, **53**, pp. 1317-1366, 2006.

# outline


---

- 1) Review
- 2) Speed
- 3) Power**
- 4) Circuit performance

# power

 


# discharge cycle

 

$$E_C(0) = \frac{1}{2} C_{TOT} V_{DD}^2$$

$$E_C(T/2) = 0$$


 
$$P_{dynamic} = \frac{\Delta E}{T/2} = \frac{C_{TOT} V_{DD}^2}{T}$$



$$P_{dynamic} = \alpha f C_{TOT} V_{DD}^2$$

switching activity

# discharge through a resistor

  


$$V_C(t) = V_c(0)e^{-t/RC_{TOT}} = V_{DD} e^{-t/\tau}$$

$$V_c(t) \quad P_R(t) = V_C^2(t)/R$$



$$\begin{aligned} P_{AVE} &= \frac{\int_0^{T/2} P_R(t) dt}{T/2} \\ &= \frac{2}{T} \int_0^{T/2} \frac{V_{DD}^2}{R} e^{-2t/\tau} dt \\ &= f C_{TOT} V_{DD}^2 \end{aligned}$$
 
# charging cycle

does it take power to put energy in the capacitor?



# charging cycle (ii)

  

$$E_C(0) = 0$$

$$E_C(T / 2) = \frac{1}{2} C_{TOT} V_{DD}^2$$



$$E_B = \int_0^{T/2} V_{DD} i(t) dt$$

$$E_B = V_{DD} \int_0^{T/2} i(t) dt = V_{DD} Q$$

$$E_B = V_{DD} Q = C_{TOT} V_{DD}^2$$

$$E_{diss} = \frac{1}{2} C_{TOT} V_{DD}^2$$

# charging cycle (iii)

  

$$i(t) = C_{TOT} \frac{dV_c}{dt}$$

$$V_c(t) = V_{DD} - i(t)R$$


$$i(t) = -RC_{TOT} \frac{di}{dt}$$

$$i(t) = i(0^+) e^{-t/\tau} = (V_{DD}/R) e^{-t/\tau}$$

$$E_B = \int_0^{T/2} V_{DD} i(t) dt = C_{TOT} V_{DD}^2$$

$$E_{diss} = \frac{1}{2} C_{TOT} V_{DD}^2$$

# adiabatic charging

 

$$i(t) = C_{TOT} \frac{dV}{dt} = C_{TOT} \frac{V_{DD}}{T}$$

$$P_R = i^2 R = \left( \frac{C_{TOT} V_{DD}}{T} \right)^2 R$$

$$E_{diss} = \int_0^T P_R dt = \frac{C_{TOT}^2 V_{DD}^2}{T^2} RT$$

$$E_{diss} = C_{TOT} V_{DD}^2 \left( \frac{R C_{TOT}}{T} \right)$$

# outline

---

- 1) Review
- 2) Speed
- 3) Power
- 4) Circuit performance**
- 5) CMOS circuit metrics

# device impact on circuit performance

---

Question:

Given a technology, how does circuit performance depend on transistor design ( $W$ ,  $T_{ox}$ ,  $V_{DD}$ , etc.)

Taur and Ning assume a 250nm technology and explore this question by Spice simulation (see pp. 264 - 279). Can we understand the major trends simply?

# effect of transistor $W$ on delay

$$\tau = \frac{(R_{swn} + R_{swp})}{2} C_{TOT} = R_{sw} C_{TOT}$$

$$C_{TOT} = C_{out} + C_{wire} + FO \times C_{in}$$

$$R_{sw} = k V_{DD} / I_D(\text{on})$$

$$C_{out} \sim W$$

$$I(\text{on}) \sim W$$

$$C_{in} \sim W$$

$$R_{sw} \sim 1/W$$

# loaded vs. unloaded delay

---

$$\tau = R_{sw} C_{TOT} = R_{sw} (C_{out} + FO \times C_{in} + C_{wire})$$

i) *unloaded:*

$C_{in}$  and  $C_{out}$  dominate,  $C_{TOT} \sim W$   
-->  $\tau$  **independent of  $W$**

ii) *loaded:*

$C_L$  dominates,  $C_{TOT} \sim$  *independent of  $W$*   
-->  $\tau \sim 1/W$

# effect of $T_{OX}$ on delay

---

$$\tau = R_{sw} C_{TOT} = R_{sw} (C_{out} + FO \times C_{in} + C_L)$$

i) intrinsic delay ( $C_L = 0$ )

$$\left. \begin{array}{l} R_{sw} = kV_{DD} / I_D(\text{ON}) \sim T_{OX} \\ C_{in} \sim 1/T_{OX} \\ C_{out} \quad \text{constant} \end{array} \right\} \quad \tau_{\text{int}} \sim \text{constant}$$

ii) loaded delay ( $C_L > 0$ )

$$\left. \begin{array}{l} \tau_{loaded} \approx R_{sw} C_L \end{array} \right\} \quad \tau_{loaded} \uparrow \quad \text{as} \quad T_{OX} \uparrow$$

(see Fig. 5.32 of Taur and Ning)

# effect of $L$ on delay

$$\tau = R_{sw} C_{TOT} = R_{sw} (C_{out} + FO \times C_{in} + C_L)$$

$$R_{sw} = kV_{DD} / I_D(\text{ON})$$

$$I_D(\text{ON}) = W C_{OX} v(0) (V_{GS} - V_T) \downarrow \text{ as } L \uparrow$$

$$R_{sw} \uparrow \text{ as } L \uparrow$$

$$C_{in} \sim L$$

$$C_{out}, C_L \text{ constant}$$

$$\left. \begin{array}{l} \\ \\ \\ \end{array} \right\} \tau \uparrow \text{ as } L \uparrow$$

(see Fig. 5.31 of Taur and Ning)

# effect of $V_{DD}$ on delay

---

$$\tau = R_{sw} C_{TOT} = R_{sw} (C_{out} + FO \times C_{in} + C_L)$$

$$R_{sw} = kV_{DD} / I_D(\text{ON})$$

$$I_D(\text{ON}) = W C_{OX} v(0) (V_{GS} - V_T)$$


$$R_{sw} \sim V_{DD} / (V_{DD} - V_T)$$

$$R_{sw} \sim 1 / (1 - V_T / V_{DD})$$

$$C_{out} = \epsilon_{Si} / W_D \sim 1 / \sqrt{V_{DD} + V_{bi}}$$

$$\left. \begin{array}{l} \\ \\ \\ \end{array} \right\} \quad \tau \sim \frac{1}{1 - V_T / V_{DD}}$$

# delay vs. $V_{DD}$

 

$$I_D(\text{off}) \sim e^{-qV_T/mk_{BT}}$$

(see Fig. 5.33 of Taur and Ning)

# power-delay trade-off

---

circuit speed:

$$\tau \sim V_{DD} / (V_{DD} - V_T) \quad f \sim (1 - V_T / V_{DD})$$

dynamic (switching) power:


$$P_{dynamic} = \alpha f C_{TOT} V_{DD}^2 \sim V_{DD}^2 (1 - V_T / V_{DD})$$

static (leakage) power:

$$P_{static} \sim I_D(\text{OFF}) V_{DD} \sim e^{-qV_T/mk_B T} V_{DD}$$
 
# power-delay trade-off

$$P_{dynamic} \sim V_{DD}^2 \left(1 - V_T / V_{DD}\right)$$



(see Fig. 5.34 of Taur and Ning)

# Outline

---

- 1) Review
- 2) Speed
- 3) Power
- 4) Circuit performance
- 5) CMOS circuit metrics**

# key metrics

---

1) Switching energy:

$$E_S = \frac{1}{2} C V_{DD}^2$$

2) Switching delay:

$$\tau_S = \frac{C V_{DD}}{I_D(\text{ON})}$$

3) Dynamic power:

$$P_D = \alpha f C V_{DD}^2$$

4) Energy-delay product:

$$E_S \tau = \frac{1}{2} \frac{C^2 V_{DD}^3}{I_D(\text{on})}$$

# the energy-delay metric

---

Energy-delay product:

$$E_S \tau = \frac{1}{2} \frac{C^2 V_{DD}^3}{I_D(\text{on})} \sim \frac{V_{DD}^3}{(V_{DD} - V_T)}$$

Minimum energy-delay product:

$$\frac{\partial(E_S \tau)}{\partial V_{DD}} = 0 \Rightarrow V_{DD}^{opt} = 1.5V_T$$

# device metrics for 65 nm technology node

---

1) Switching energy:

$$E_s = \frac{1}{2} CV_{DD}^2 \approx 21 \text{ aJ}$$

2) Switching delay:

$$\tau_s = \frac{CV_{DD}}{I_D(\text{ON})} = 0.64 \text{ ps}$$

3) Dynamic power:

$$P_D = \alpha f CV_{DD}^2$$

4) Energy-delay product:

$$E_s \tau = \frac{1}{2} \frac{C^2 V_{DD}^3}{I_D(\text{on})} = 1.4 \times 10^{-29} \text{ J-s}$$

# circuit performance (high-speed logic)

---

Typical power dissipation of a logic chip: 100 W

Dissipation of logic core:  $\approx 20$  W

$$P_{core} = N_{core} \frac{C_S V_{DD}^2}{2} f\alpha = 10^7 \times \frac{C_S \times 1^2}{2} \times (4 \times 10^9) \times 10^{-1}$$

$$C_S \approx 10 \text{ fF/node}$$

Average switching energy:  $E_S \approx \frac{C_S V_{DD}^2}{2} = 6,000 \text{ aJ}$

Energy-delay product:  $E_S \tau \approx 1.5 \times 10^{-24} \text{ J-s}$

# from device to circuit

---

	device	circuit	increase
delay:	0.64 ps	250 ps	$\sim 400 \times$
switching energy:	21 aJ	6000 aJ	$\sim 300 \times$
energy-delay:	$\sim 10^{-29}$ J-s	$\sim 10^{-24}$ J-s	$\sim 100,000 \times$

# Outline

---

- 1) Review
- 2) Speed
- 3) Power
- 4) Circuit performance
- 5) CMOS circuit metrics

# conclusions / questions

---

- 1) Device metrics aren't enough; the circuit is critical.
- 2) How close is CMOS to fundamental limits?