




Digital Design: An Embedded Systems Approach Using Verilog

Chapter 5 Memories

Portions of this work are from the book, *Digital Design: An Embedded Systems Approach Using Verilog*, by Peter J. Ashenden, published by Morgan Kaufmann Publishers, Copyright 2007 Elsevier Inc. All rights reserved.

General Concepts

 
- A memory is an array of storage locations
 - Each with a unique address
 - Like a collection of registers, but with optimized implementation
- Address is unsigned-binary encoded
 - n address bits $\Rightarrow 2^n$ locations
- All locations the same size
 - $2^n \times m$ bit memory



Memory Sizes

- Use power-of-2 multipliers
 - Kilo (K): $2^{10} = 1,024 \approx 10^3$
 - Mega (M): $2^{20} = 1,048,576 \approx 10^6$
 - Giga (G): $2^{30} = 1,073,741,824 \approx 10^9$
- Example
 - 32K × 32-bit memory
 - Capacity = 1,024K = 1Mbit
 - Requires 15 address bits
- Size is determined by application requirements


Basic Memory Operations

 

- a inputs: unsigned address
- d_in and d_out
 - Type depends on application
- Write operation
 - $en = 1, wr = 1$
 - d_in value stored in location given by address inputs
- Read operation
 - $en = 1, wr = 0$
 - d_out driven with value of location given by address inputs
- Idle: $en = 0$


Wider Memories

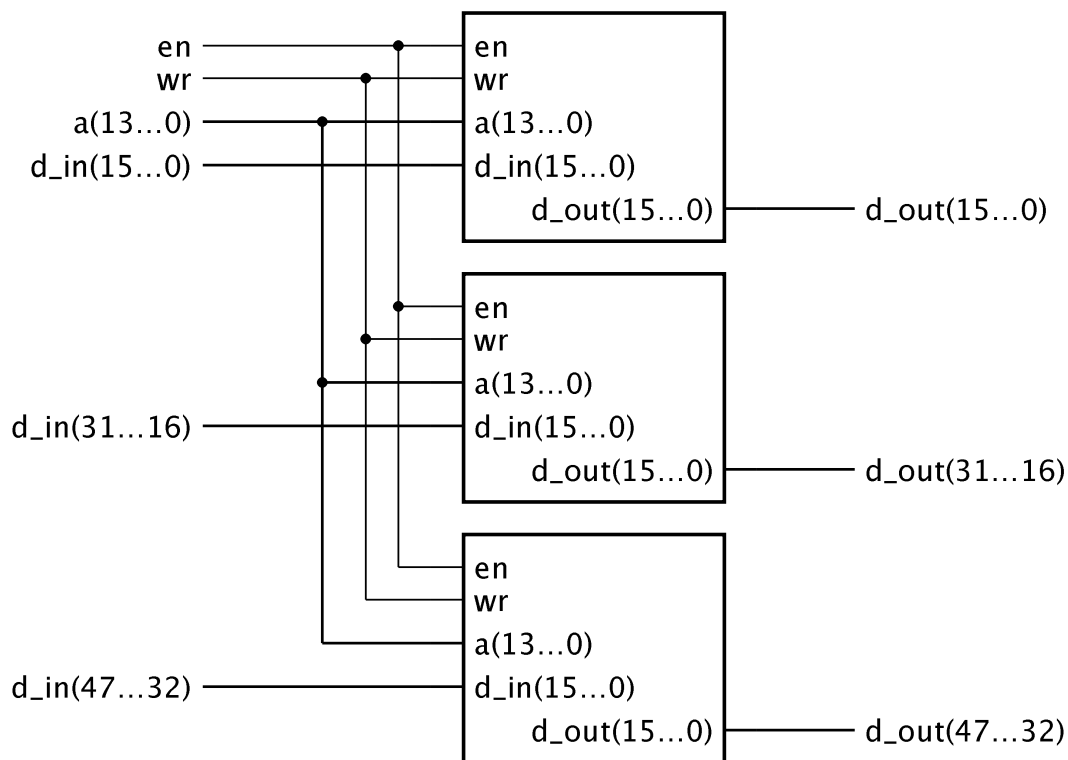- Memory components have a fixed width
 - E.g., $\times 1$, $\times 4$, $\times 8$, $\times 16$, ...
- Use memory components in parallel to make a wider memory
 - E.g, three $16\text{K} \times 16$ components for a $16\text{K} \times 48$ memory




More Locations

 - To provide 2^n locations with 2^k -location components
 - Use $2^n/2^k$ components
- Address A
 - at offset $A \bmod 2^k$
 - least-significant k bits of A
 - in component $\lfloor A/2^k \rfloor$
 - most-significant $n-k$ bits of A
 - decode to select component



More Locations

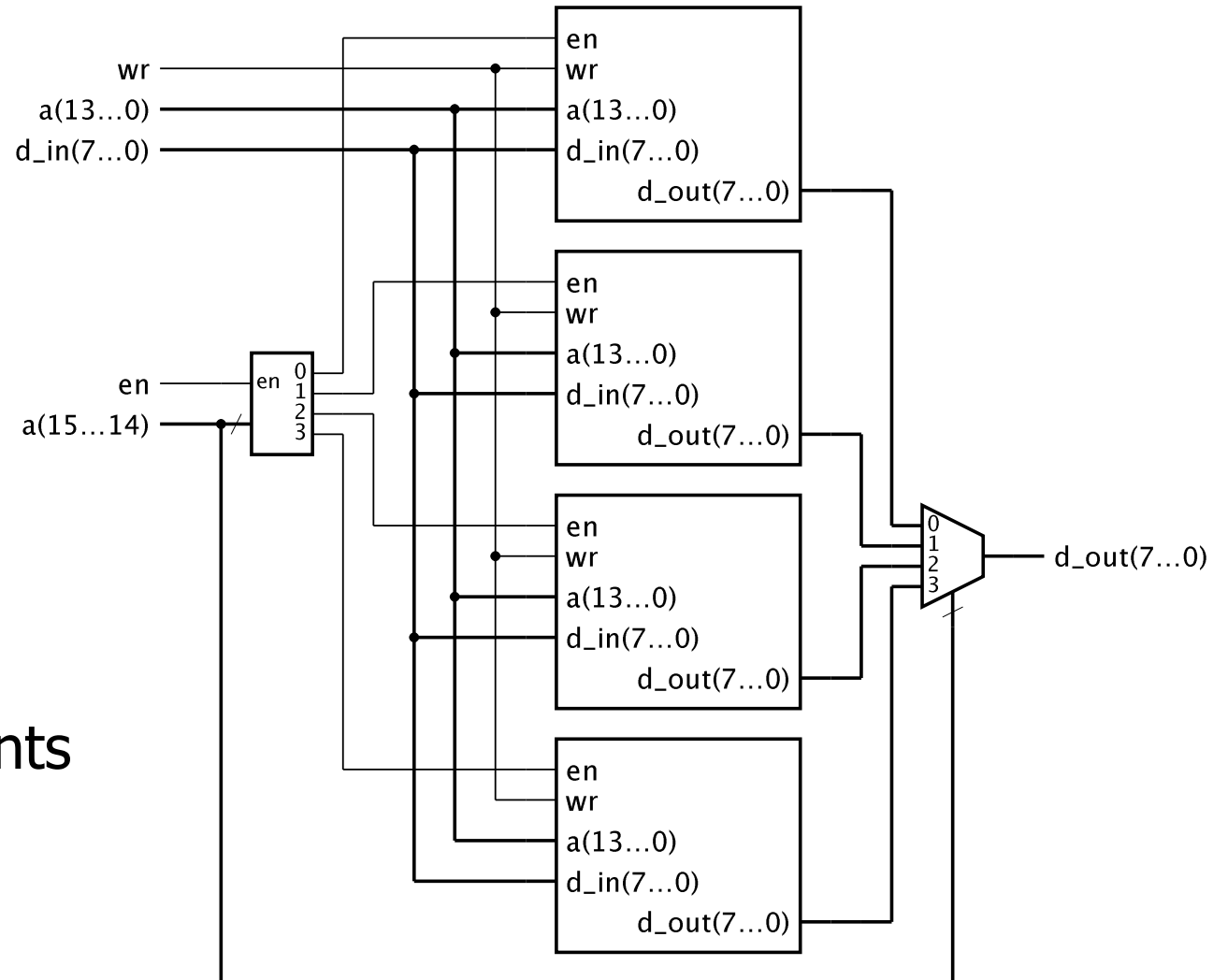- Example:
64K×8 memory
composed of
16K×8 components





Memory Types

- Random-Access Memory (RAM)
 - Can read and write
 - Static RAM (SRAM)
 - Stores data so long as power is supplied
 - Asynchronous SRAM: not clocked
 - Synchronous SRAM (SSRAM): clocked
 - Dynamic RAM (DRAM)
 - Needs to be periodically refreshed
- Read-Only Memory (ROM)
 - Combinational
 - Programmable and Flash rewritable
- Volatile and non-volatile

Asynchronous SRAM

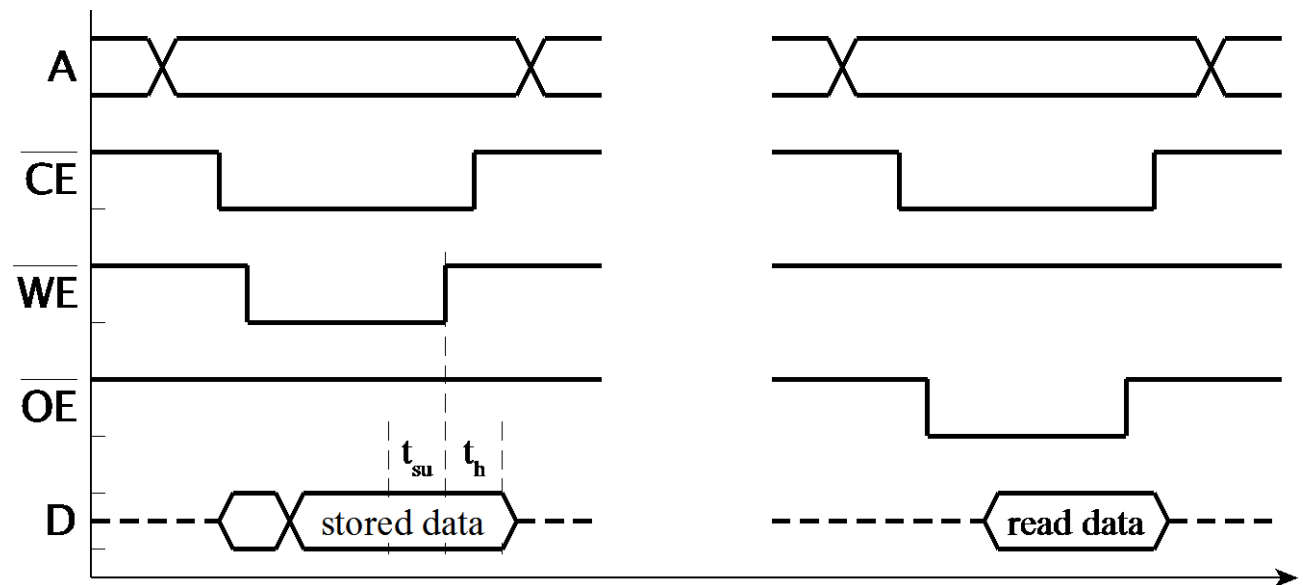 - Data stored in 1-bit latch cells
 - Address decoded to enable a given cell
- Usually use active-low control inputs
- Not available as components in ASICs or FPGAs



Asynch SRAM Timing

- Timing parameters published in data sheets
- Access time
 - From address/enable valid to data-out valid
- Cycle time
 - From start to end of access
- Data setup and hold
 - Before/after end of WE pulse
 - Makes asynch SRAMs hard to use in clocked synchronous designs

Example Data Sheet




CY7C1041BV33

Switching Characteristics^[4] Over the Operating Range

Parameter	Description	-12		-15		-17		Unit
		Min.	Max.	Min.	Max.	Min.	Max.	
READ CYCLE								
t_{RC}	Read Cycle Time	12		15		17		ns
t_{AA}	Address to Data Valid		12		15		17	ns
t_{OHA}	Data Hold from Address Change	3		3		3		ns
t_{ACE}	\overline{CE} LOW to Data Valid		12		15		17	ns
t_{DOE}	\overline{OE} LOW to Data Valid		6		7		8	ns
WRITE CYCLE^[7, 8]								
t_{WC}	Write Cycle Time	12		15		17		ns
t_{SCE}	\overline{CE} LOW to Write End	10		12		12		ns
t_{AW}	Address Set-Up to Write End	10		12		12		ns
t_{HA}	Address Hold from Write End	0		0		0		ns
t_{SA}	Address Set-Up to Write Start	0		0		0		ns
t_{PWE}	\overline{WE} Pulse Width	10		12		12		ns
t_{SD}	Data Set-Up to Write End	7		8		9		ns
t_{HD}	Data Hold from Write End	0		0		0		ns
t_{LZWE}	\overline{WE} HIGH to Low Z ^[6]	3		3		3		ns
t_{HZWE}	\overline{WE} LOW to High Z ^[5, 6]		6		7		8	ns
t_{BW}	Byte Enable to End of Write	10		12		12		ns


Synchronous SRAM (SSRAM)

 - Clocked storage registers for inputs
 - address, data and control inputs
 - stored on a clock edge
 - held for read/write cycle
- Flow-through SSRAM
 - no register on data output



Pipelined SSRAM

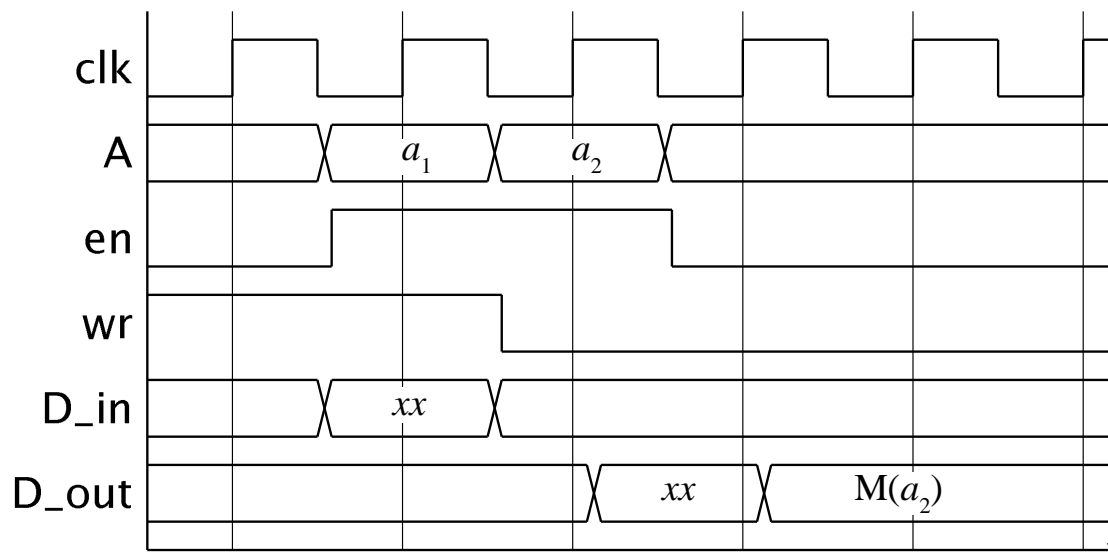- Data output also has a register
 - More suitable for high-speed systems
 - Access RAM in one cycle, use the data in the next cycle



Memories in Verilog

- RAM storage represented by an array variable

```
reg [15:0] data_RAM [0:4095];
...
always @(posedge clk)
  if (en)
    if (wr) begin
      data_RAM[a] <= d_in;  d_out <= d_in;
    end
  else
    d_out <= data_RAM[a];
```

Example: Coefficient Multiplier

```
module scaled_square ( output reg signed [7:-12] y,
                      input  signed [7:-12] c_in, x,
                      input                [11:0] i,
                      input                start,
                      input                clk, reset );

wire          c_ram_wr;
reg          c_ram_en, x_ce, mult_sel, y_ce;
reg signed [7:-12] c_out, x_out;
reg signed [7:-12] c_RAM [0:4095];
reg signed [7:-12] operand1, operand2;

parameter [1:0] step1 = 2'b00, step2 = 2'b01, step3 = 2'b10;
reg          [1:0] current_state, next_state;

assign c_ram_wr = 1'b0;
```

Example: Coefficient Multiplier

```
always @(posedge clk) // c RAM - flow through
  if (c_ram_en)
    if (c_ram_wr) begin
      c_RAM[i] <= c_in;
      c_out    <= c_in;
    end
    else
      c_out <= c_RAM[i];

always @(posedge clk) // y register
  if (y_ce) begin
    if (!mult_sel) begin
      operand1 = c_out;
      operand2 = x_out;
    end
    else begin
      operand1 = x_out;
      operand2 = y;
    end
    y <= operand1 * operand2;
  end
end
```


Example: Coefficient Multiplier

```
always @(posedge clk) // State register
...
always @* // Next-state logic
...
always @* begin // Output logic
...
endmodule
```

Pipelined SSRAM in Verilog

```
reg    pipelined_en;
reg [15:0] pipelined_d_out;
...

always @(posedge clk) begin
    if (pipelined_en) d_out <= pipelined_d_out;
    pipelined_en <= en;
    if (en)
        if (wr) begin
            data_RAM([a] <= d_in;  pipelined_d_out <= d_in;
        end
        else
            pipelined_d_out <= data_RAM[a];
end
```

output
register

SSRAM

Example: RAM Core Generator

