

CMSC 411

Computer Architecture

Lecture 14

Pipelined Datapath and Control



Lecture's Overview

Previous Lecture:


- An overview of pipelining
 - Pipelining concept is natural
 - Start handling of next instruction while current one is in progress
- Pipeline performance
 - Performance improvement by increasing instruction throughput
 - Ideal and upper bound for speedup is number of stages in pipeline
- Pipelined hazards
 - Structural, data and control hazards
 - Hazard resolution techniques

This Lecture:


- Designing a pipelined datapath
- Controlling pipeline operations



Multi-cycle Instruction Execution

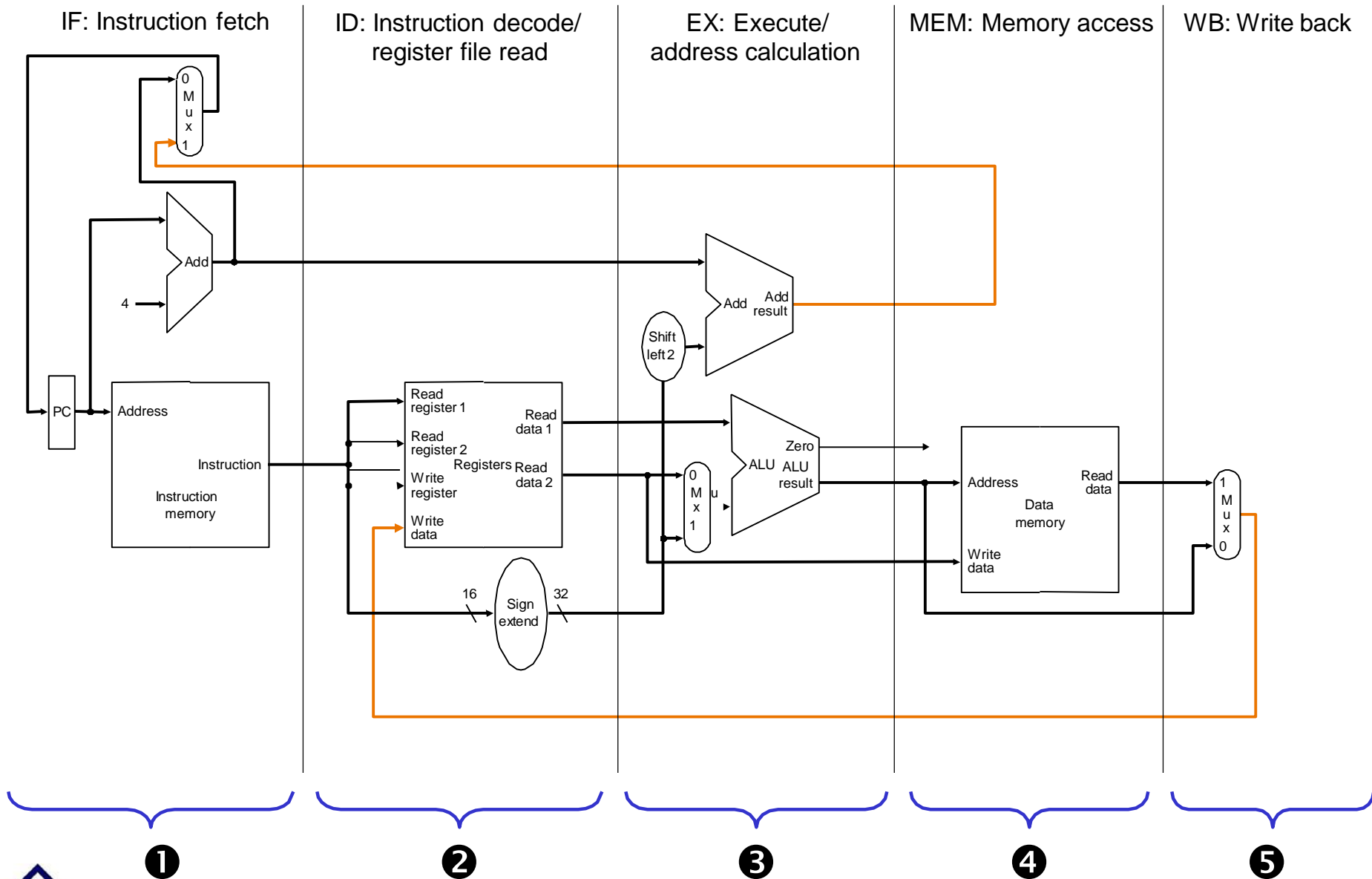


Stages of Instruction Execution

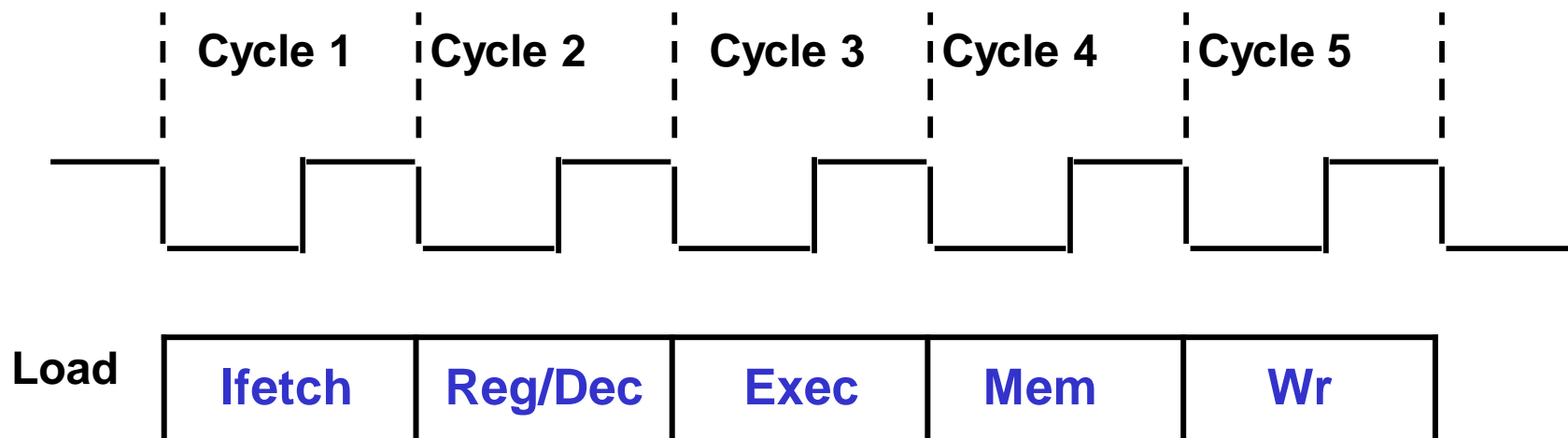

- ❑ The load instruction is the longest
- ❑ All instructions follows at most the following five steps:
 - ➔ **Ifetch:** Instruction Fetch
 - Fetch the instruction from the Instruction Memory
 - ➔ **Reg/Dec:** Registers Fetch and Instruction Decode
 - ➔ **Exec:** Calculate the memory address
 - ➔ **Mem:** Read the data from the Data Memory
 - ➔ **Wr:** Write the data back to the register file

Instruction Pipelining

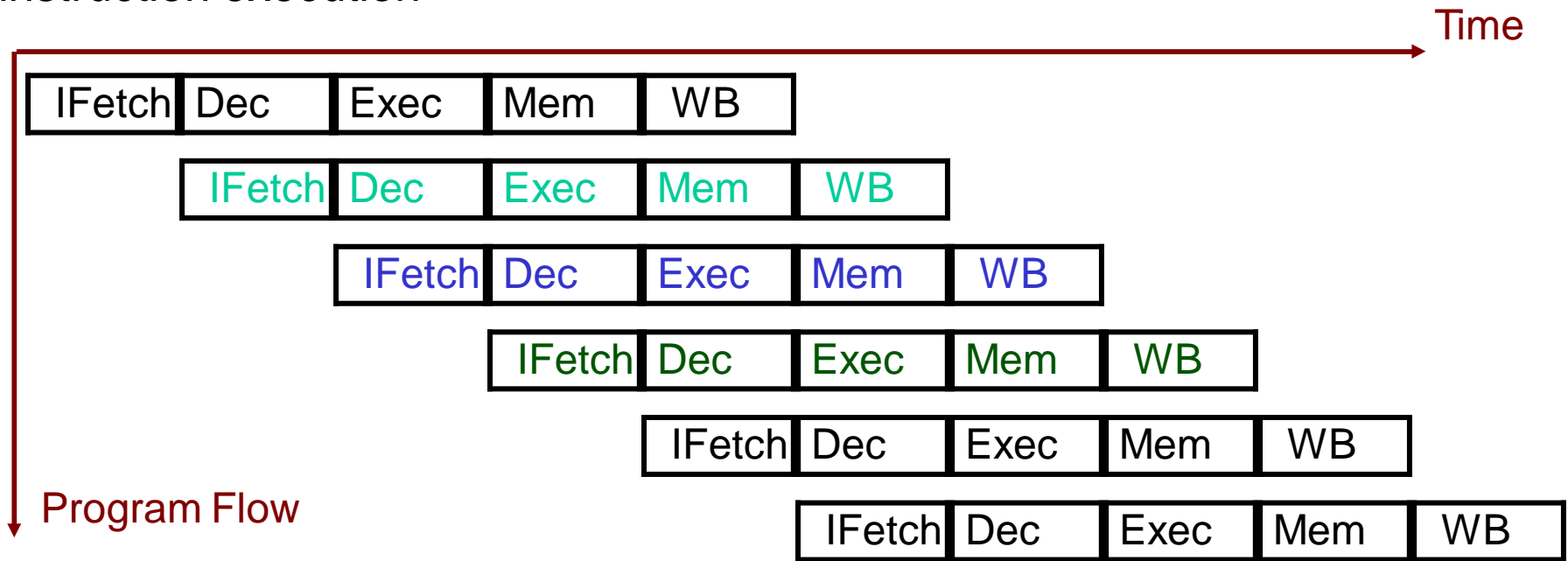- ❑ Start handling of next instruction while the current instruction is in progress
- ❑ Pipelining is feasible when different devices are used at different stages of instruction execution




$$\text{Time between instructions}_{\text{pipelined}} = \frac{\text{Time between instructions}_{\text{nonpipelined}}}{\text{Number of pipe stages}}$$

Pipelining improves performance by increasing instruction throughput



Pipelined Datapath

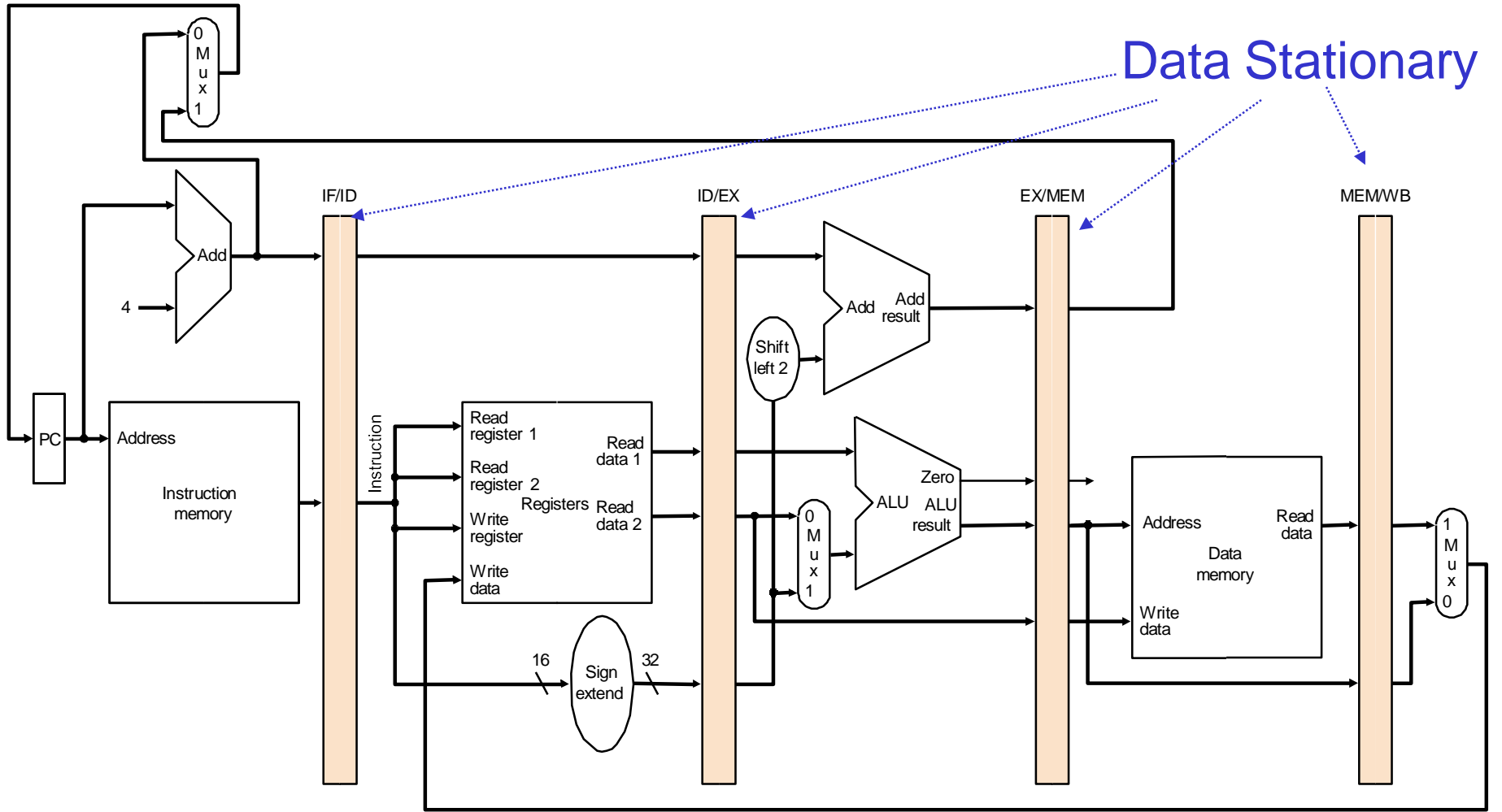

1

2


3

4

5




Datapath for Pipelined Processor


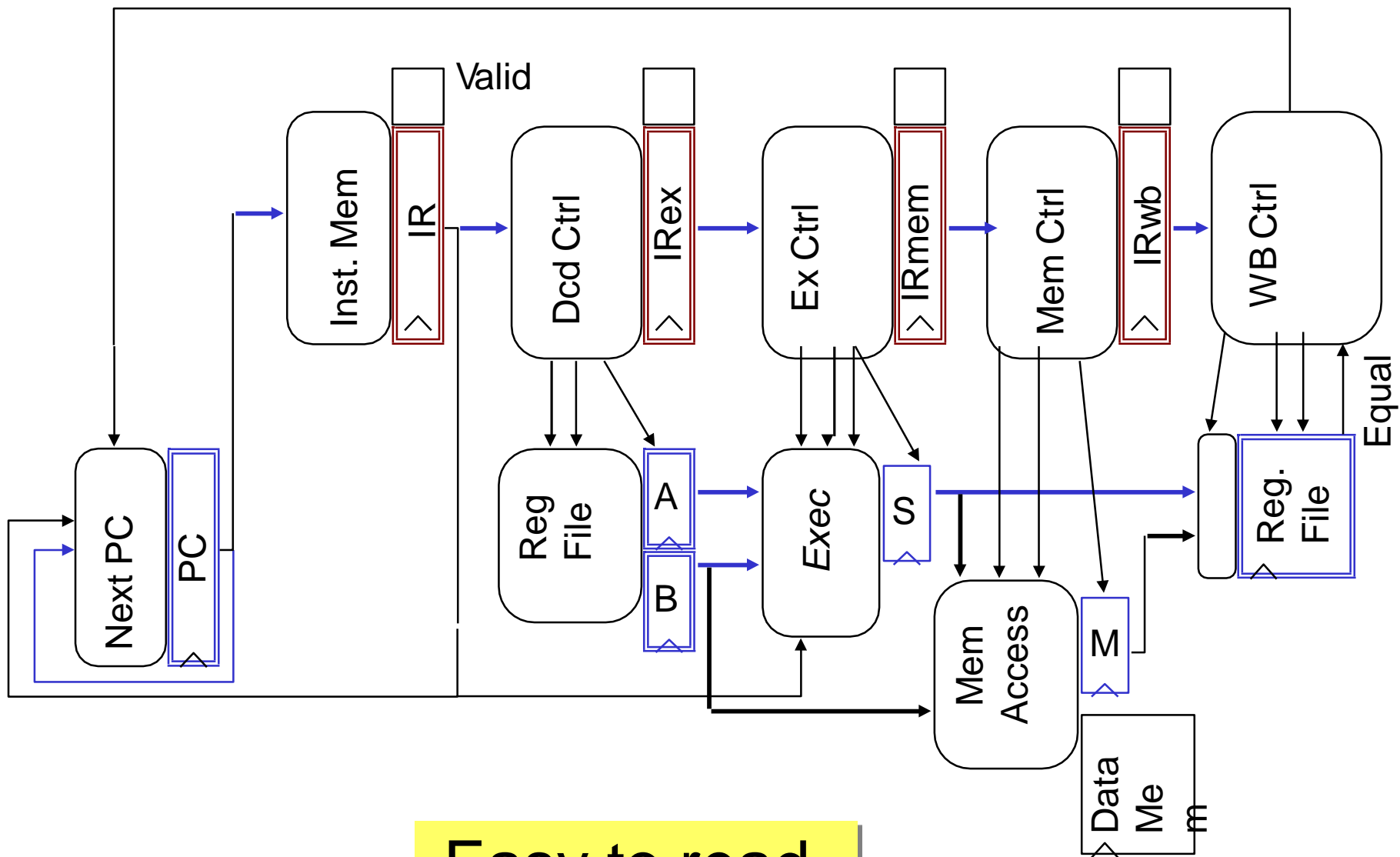


Easy to read


Control and Datapath

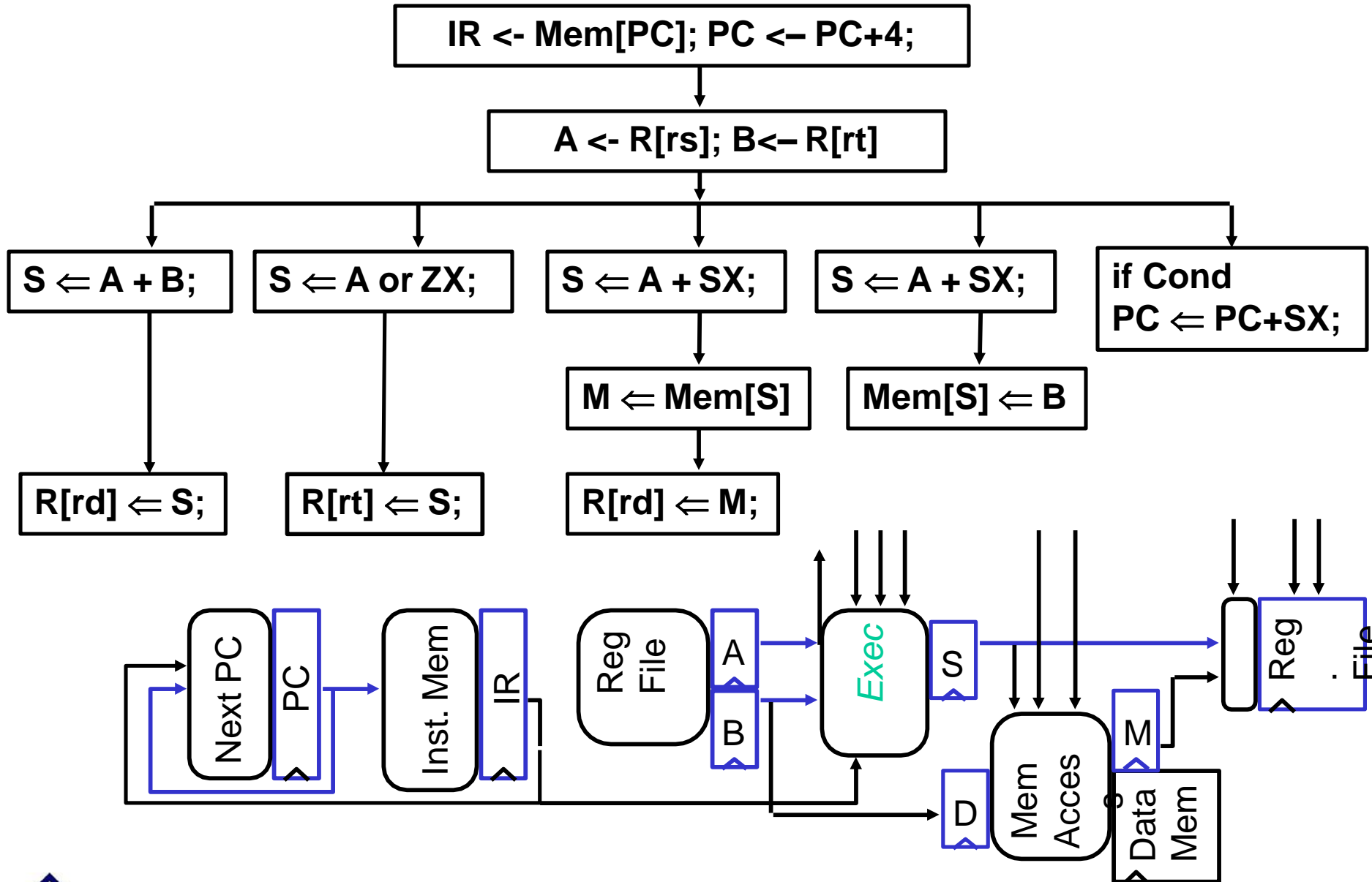

Pipelining the same Instruction

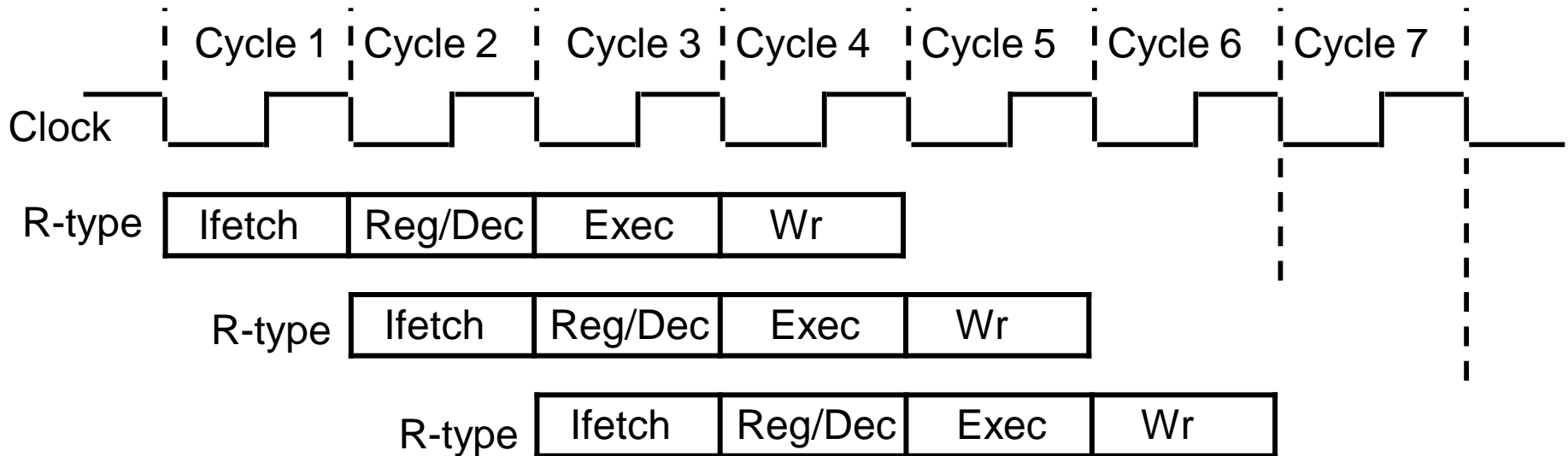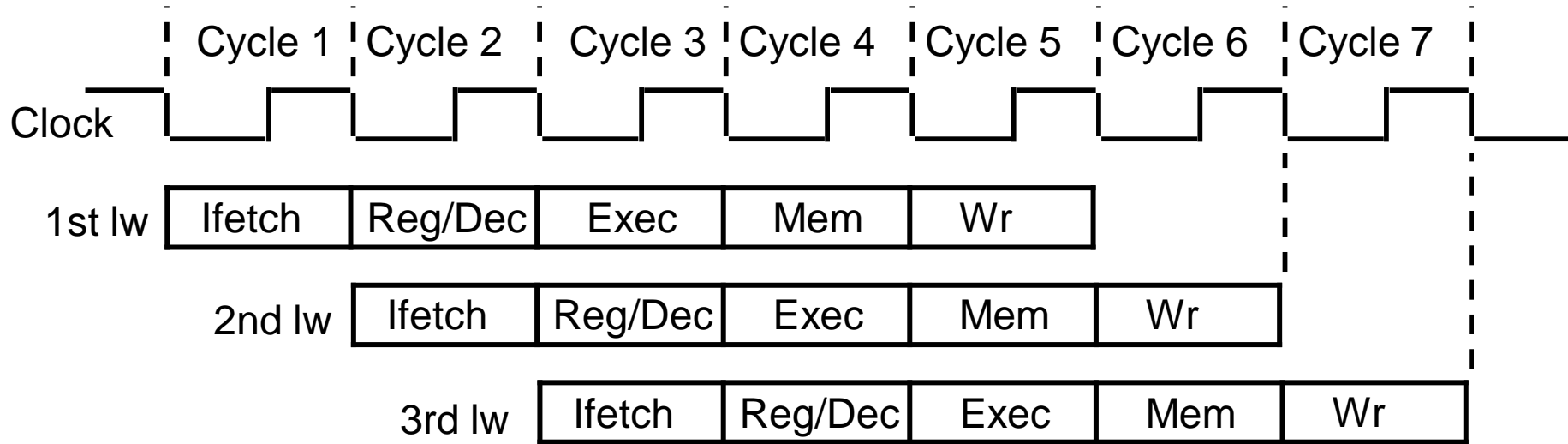

Pipelining R-type & Load Instructions

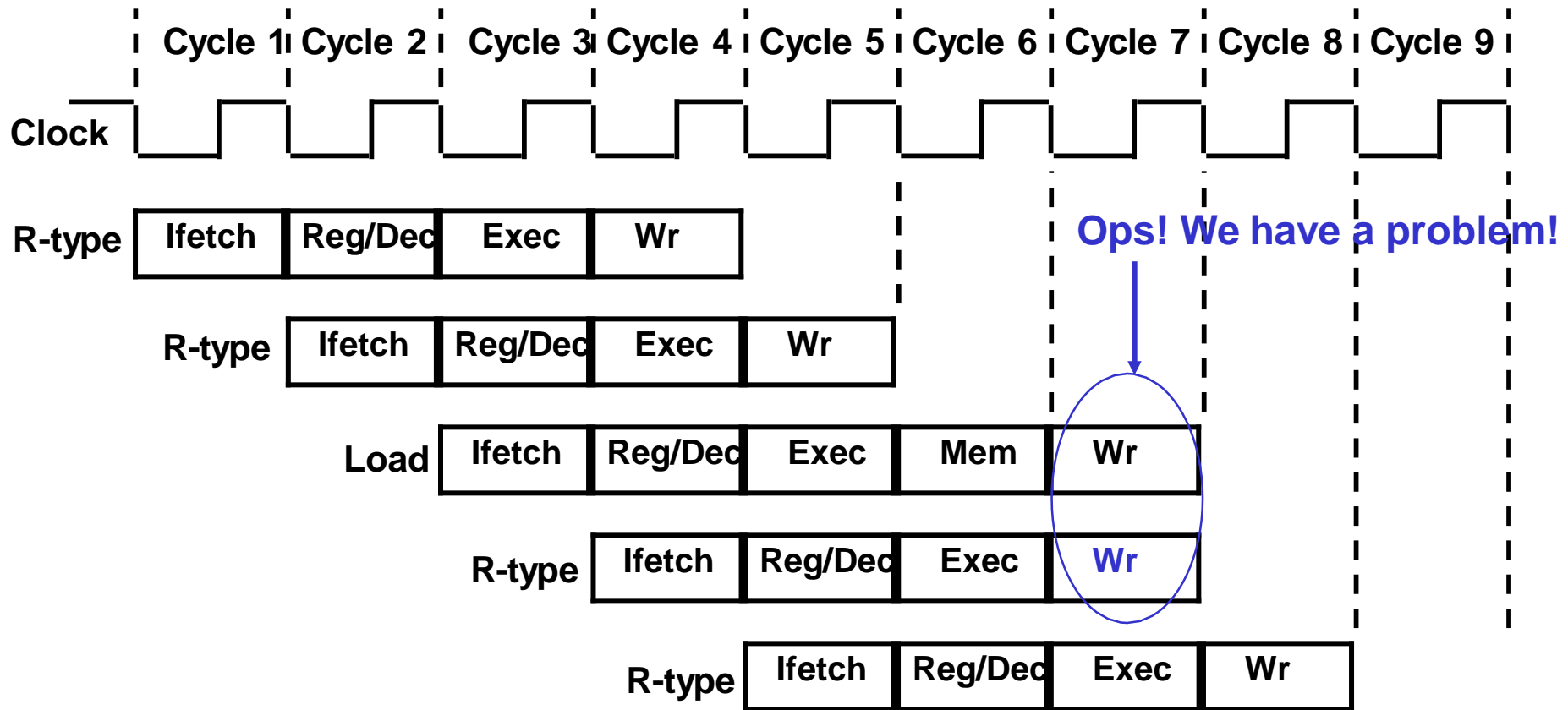


We have pipeline conflict or structural hazard:

- Two instructions try to write to register file at the same time!
- Only one write port



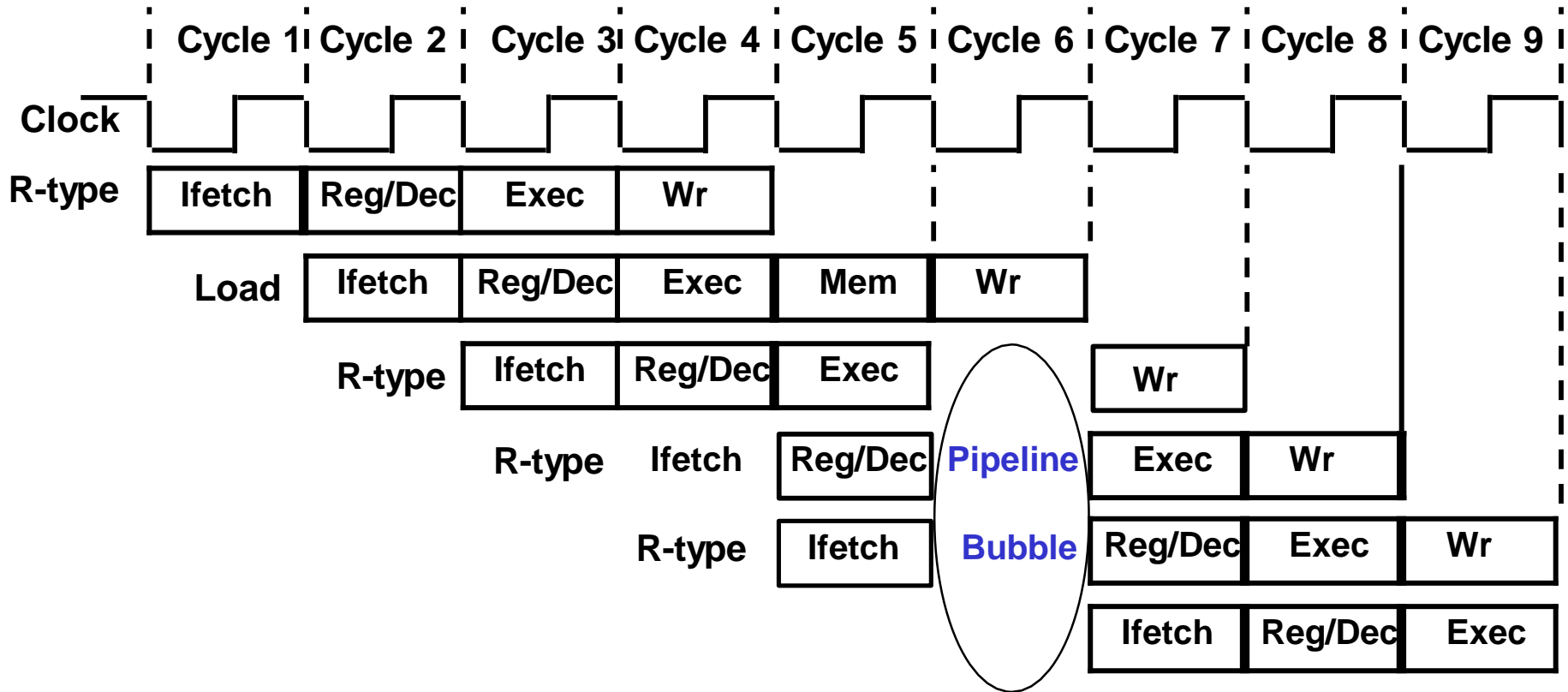Solution 1: Insert “Bubble” into Pipeline





- ❑ Insert a “bubble” into pipeline to prevent 2 writes at same cycle
 - ➔ The control logic can be complex.
 - ➔ Lost instruction fetch and speedup opportunity
- ❑ No instruction is started in Cycle 6!



Solution 2: Delay Write by One Cycle



Delay R-type's register write by one cycle:

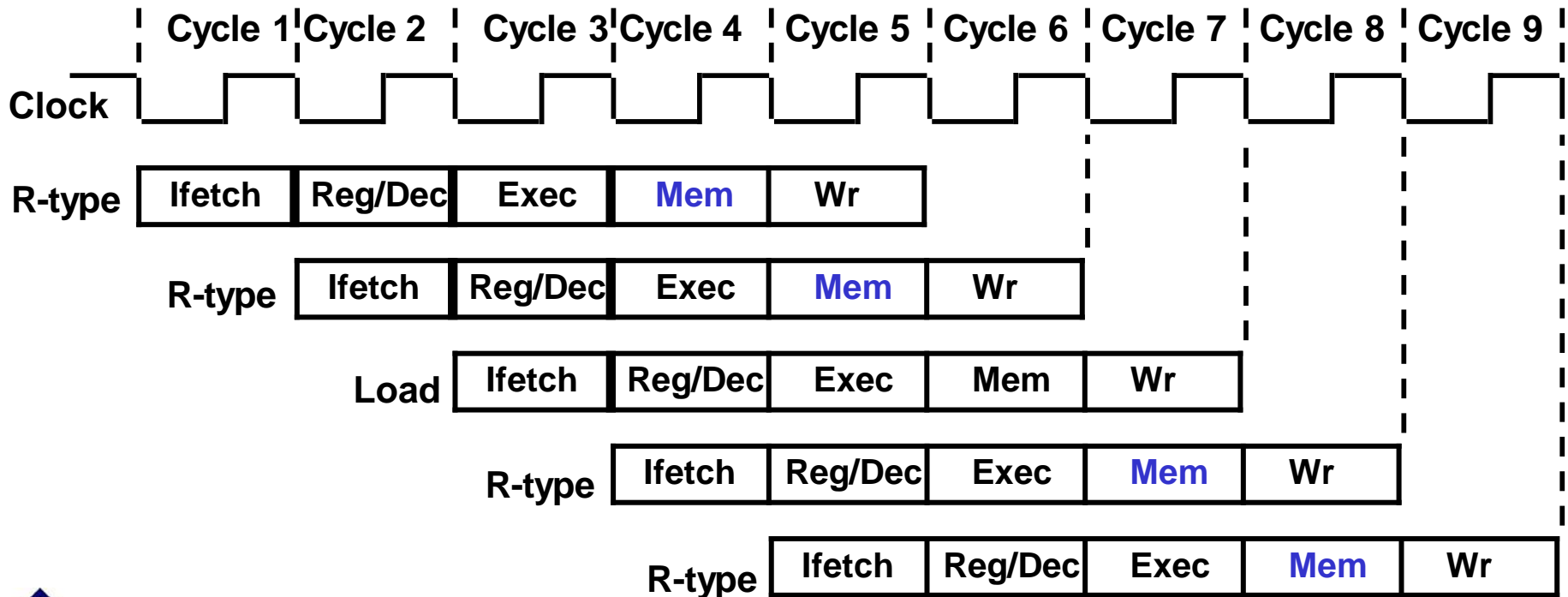 - Now R-type instructions also use Reg File's write port at Stage 5
- Mem stage is a **NOOP** stage: nothing is being done.




* Slide is courtesy of Dave Patterson

Modified Control & Datapath

 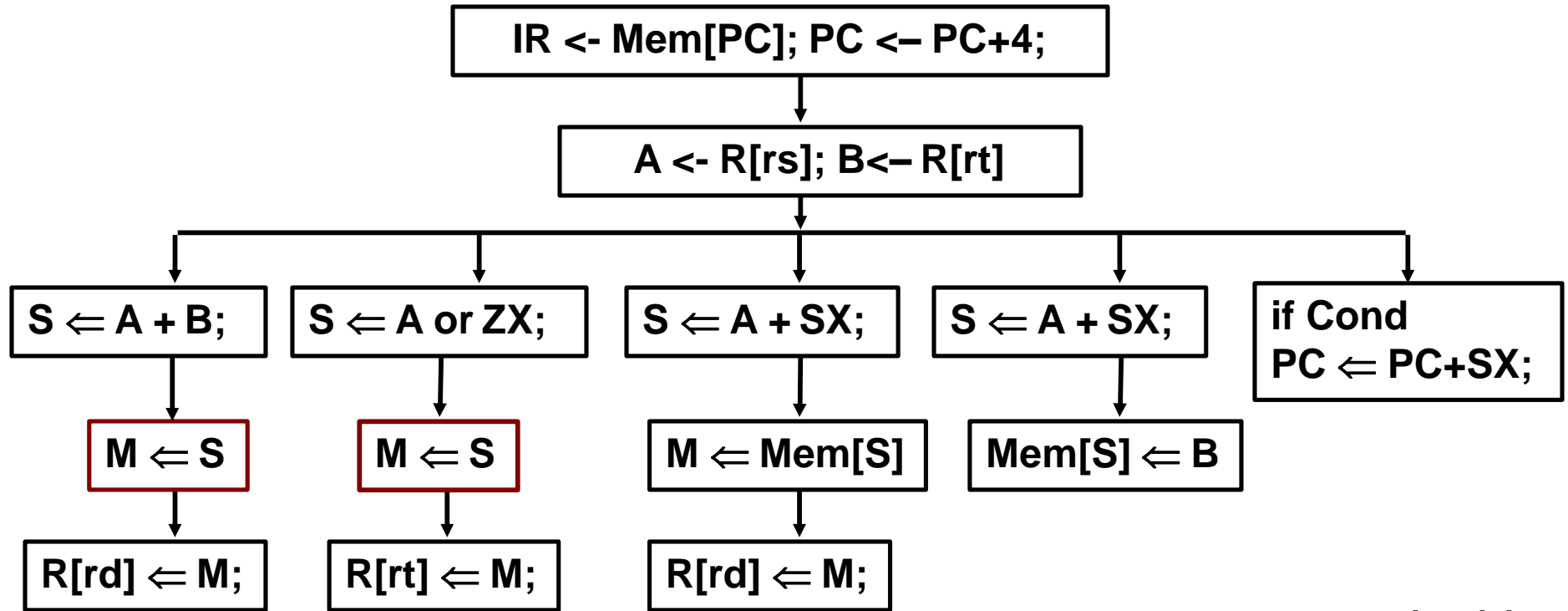


Standardized Five Stages Instructions

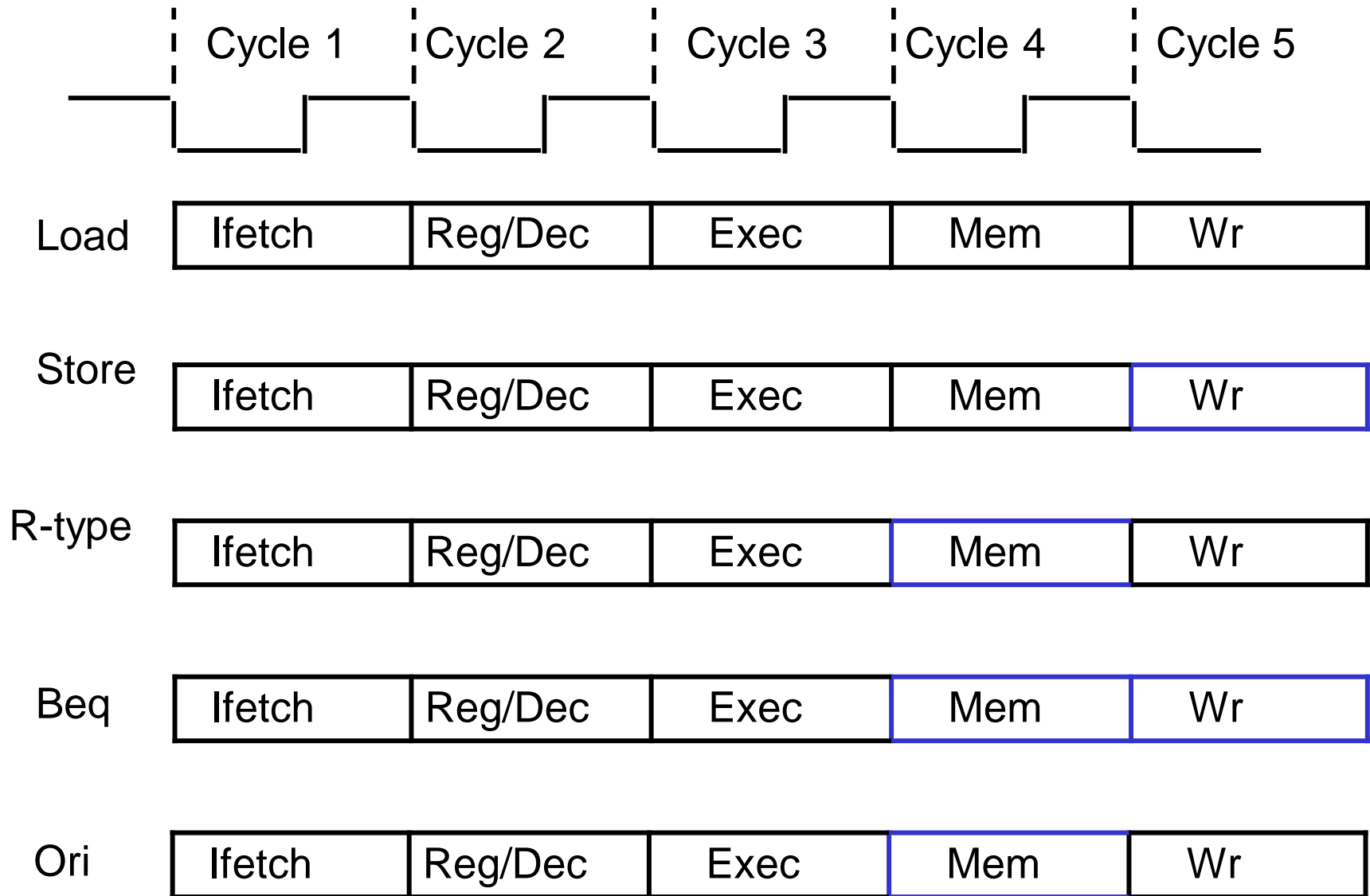


Data Stationary Control

The Main Control generates the control signals during Reg/Dec

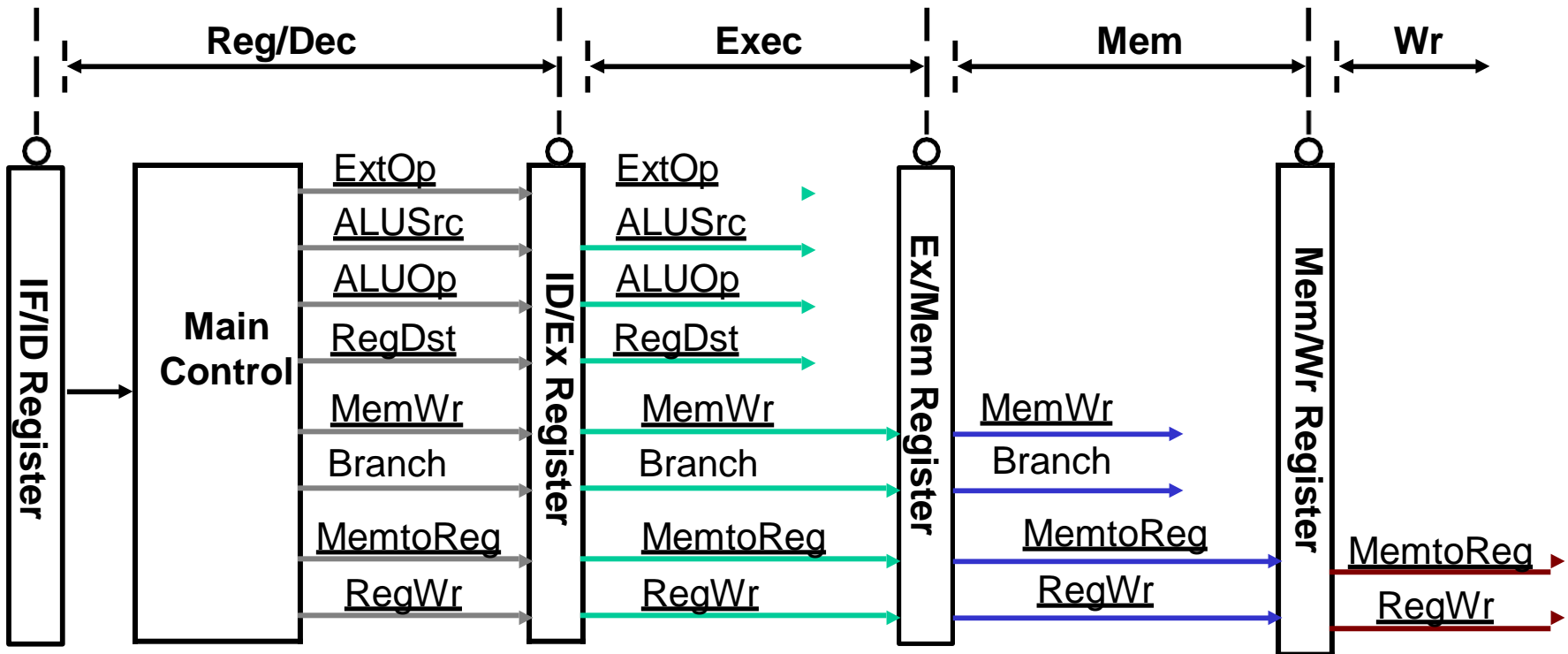
- ➔ Control signals for Exec (ExtOp, ALUSrc, ...) are used 1 cycle later
- ➔ Control signals for Mem (MemWr Branch) are used 2 cycles later
- ➔ Control signals for Wr (MemtoReg MemWr) are used 3 cycles later



Datapath + Data Stationary Control

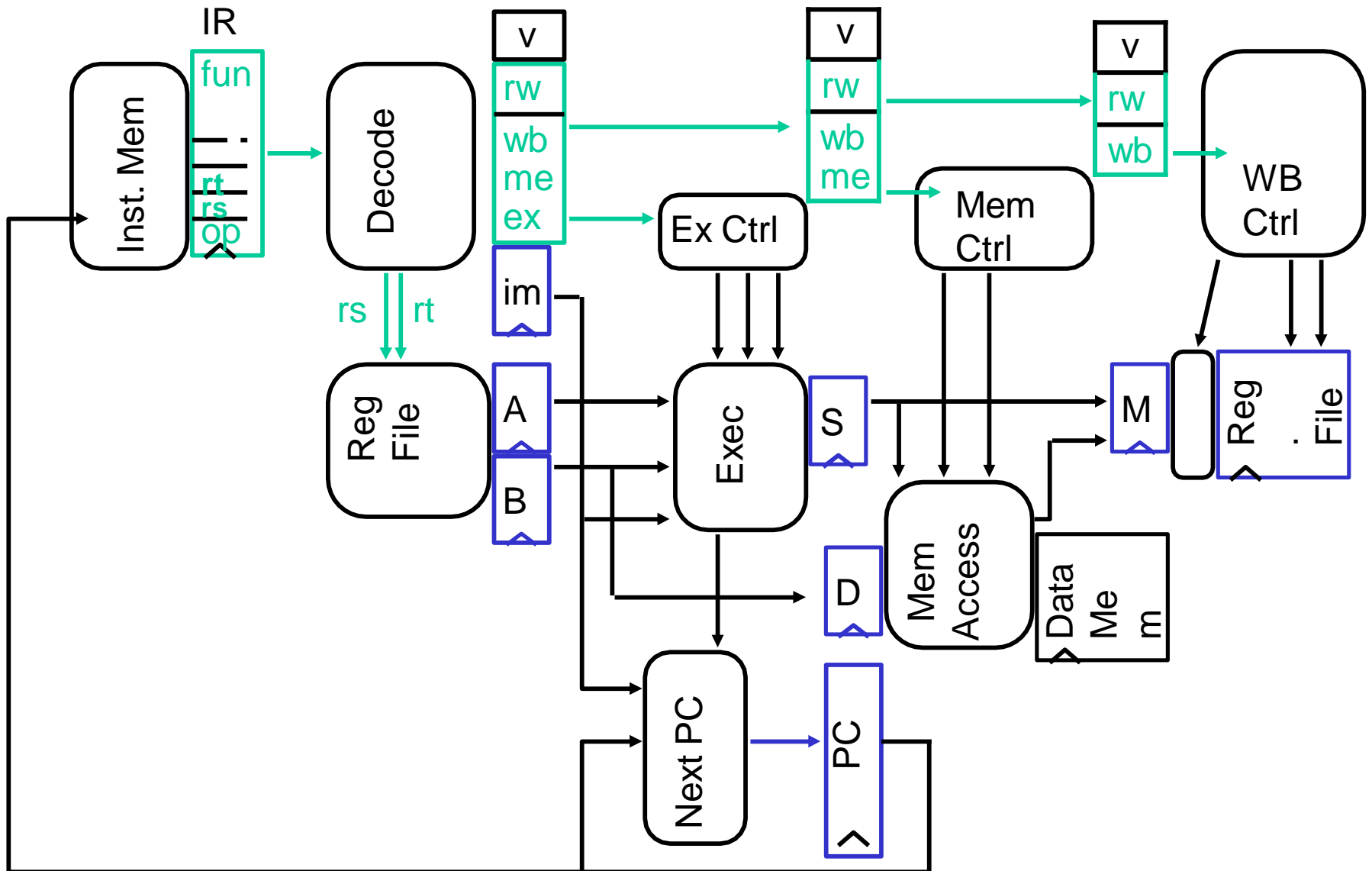

An example

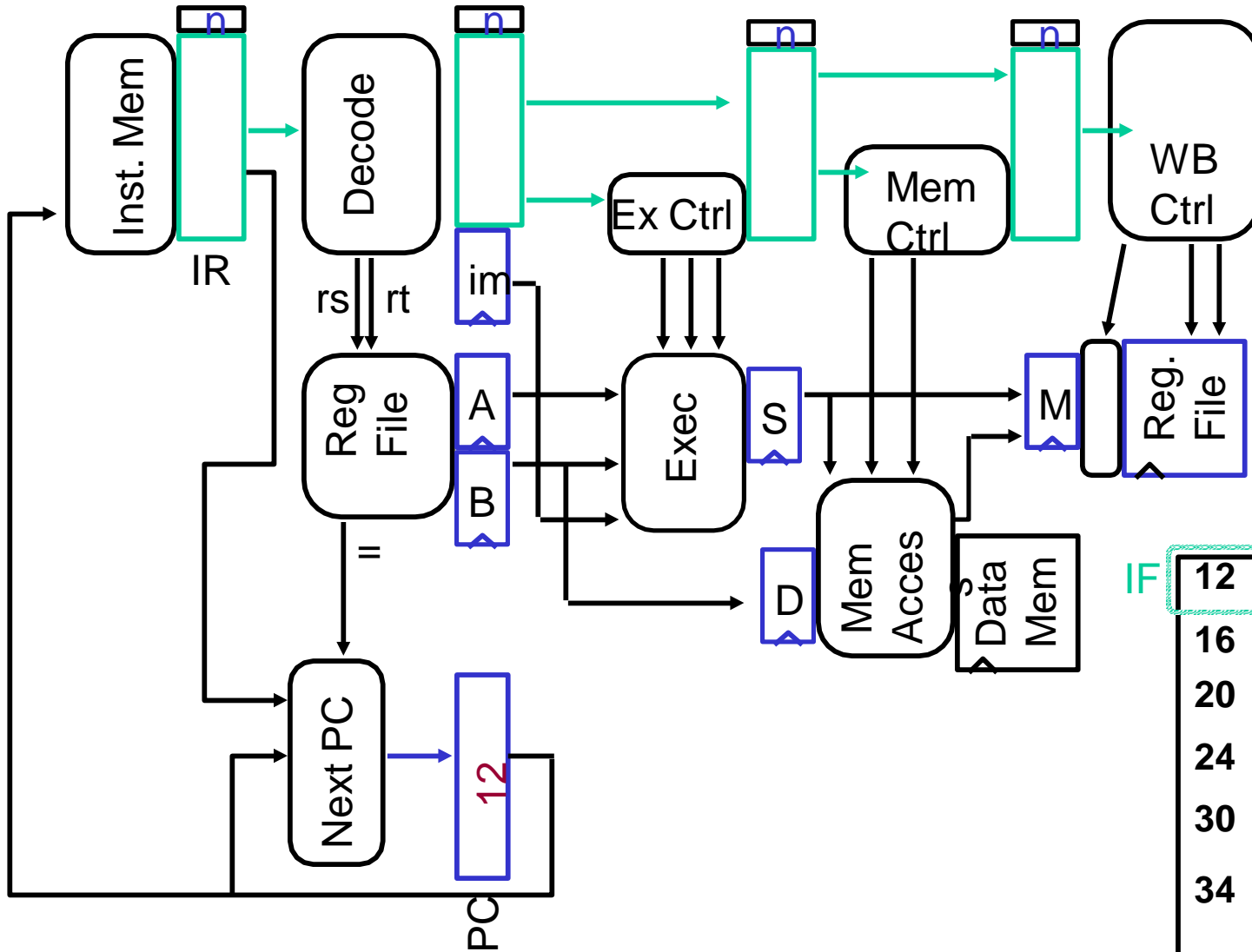


```

IF 12 lw r1, r2(35)
16 addl r2, r2, 3
20 sub r3, r4, r5
24 beq r6, r7, 100
30 ori r8, r9, 17
34 add r10, r11, r12
128 and r13, r14, 15
    
```

Start: **Fetch 12**




An example

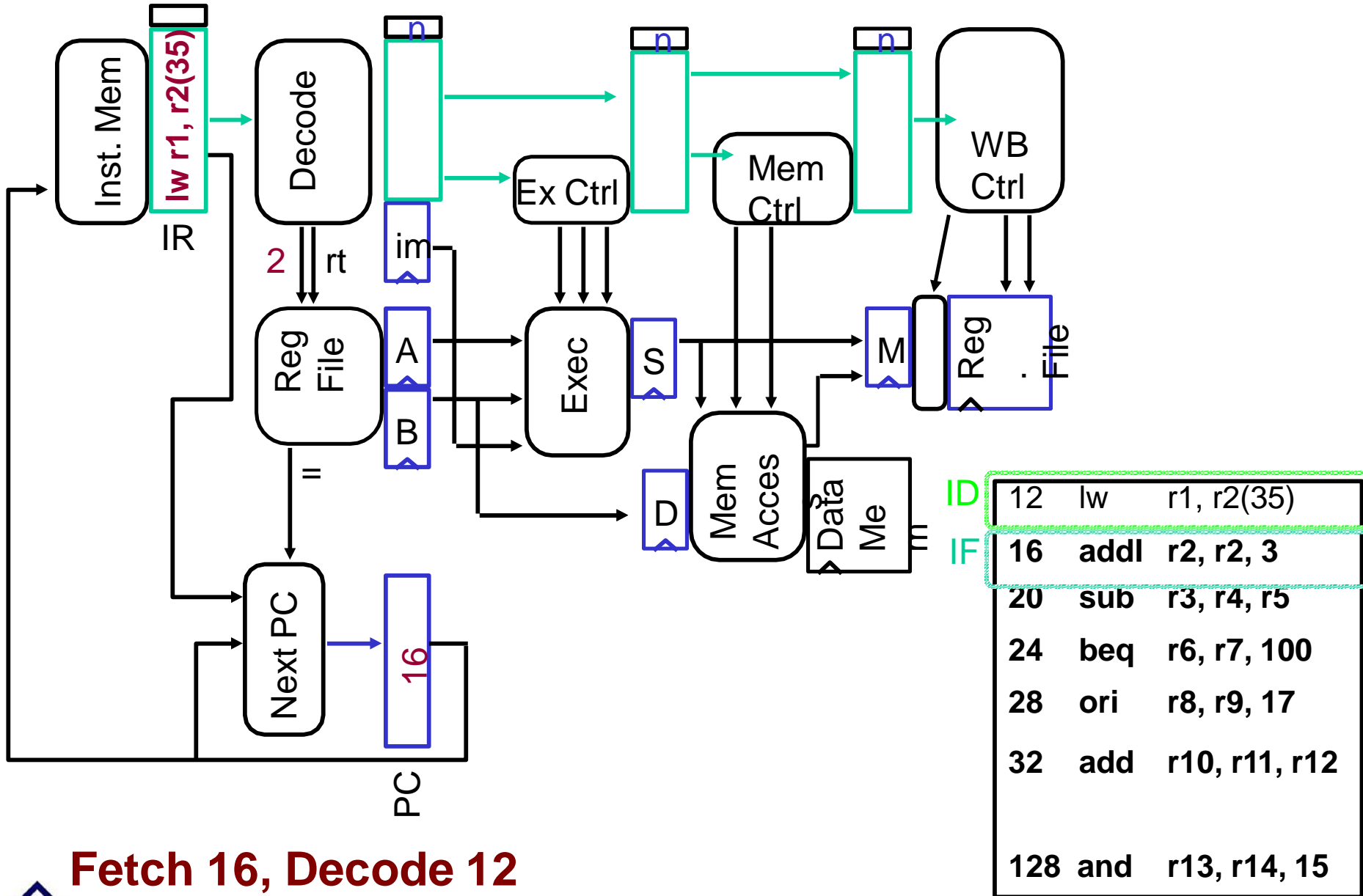

Fetch 16, Decode 12




An example

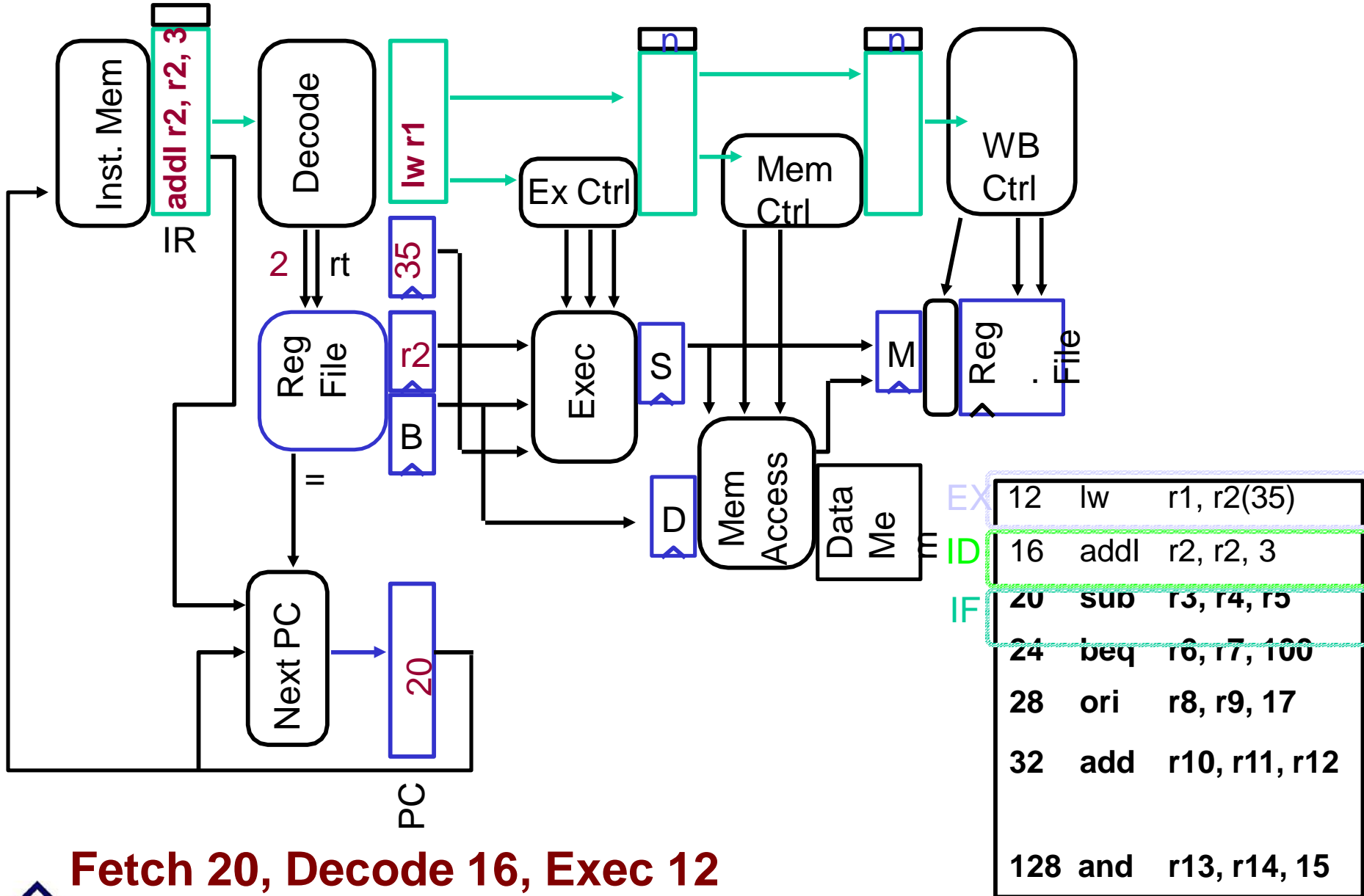

Fetch 20, Decode 16, Exec 12



An example

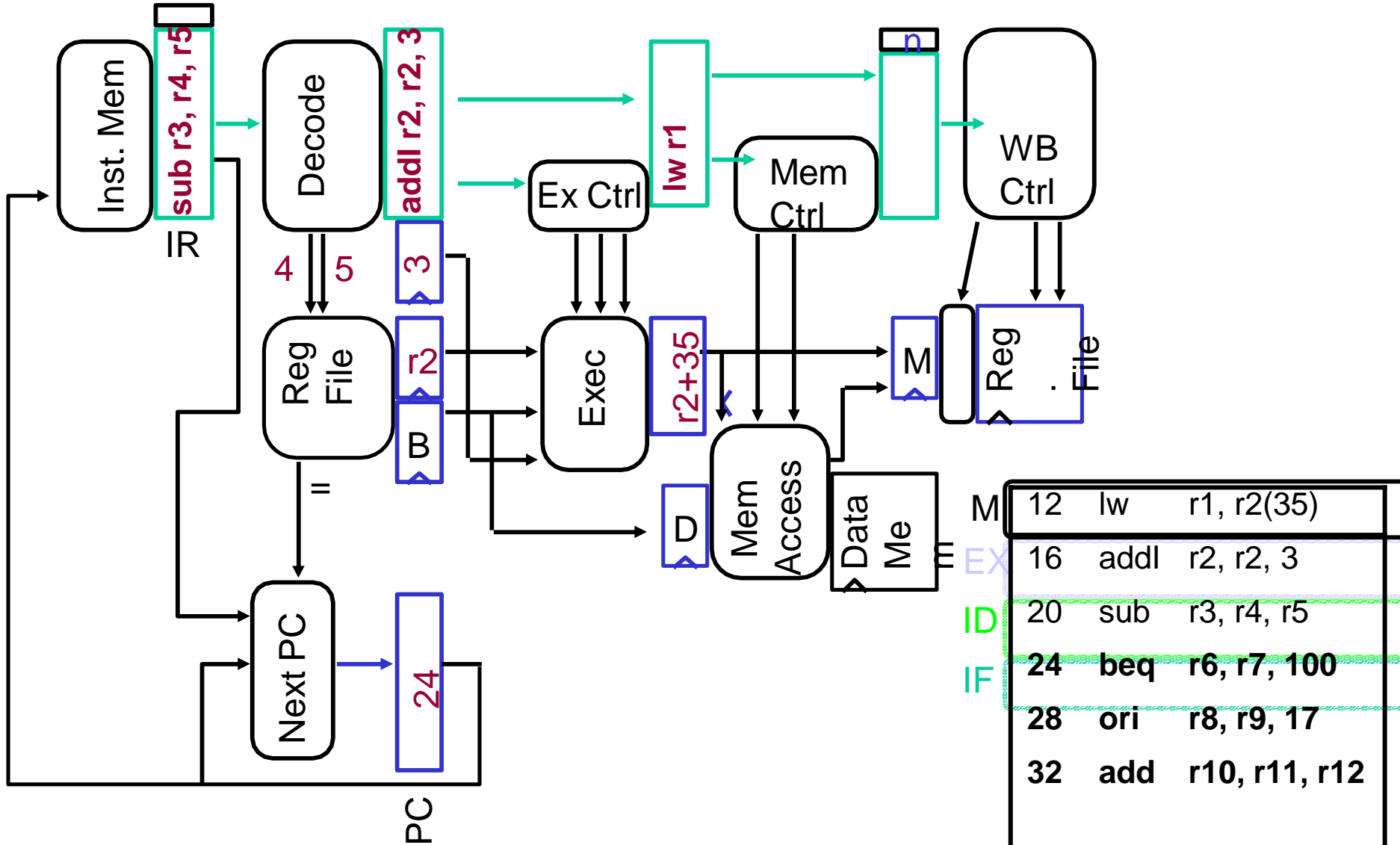


Fetch 24, Decode 20, Exec 16, Mem 12

M	12	lw	r1, r2(35)
EX	16	addl	r2, r2, 3
ID	20	sub	r3, r4, r5
IF	24	beq	r6, r7, 100
	28	ori	r8, r9, 17
	32	add	r10, r11, r12
	128	and	r13, r14, 15




An example

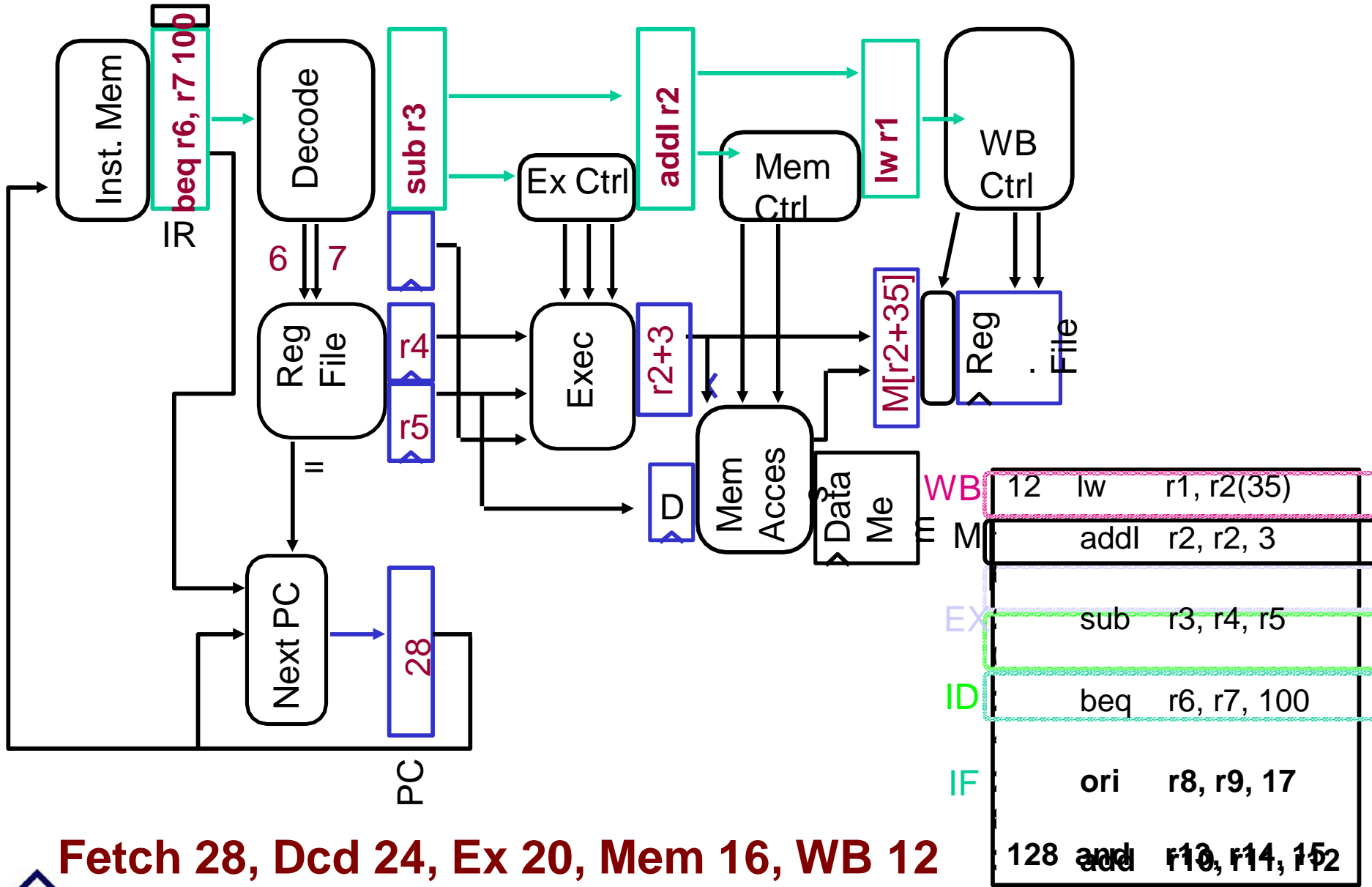

Fetch 28, Dcd 24, Ex 20, Mem 16, WB 12




An example

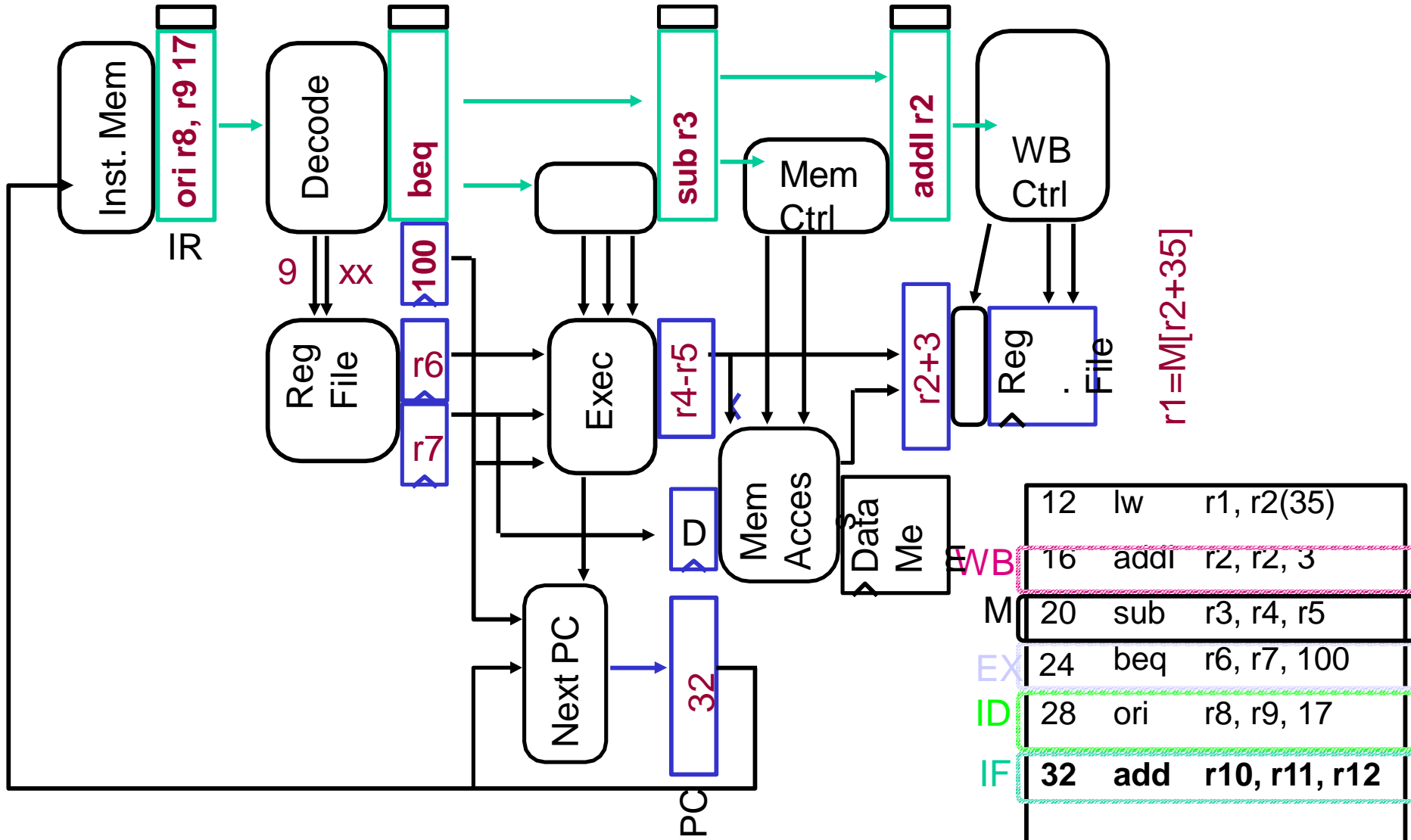

Fetch 32, Dcd 28, Ex 24, Mem 20, WB 16




An example

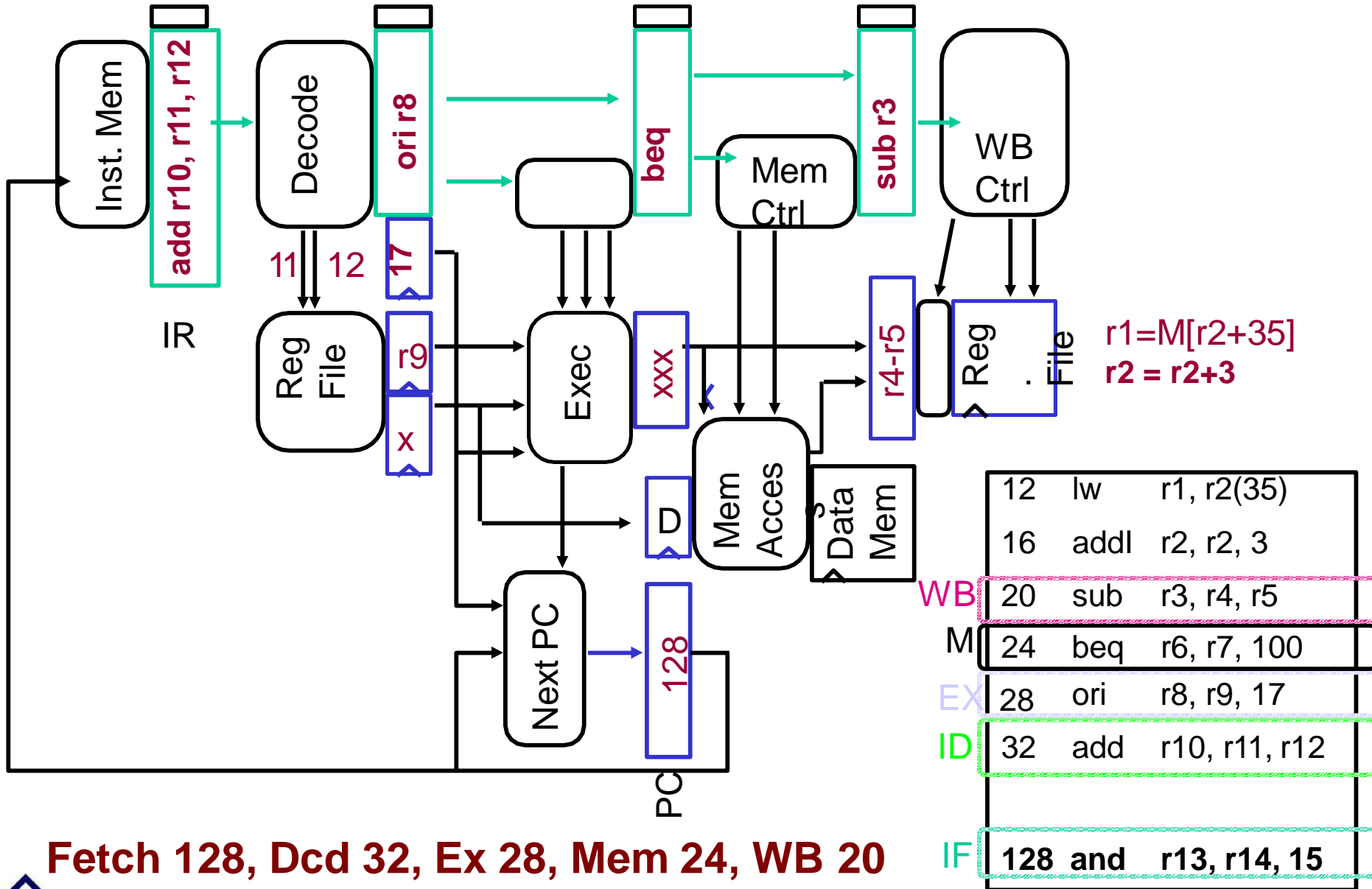

Fetch 128, Dcd 32, Ex 28, Mem 24, WB 20




An example

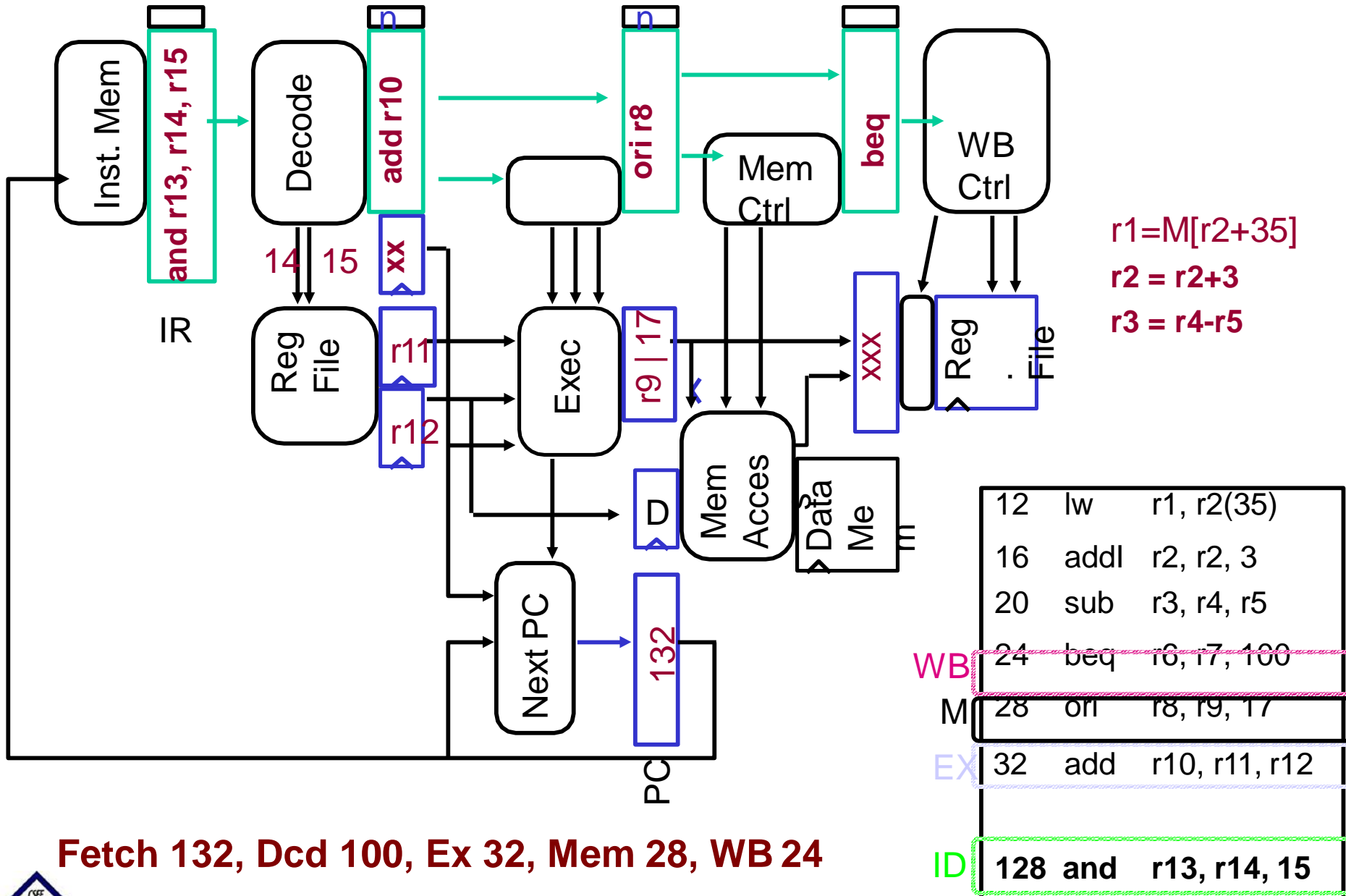


Fetch 132, Dcd 100, Ex 32, Mem 28, WB 24



An example

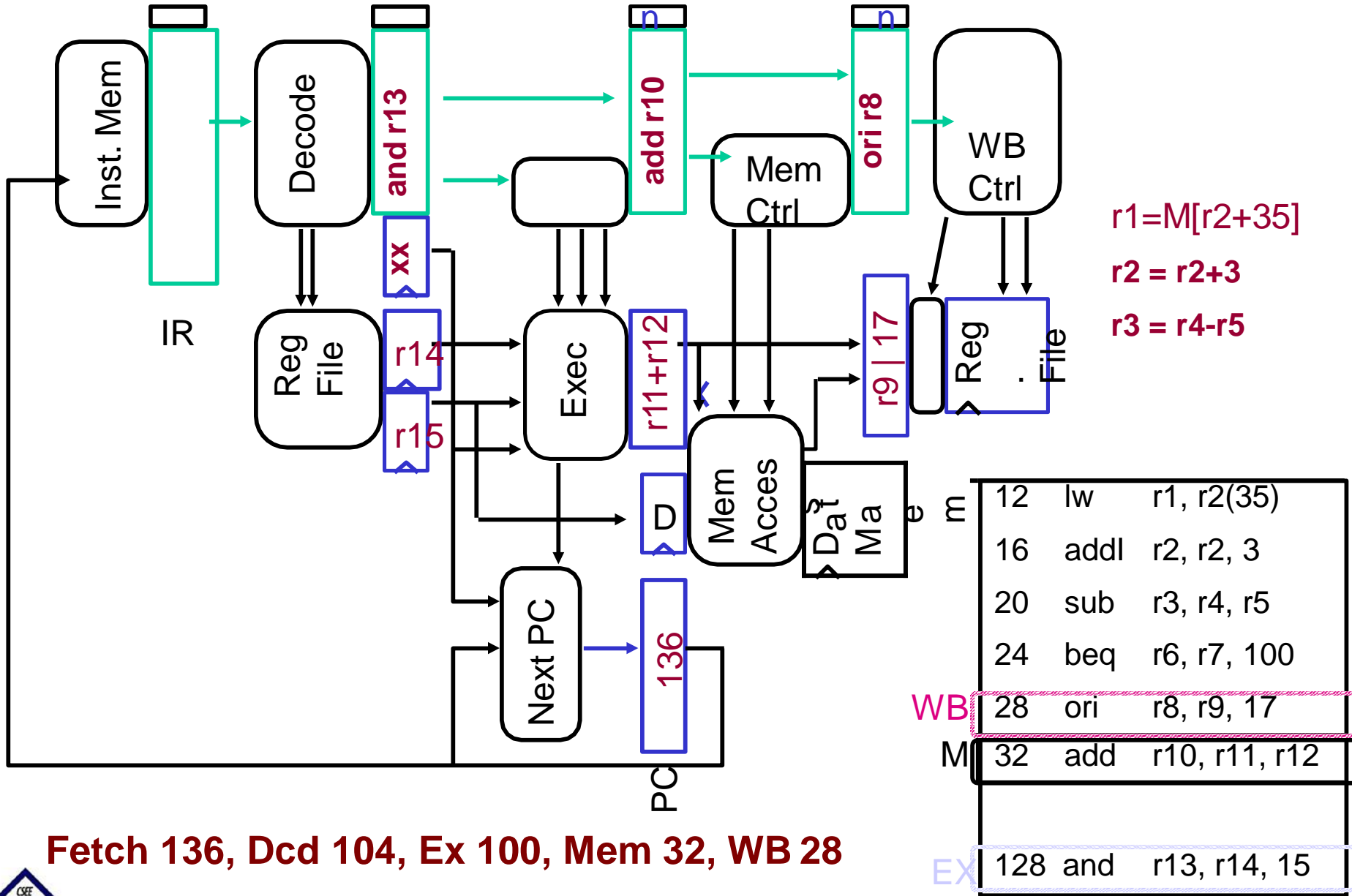

An example

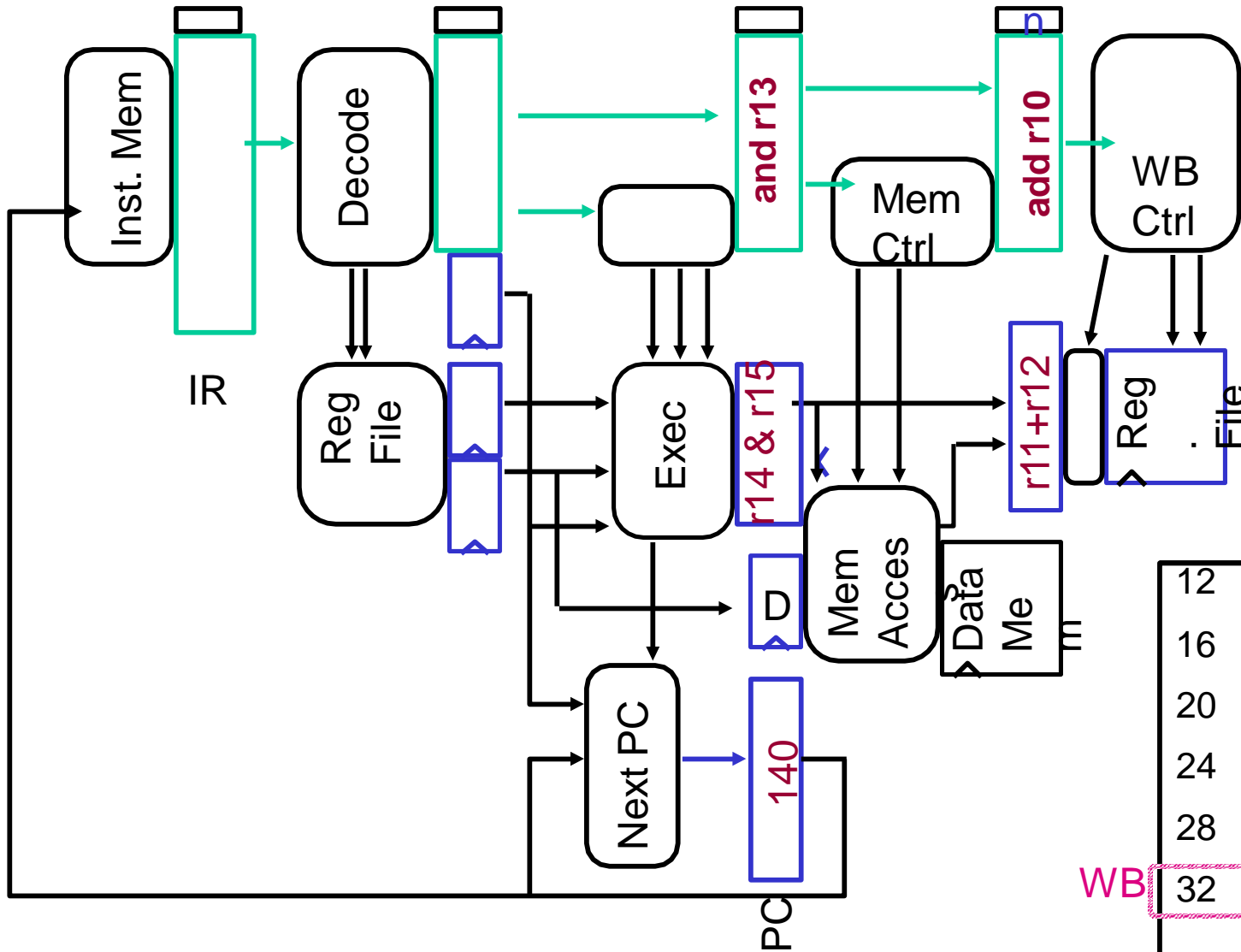

$r1 = M[r2 + 35]$
 $r2 = r2 + 3$
 $r3 = r4 - r5$

12	lw	r1, r2(35)
16	addi	r2, r2, 3
20	sub	r3, r4, r5
24	beq	r6, r7, 100
28	ori	r8, r9, 17
32	add	r10, r11, r12
36	and	r13, r14, 15

Fetch 140, Dcd 108, Ex 104, Mem 100, WB 32



Conclusion

□ Summary

- Designing a pipelined datapath
 - Standardized multi-stage instruction execution
 - Unique resources per stage
- Pipeline control
 - Simplified stage-based control
 - Detailed working example

□ Next Lecture

- Pipeline hazard detection
- Handling hazard in the pipeline design

Read sections 4.6 in the 5th Ed. or section 4.6 in the 4th Ed. of the textbook

