

8086 - 80386SX 16-bit Memory Interface


These machines differ from the 8088/80188 in several ways:

- The data bus is *16-bits* wide.
- The $\overline{\text{IO}/\overline{\text{M}}}$ pin is replaced with $\overline{\text{M}/\overline{\text{IO}}}$ (8086/80186) and $\overline{\text{MRDC}}$ and $\overline{\text{MWTC}}$ for 80286 and 80386SX.
- $\overline{\text{BHE}}$, *Bus High Enable*, control signal is added.
- Address pin A_0 (or $\overline{\text{BLE}}$, *Bus Low Enable*) is used differently.

The 16-bit data bus presents a new problem:

The microprocessor must be able to read and write data to any 16-bit location in addition to any 8-bit location.

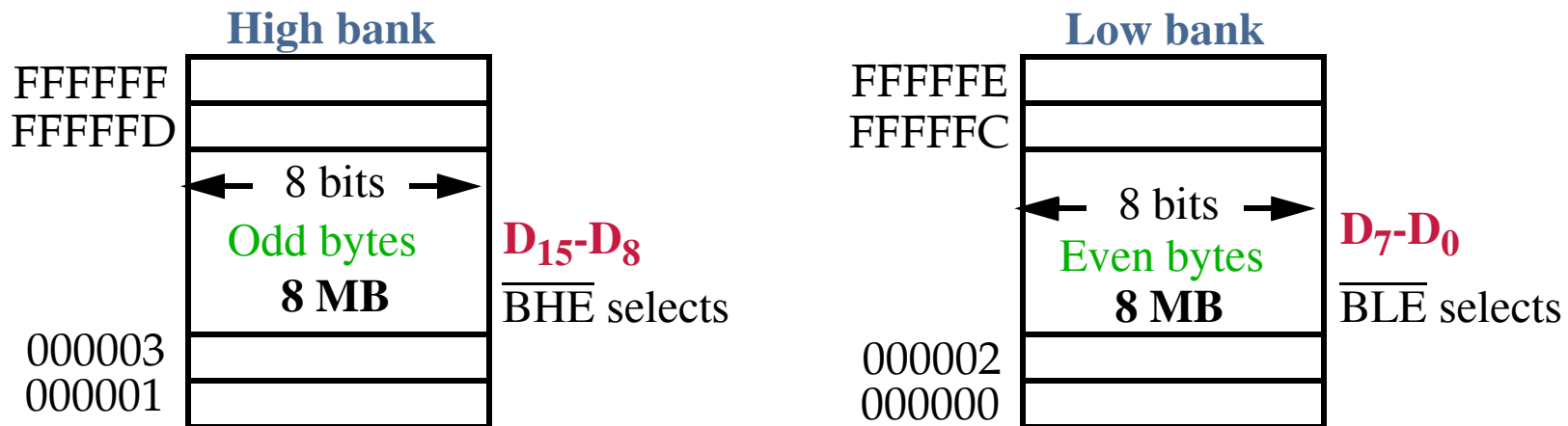The data bus and memory are divided into banks:



8086 - 80386SX 16-bit Memory Interface

BHE and BLE are used to select one or both:

\overline{BHE}	\overline{BLE}	Function
0	0	Both banks enabled for 16-bit transfer
0	1	High bank enabled for an 8-bit transfer
1	0	Low bank enabled for an 8-bit transfer
1	1	No banks selected

Bank selection can be accomplished in two ways:


- Separate write decoders for each bank (which drive \overline{CS}).
- A separate write signal (strobe) to each bank (which drive \overline{WE}).

Note that 8-bit read requests in this scheme are handled by the microprocessor (it selects the bits it wants to read from the 16-bits on the bus).

There does not seem to be a big difference between these methods although the book claims that there is.

Note in either method that A_0 does not connect to memory and bus wire A_1 connects to memory pin A_0 , A_2 to A_1 , etc.

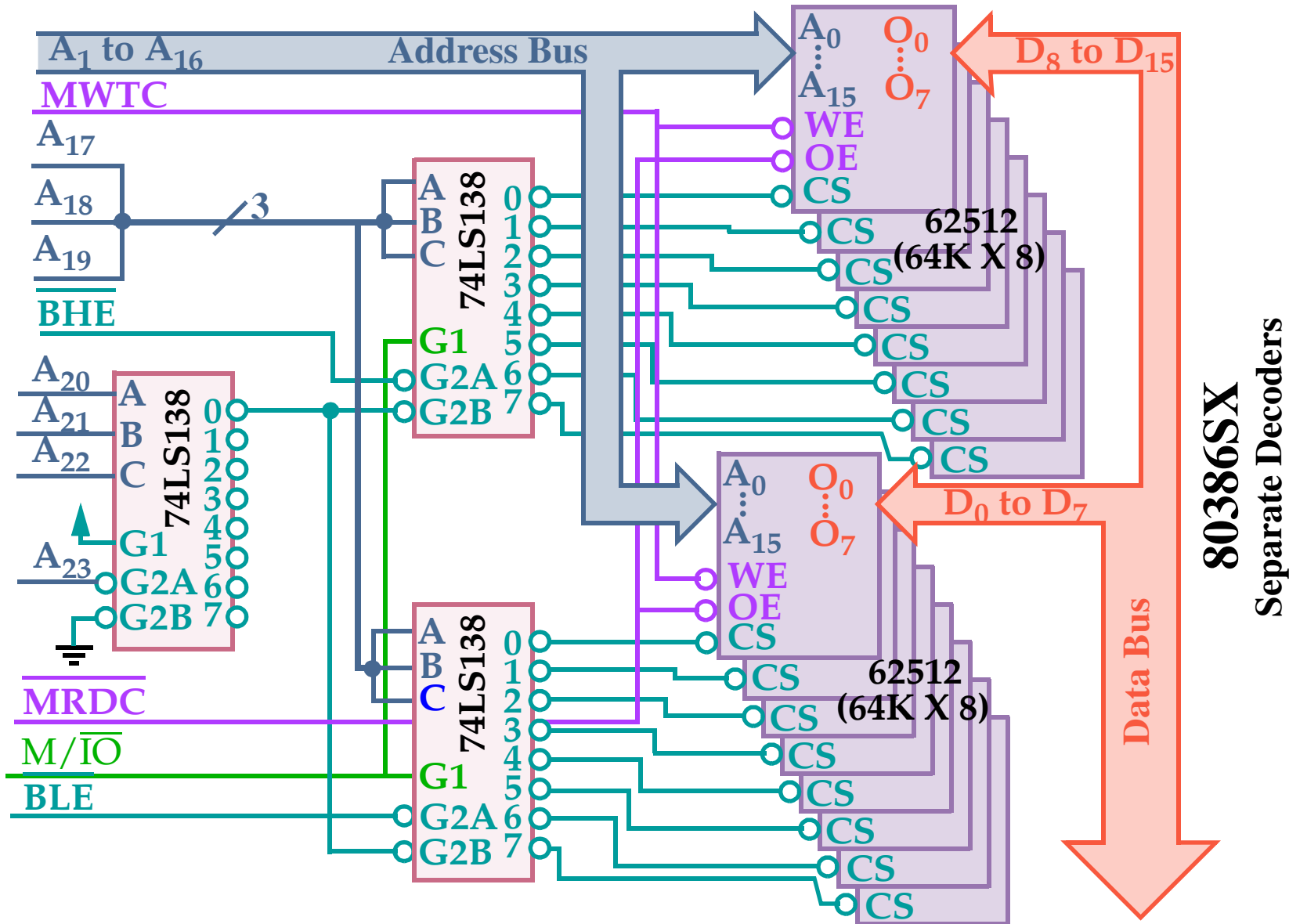80386SX 16-bit Memory Interface (Separate Decoders)



Memory Interfaces

See text for *Separate Write Strobe* scheme plus some examples of the integration of EPROM and SRAM in a complete system.

It is just an application of what we've been covering.

80386DX and 80486 have *32-bit* data buses and therefore 4 banks of memory.

32-bit, *16-bit* and *8-bit* transfers are accomplished by different combinations of the bank selection signals $\overline{BE3}$, $\overline{BE2}$, $\overline{BE1}$, $\overline{BE0}$.

The Address bits A_0 and A_1 are used within the microprocessor to generate these signals.

They are *don't cares* in the decoding of the 32-bit address outside the chip (using a PLD such as the **PAL 16L8**).

The high clock rates of these processors usually require *wait states* for memory access. We will come back to this later.


Pentium Memory Interface

The Pentium, Pentium Pro, Pentium II and III contain a 64-bit data bus.


Therefore, 8 decoders or 8 write strobes are needed as well as 8 memory banks.

The write strobes are obtained by combining the bank enable signals ($\overline{\text{BE}}_x$) with the $\overline{\text{MWTC}}$ signal.

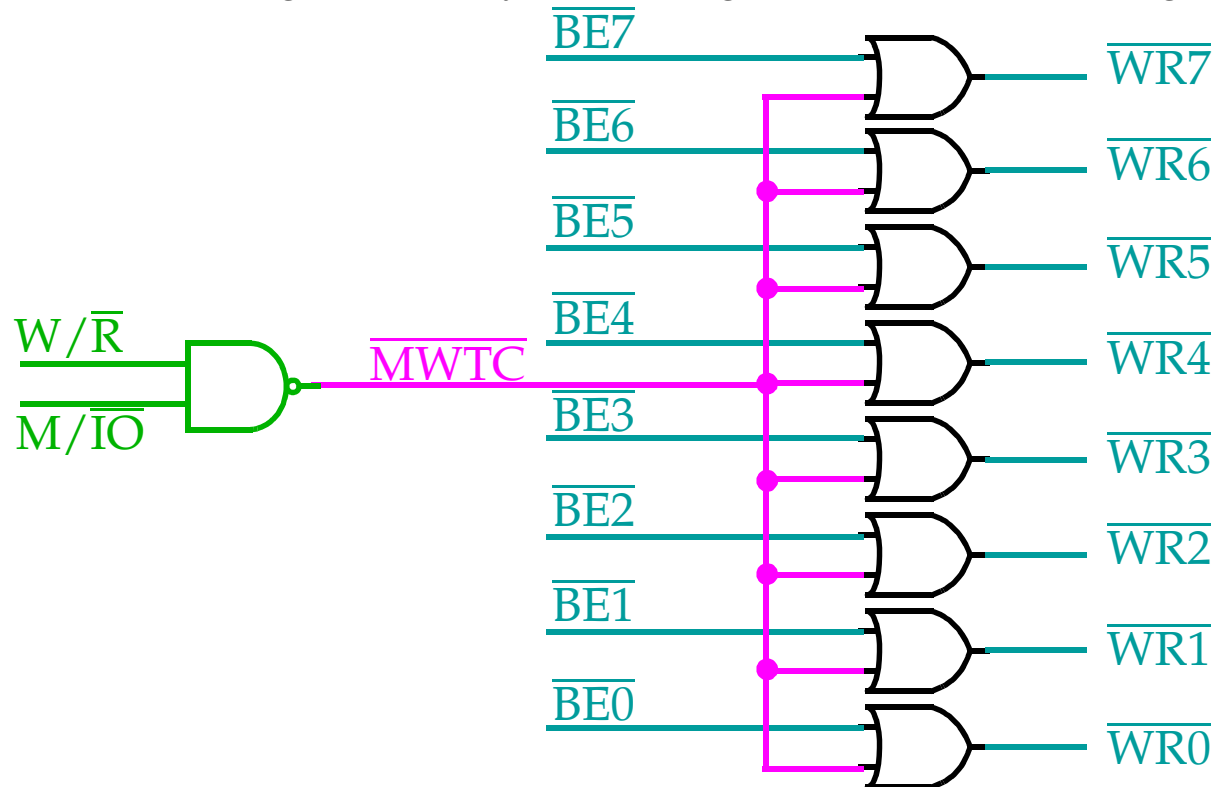$\overline{\text{MWTC}}$ is generated by combining the $\text{M}/\overline{\text{IO}}$ and $\text{W}/\overline{\text{R}}$ signals.




Pentium Memory Interface

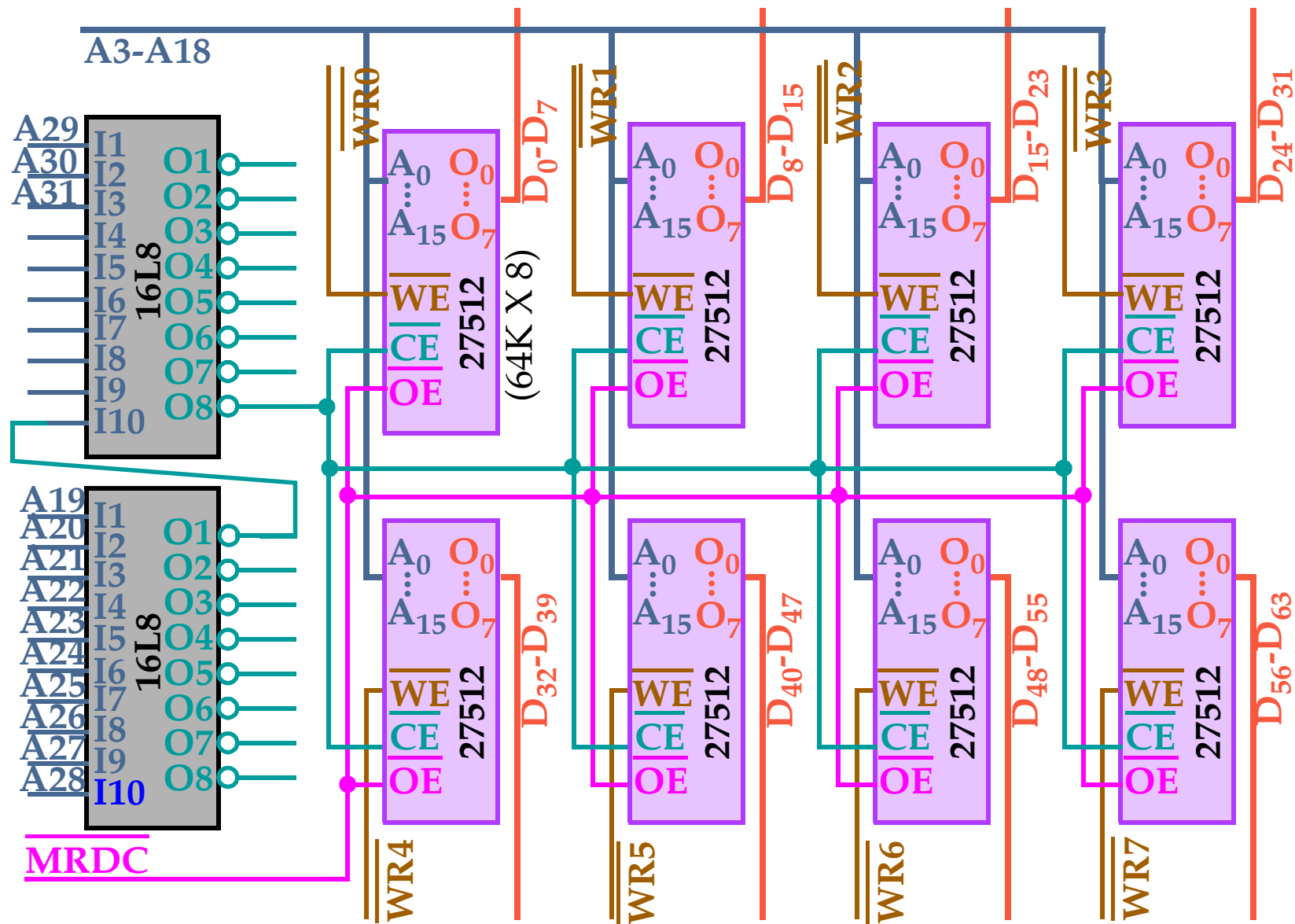

Pentium Memory Interface

 In order to map previous memory into addr. space $FFF80000H-FFFFFFFFH$




;pins 1 2 3 4 5 6 7 8 9 10
A29 A30 A31 NC NC NC NC NC NC GND

;pins 11 12 13 14 15 16 17 18 19 20
U2 CE NC NC NC NC NC NC NC VCC

Equations:
 
$$\overline{/CE} = \overline{/U2} * A29 * A30 * A31$$



;pins 1 2 3 4 5 6 7 8 9 10
A19 A20 A21 A22 A23 A24 A25 A26 A27 GND

;pins 11 12 13 14 15 16 17 18 19 20
A28 U2 NC NC NC NC NC NC NC VCC

Equations:


$$\overline{/U2} = A19 * A20 * A21 * A22 * A23 * A24 * A25 * A26 * A27 * A28$$

Use a **16L8** to do the $\overline{WR0} - \overline{WR7}$ decoding using \overline{MWTC} and $\overline{BE0} - \overline{BE7}$.

See the text -- Figure 10-35.

Memory Architecture

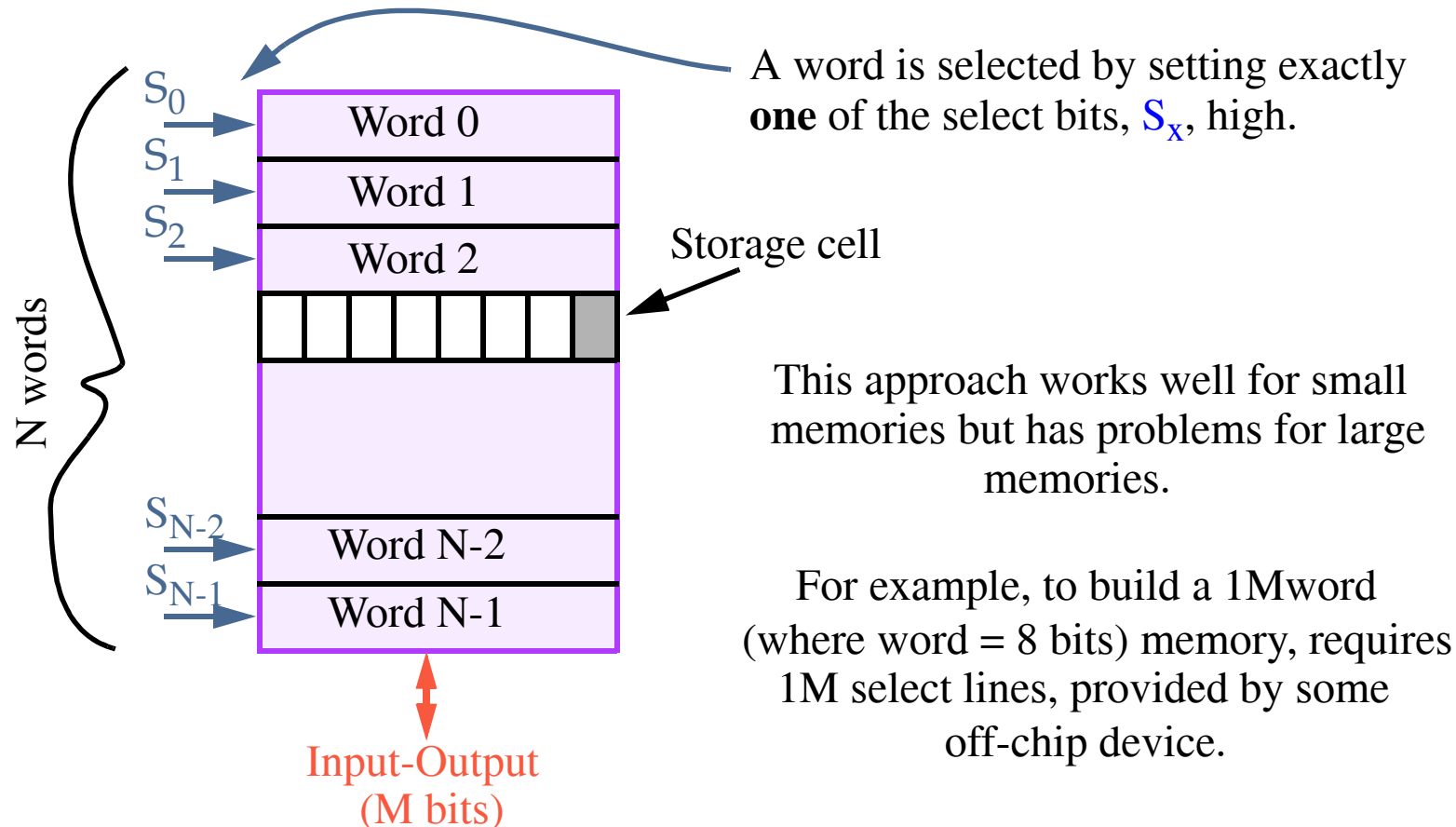In order to build an N -word memory where each word is M bits wide (typically 1, 4 or 8 bits), a straightforward approach is to stack memory:



A word is selected by setting exactly **one** of the select bits, S_x , high.


This approach works well for small memories but has problems for large memories.

For example, to build a 1Mword (where word = 8 bits) memory, requires 1M select lines, provided by some off-chip device.

This approach is not practical. What can we do?

Memory Architecture

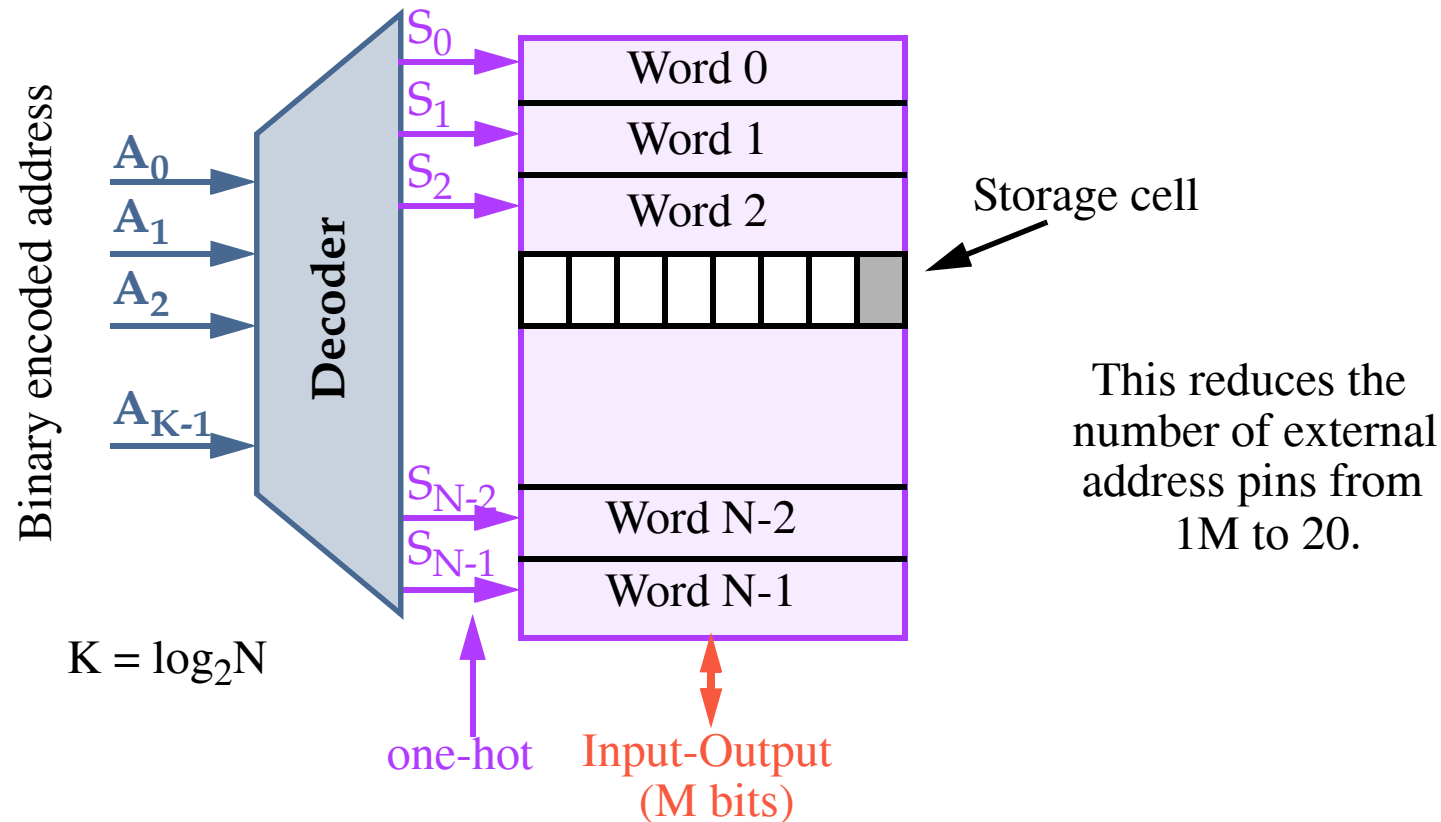Add a decoder to solve the package problem:




This does not address the *memory aspect ratio* problem:

The memory is 128,000 times higher than wide ($2^{20}/2^3$)!

Besides the bizarre shape factor, the design is *extremely slow* since the vertical wires are VERY long (delay is at least linear to length).

Memory Architecture

 The vertical and horizontal dimensions are usually very similar, for an aspect ratio of *unity*. Multiple words are stored in each row and selected simultaneously:




Memory Architecture

This strategy works well for memories up to 64 Kbits to 256 Kbits.

Larger memories start to suffer excess delay along bit and word lines.

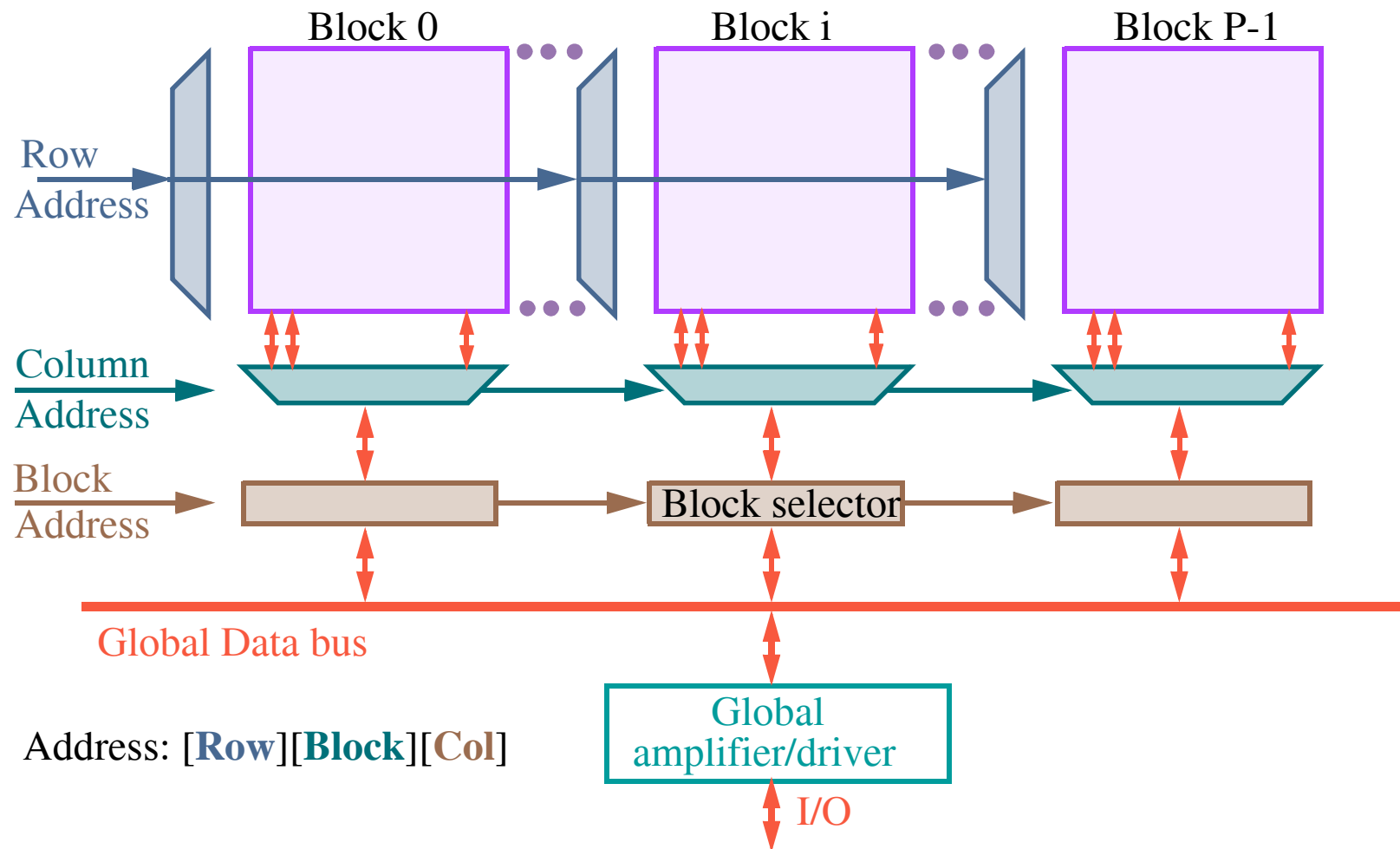A *third dimension* is added to the address space to solve this problem:



Dynamic RAM

DRAM requires refreshing every 2 to 4 *ms*. (some even at 16ms)

This is due to the storage mechanism. Data is stored as charge on a capacitor

This capacitor is not perfect, i.e., it discharges over the course of time via the access transistor.

Refreshing occurs automatically during a read or write.

Internal circuitry takes care of refreshing cells that are not accessed over this interval.

Three different refresh methods are used:

- RAS-only refresh
- CAS before RAS refresh
- Hidden refresh

Refresh time example:


For a 256K X 1 DRAM with 256 rows, a refresh must occur every 15.6 μ s (4ms/256).

For the 8086, a read or write occurs every 800ns.

This allows **19** memory reads/writes per refresh or **5%** of the time.

DRAM Refreshing

RAS-only refresh

 

Simplest and most widely used method for refreshing, carry out a dummy read cycle

\overline{RAS} is activated and a row address (refresh address) is applied to the DRAM, \overline{CAS} inactive


DRAM internally reads one row and amplifies the read data. Not transferred to the output pins as \overline{CAS} is disabled.

The main disadvantage of this refresh method is that an external logic device, or some program, is required to generate the DRAM row addresses in succession.

DMA chip 8237 (will be discussed later) can be used to generate these addresses

DRAM Refreshing

CAS-before-RAS refresh

 

Most modern DRAM chips have one or more internal refresh mode, the most important is the CAS-before-RAS refresh

DRAM chip has its own refresh logic with an address counter


When the above sequence is applied on CAS and RAS the internal refresh logic generates an address and refreshes the associated cells

After every cycle, the internal address counter is incremented

The memory controller just needs to issue the above signals from time-to-time

DRAM Refreshing

Hidden refresh

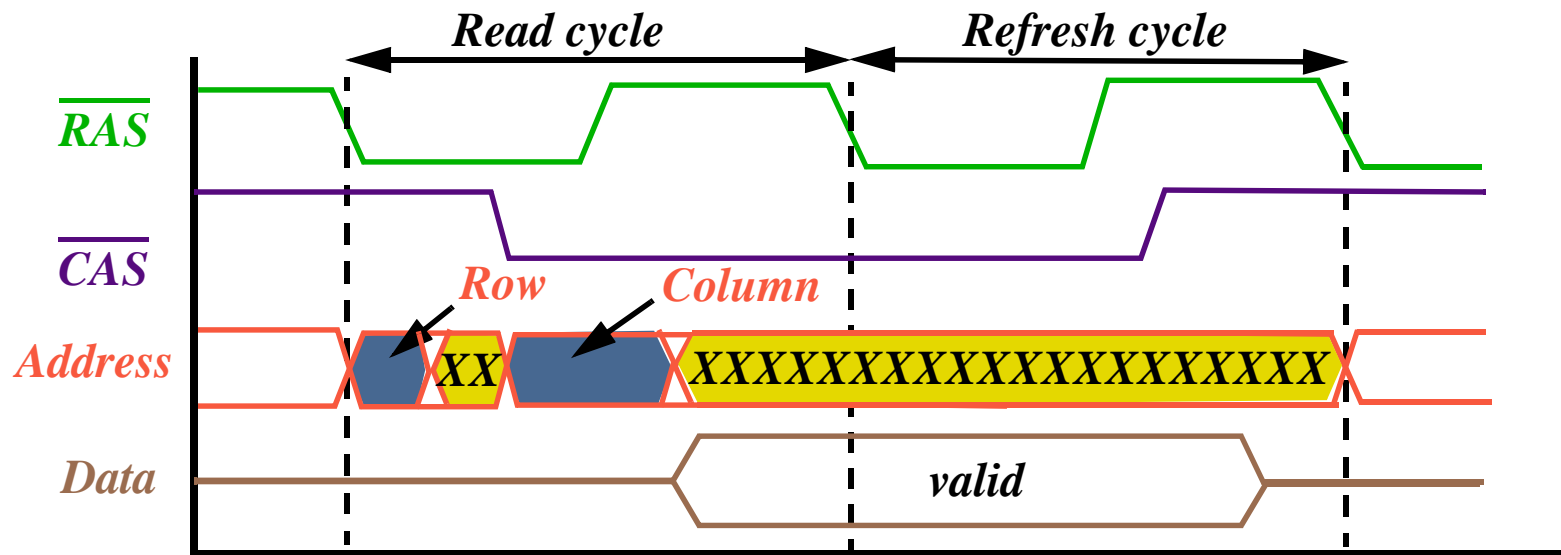

The more elegant option is the hidden refresh

The actual refresh cycle is *hidden* behind a normal read access.

During a hidden refresh the CAS signal is further held on a low level, and only the RAS signal is switched

DRAM Refreshing

Hidden refresh

The data read during the read cycle remains valid even while the refresh cycle is in progress

As the time required for a refresh cycle is less than that of a read cycle this saves time


The address counter for refresh cycle is in the DRAM, the row and column addresses shown in the timing diagram are only for the read cycle

If the CAS signal stays low for a sufficiently long time, several refresh cycles can be carried out in succession by switching the RAS signal frequently between 0 and 1

Most new motherboards implement the option of refreshing the DRAM memory with the CAS-before-RAS or hidden refresh instead of using the DMA chip and the timer chip (as done for older 8086 systems)

Dynamic RAM

256K X 1 DRAM

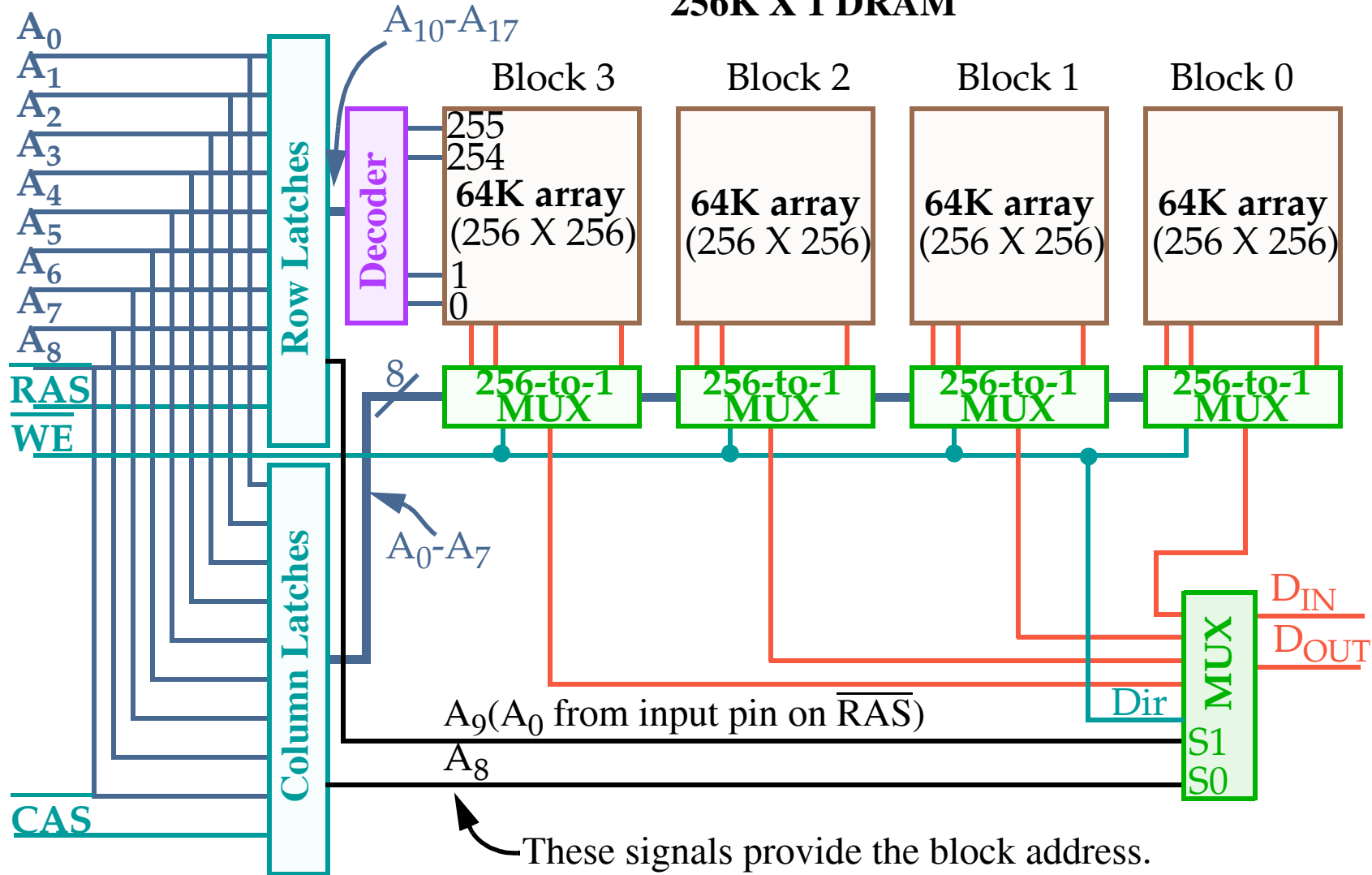

DRAM Controllers

A DRAM controller is usually responsible for address multiplexing and generation of the DRAM control signals.


These devices tend to get very complex. We will focus on a simpler device, the *Intel 82C08*, which can control **two** banks of *256K X 16* DRAM memories for a total of 1 MB.

Microprocessor bits A_1 through A_{18} (18 bits) drive the 9 *Address Low* (AL) and 9 *Address High* (AH) bits of the *82C08*. 9 of each of these are strobed onto the address wires A_0 through A_8 to the memories.

Either RAS0/CAS0 or RAS1/CAS1 are strobed depending on the address.

This drives a *16-bit* word onto the High and Low data buses (if WE is low) or writes an 8 or 16 bit word into the memory otherwise.

DRAM Controllers

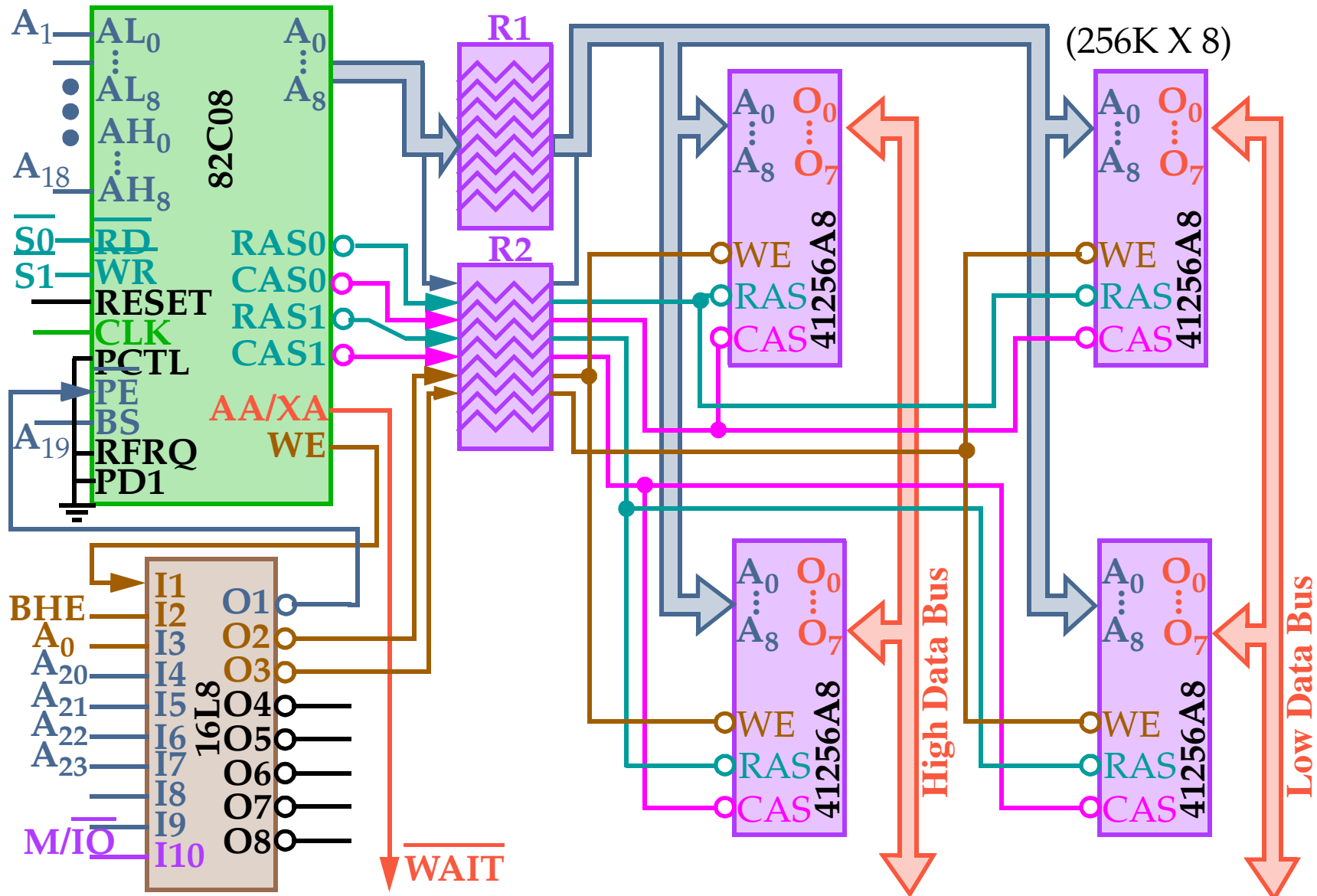


DRAM Controllers

WE (from the 82C08), BHE and A_0 are used to determine if a write is to be performed and which byte(s) (low or high or both) is to be written.

Address bit A_{20} through A_{23} along with $\overline{M/\overline{IO}}$ enable these memories to map onto 1 MByte range (**000000H-0FFFFFFH**).

16L8 Programming:

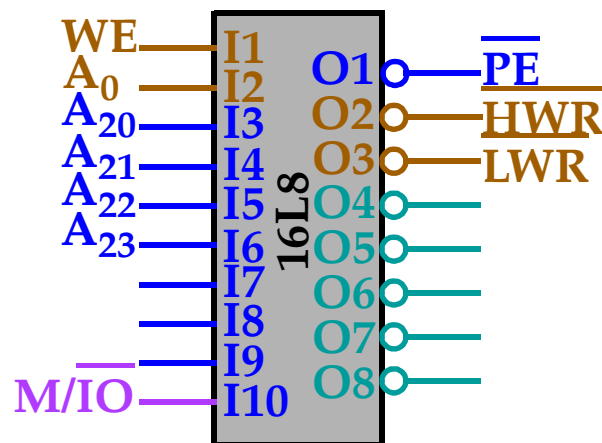

	pins 1	2	3	4	5	6	7	8	9	10
	WE	BHE	A0	A20	A21	A22	A23	NC	NC	GND
	pins 11	12	13	14	15	16	17	18	19	20
	MIO	CE	NC	NC	NC	NC	LWR	HWR	PE	VCC

Equations:

$$/LWR = /A0 * /WE$$

$$/HWR = /BHE * /WE$$

$$/PE = /A20 * /A21 * /A22 * /A23 * MIO$$