

CMPE 641: Assignment 1

Standard Cell Layout and Abstract Generation

Design using the guidelines provided in class slides, the following three cells:

- (1) AND2x1
- (2) XOR2x1 (CMOS version)
- (3) Positive edge-triggered D flip-flop with active low asynchronous set and reset

