

**The Place where
1 + 1 = 1....**

~~Or~~

Boolean Functions and Truth Tables

Review of Objectives

After this lecture, you should be able to.....


- **Simplify Boolean Algebra expressions**
- **Develop combinational logic solutions:**
 - **Sum of Product**
 - **Product of Sum**
- **Configure positive and negative logic circuits**
- **Identify critical parameters for logic gates from their datasheets**
- **Carry out “bubble matching”**

The Basic Properties of Boolean Algebra

Principle of duality: The dual of a Boolean function is gotten by replacing AND with OR and OR with AND, constant 1s by 0s, and 0s by 1s

	Relationship	Dual	Property
Postulates	$AB = BA$	$A + B = B + A$	Commutative
	$A(B + C) = AB + AC$	$A + BC = (A + B)(A + C)$	Distributive
	$1A = A$	$0 + A = A$	Identity
	$A\bar{A} = 0$	$A + \bar{A} = 1$	Complement
Theorems	$0A = 0$	$1 + A = 1$	Zero and one theorems
	$AA = A$	$A + A = A$	Idempotence
	$A(BC) = (AB)C$	$A + (B + C) = (A + B) + C$	Associative
	$\overline{\overline{A}} = A$		Involution
	$\overline{AB} = \overline{A} + \overline{B}$	$\overline{A + B} = \overline{A}\overline{B}$	DeMorgan's Theorem
	$AB + \overline{A}C + BC = AB + \overline{A}C$	$(A + B)(\overline{A} + C)(B + C) = (A + B)(\overline{A} + C)$	Consensus Theorem
	$A(A + B) = A$	$A + AB = A$	Absorption Theorem

Postulates

 


Theorems

A, B, etc. are Literals; 0 and 1 are constants.

DeMorgan's Theorem

A B	$\overline{A B} = \overline{A} + \overline{B}$	$\overline{A + B} = \overline{A} \overline{B}$
0 0	1 1	1 1
0 1	1 1	0 0
1 0	1 1	0 0
1 1	0 0	0 0

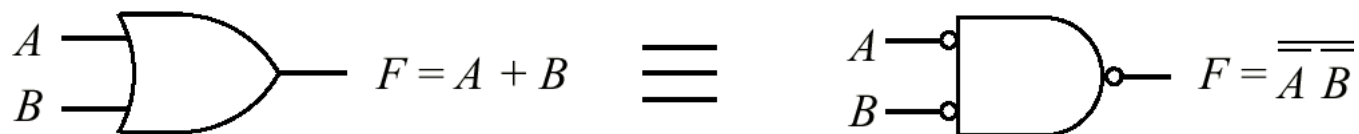DeMorgan's theorem: $A + B = \overline{\overline{A + B}} = \overline{\overline{A} \overline{B}}$




Discuss: Applying DeMorgan's theorem by "pushing the bubbles," and "bubble tricks."

The Sum-of-Products (SOP) Form

Fig. A.15—Truth Table for The Majority Function

Minterm Index	A	B	C	F
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1



A balance tips to the left or right depending on whether there are more 0's or 1's.

- Transform the function into a two-level AND-OR equation
- Implement the function with an arrangement of logic gates from the set {AND, OR, NOT}
- F is true when A=0, B=1, and C=1, or when A=1, B=0, and C=1, and so on for the remaining cases.
- Represent logic equations by using the sum-of-products (SOP) form


The SOP Form of the Majority Gate

- The SOP form for the 3-input majority gate is:

- $M = \overline{A}BC + A\overline{B}C + ABC + AB\overline{C} = m_3 + m_5 + m_6 + m_7 = \sum (3, 5, 6, 7)$


- Each of the 2^n terms are called minterms, running from 0 to $2^n - 1$
- Note the relationship between minterm number and boolean value.
- Discuss: common-sense interpretation of equation.

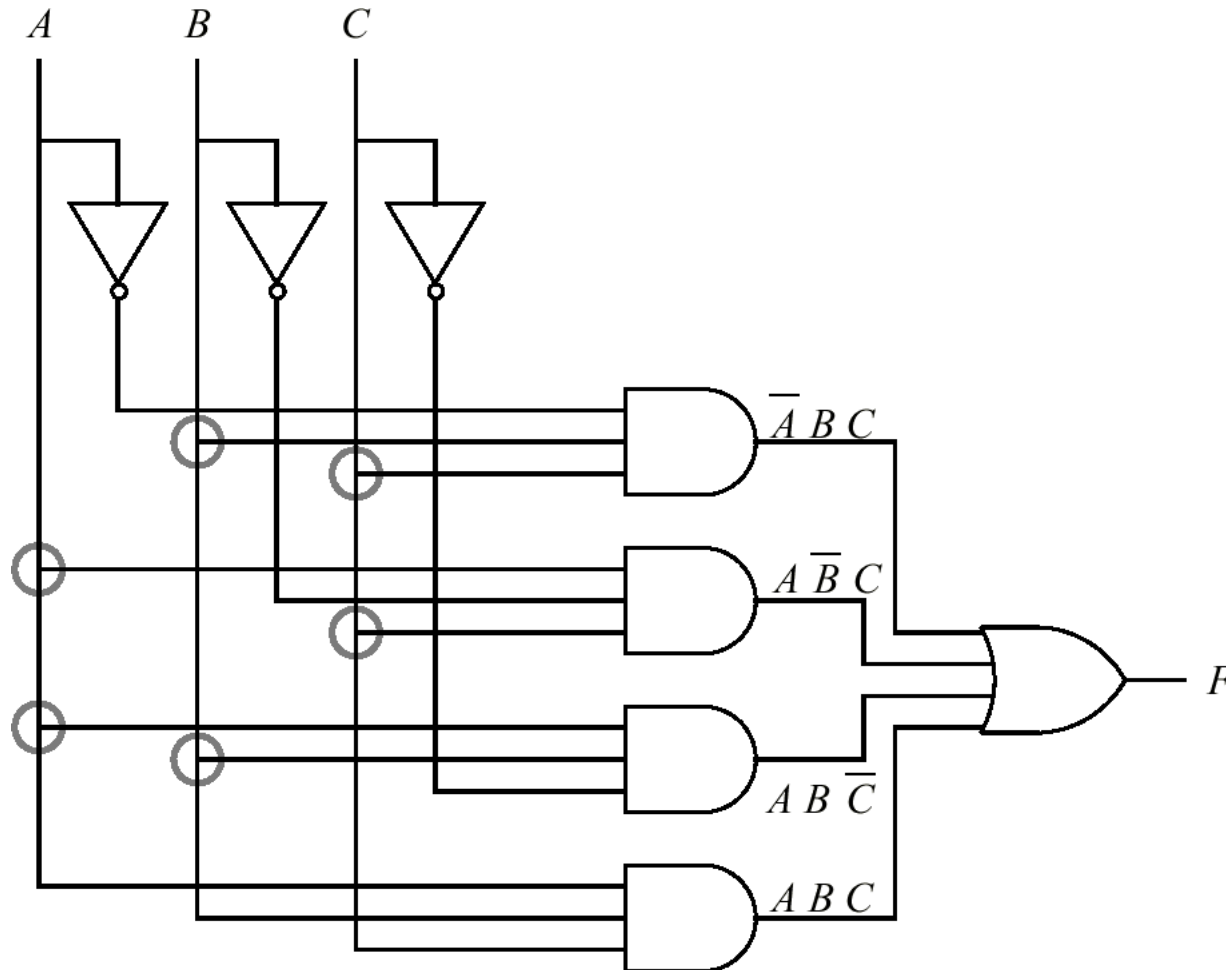A 2-Level AND-OR Circuit that Implements the Majority Function




Discuss: What is the Gate Count?


Notation Used at Circuit Intersections

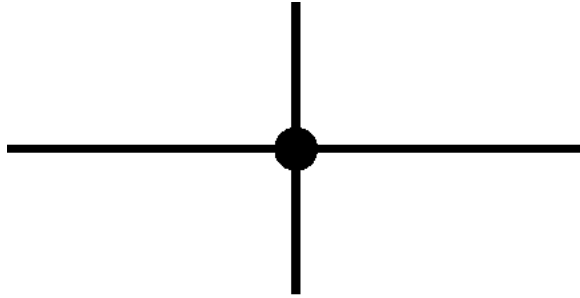


Connection

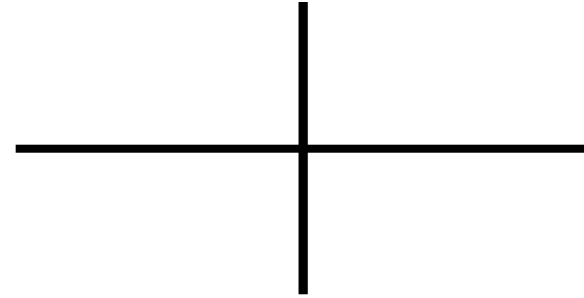

No connection

 


Connection

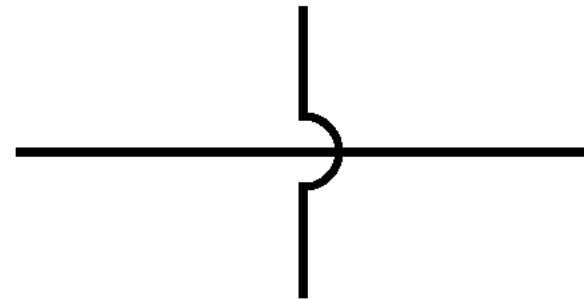

No connection

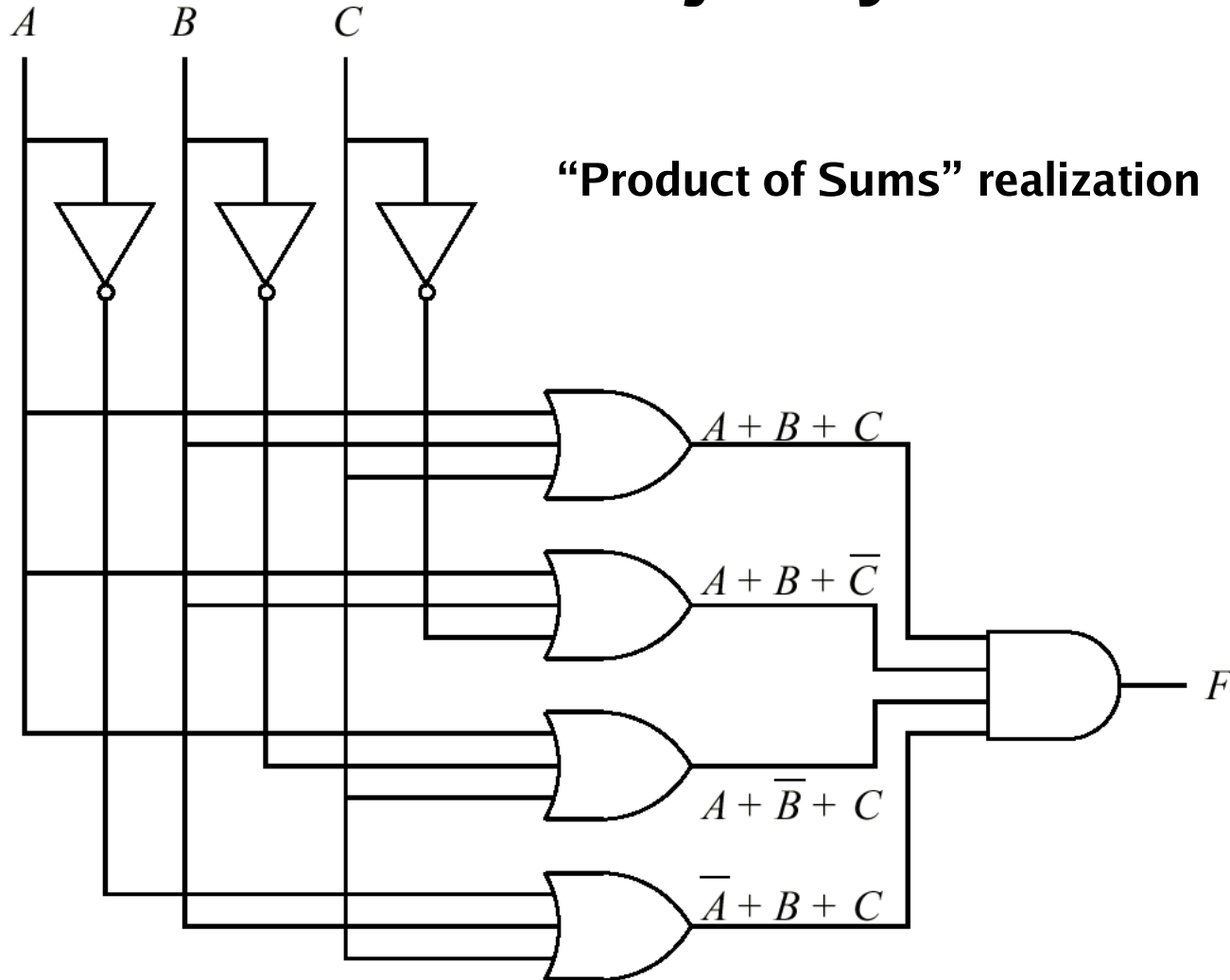A 2-Level OR-AND Circuit that Implements the Majority Function



Positive vs. Negative Logic

- Positive logic: truth, or assertion is represented by logic 1, higher voltage; falsity, de- or unassertion, logic 0, is represented by lower voltage.
- Negative logic: truth, or assertion is represented by logic 0, lower voltage; falsity, de- or unassertion, logic 1, is represented by higher voltage

Gate Logic: Positive vs. Negative Logic

Normal Convention: Positive Logic/Active High
Low Voltage = 0; High Voltage = 1


Alternative Convention sometimes used: Negative Logic/Active Low



Voltage Truth Table


A	B	F
low	low	low
low	high	low
high	low	low
high	high	high

Behavior in terms
of Electrical Levels

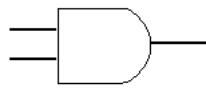

Positive Logic

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

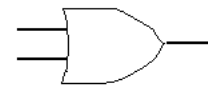

Negative Logic

A	B	F
1	1	1
1	0	1
0	1	1
0	0	0


Two Alternative Interpretations
Positive Logic AND
Negative Logic OR

Dual Operations

Positive and Negative Logic (Cont'd.)


Voltage Levels

A	B	F
low	low	low
low	high	low
high	low	low
high	high	high

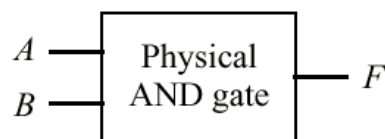


Positive Logic Levels

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

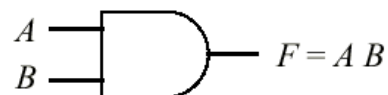


Negative Logic Levels

A	B	F
1	1	1
1	0	1
0	1	1
0	0	0

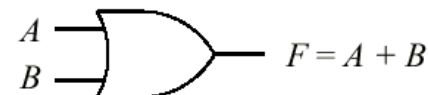

Voltage Levels

A	B	F
low	low	high
low	high	high
high	low	high
high	high	low

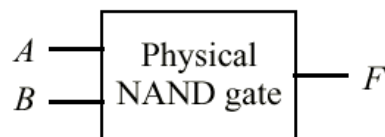


Positive Logic Levels

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0



Negative Logic Levels


A	B	F
1	1	0
1	0	0
0	1	0
0	0	1

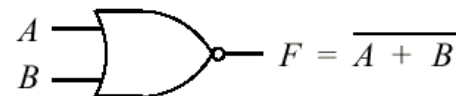


Bubble Matching

- Active low signals are signified by a prime or overbar or /.
- Active high: enable _____
- Active low: enable', enable, enable/
- Discuss microwave oven control:
- Active high: Heat = DoorClosed • Start
- Active low: ? (hint: begin with AND gate as before.)


Bubble Matching (Cont'd.)

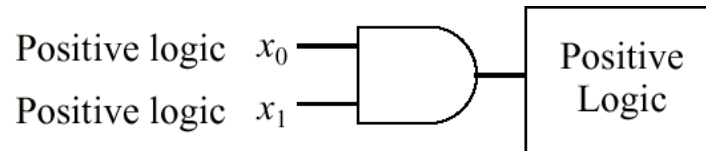


(a)

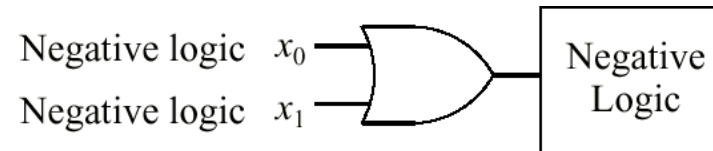

(b)

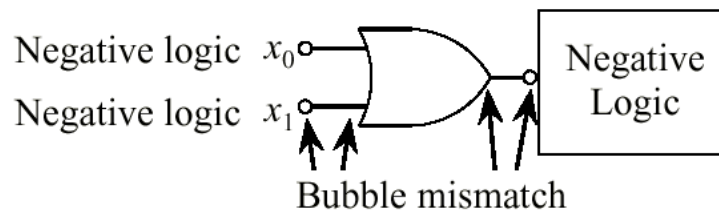

(c)

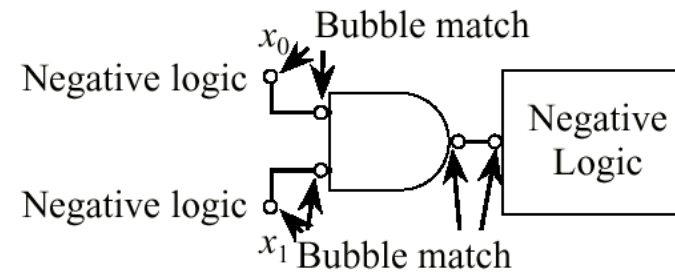

(d)

Digital Components

- **High level digital circuit designs are normally made using collections of logic gates referred to as components, rather than using individual logic gates. The majority function can be viewed as a component.**
- **Levels of integration (numbers of gates) in an integrated circuit (IC):**
- **Small scale integration (SSI): 10-100 gates.**
- **Medium scale integration (MSI): 100 to 1000 gates.**
- **Large scale integration (LSI): 1000-10,000 logic gates.**
- **Very large scale integration (VLSI): 10,000-upward.**
- **These levels are approximate, but the distinctions are useful in comparing the relative complexity of circuits.**
- **Let us consider several useful MSI components:**

Objectives Completed

- Reviewed rules of Boolean algebra
- Investigated two combinational logic forms:
 - Sum of Product : SOP
 - Product of Sum : POS
- Distinguished between positive and negative logic
- Identified critical parameters for logic gates from datasheets
- Carried out “bubble matching”

Next time we will....

- **Examine logic components**
- **Describe and apply typical component functions**
- **Develop a ripple carry adder using logic components**