

Beyond SSI Logic Integrated Circuits

Combinational Logic Components

Learning Objectives

After this lecture, you should be able to.....

- **Distinguish between logic gates and components**
- **Describe and apply the listed functions:**
 - **Multiplexer**
 - **Demultiplexer**
 - **Decoder**
 - **Priority Encoder**
 - **Programmable Logic Array**
- **Design a ripple carry adder using the different components described**

Digital Components

High level digital circuit designs are normally made using collections of logic gates referred to as components, rather than using individual logic gates. The majority function can be viewed as a component.

Levels of integration (numbers of gates) in an integrated circuit (IC):

Small scale integration (SSI): 10-100 gates.

Medium scale integration (MSI): 100 to 1000 gates.


Large scale integration (LSI): 1000-10,000 logic gates.

Very large scale integration (VLSI): 10,000-upward.

These levels are approximate, but the distinctions are useful in comparing the relative complexity of circuits.

Let us consider several useful MSI components:


A Simple Multiplexer

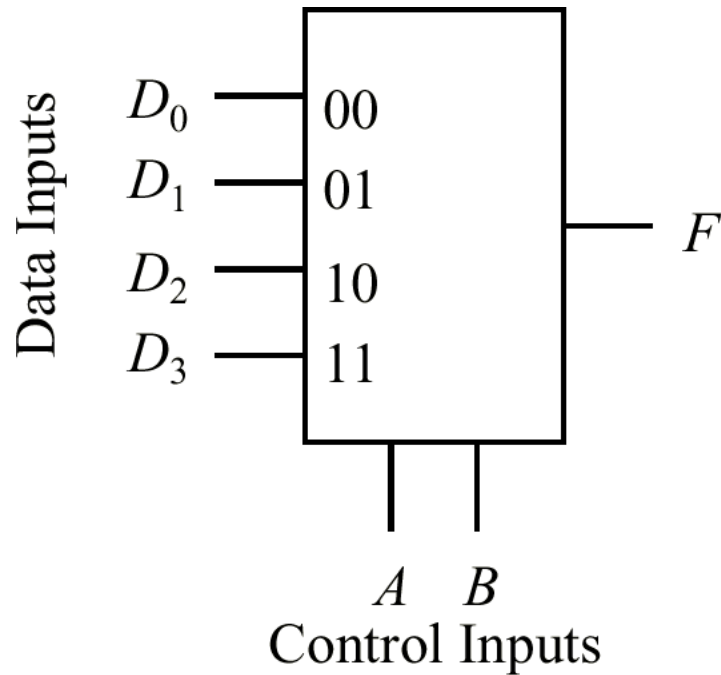

A	B	F
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3


$$F = \bar{A} \bar{B} D_0 + \bar{A} B D_1 + A \bar{B} D_2 + A B D_3$$

The Multiplexer

 

Implementing the Majority Function with an 8-1 Mux



<i>A</i>	<i>B</i>	<i>C</i>	<i>M</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

Principle: Use the mux select to pick out the selected minterms of the function.


More Efficiency: Using a 4-1 Mux to Implement the Majority Function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

  

Principle: Use the A and B inputs to select a pair of minterms. The value applied to the MUX input is selected from $\{0, 1, C, \overline{C}\}$ to pick the desired behavior of the minterm pair.

The Demultiplexer (DEMUX)

 



D	A	B	F_0	F_1	F_2	F_3
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

$$F_0 = D \bar{A} \bar{B} \quad F_2 = D A \bar{B}$$

$$F_1 = D \bar{A} B \quad F_3 = D A B$$

The Demultiplexer is a Decoder with an Enable Input

Compare to
Fig A.29

  


		Enable = 1			
A	B	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1


		Enable = 0			
A	B	D ₀	D ₁	D ₂	D ₃
0	0	0	0	0	0
0	1	0	0	0	0
1	0	0	0	0	0
1	1	0	0	0	0

$$D_0 = \bar{A}\bar{B} \quad D_1 = \bar{A}B \quad D_2 = A\bar{B} \quad D_3 = AB$$

A 2-4 Decoder

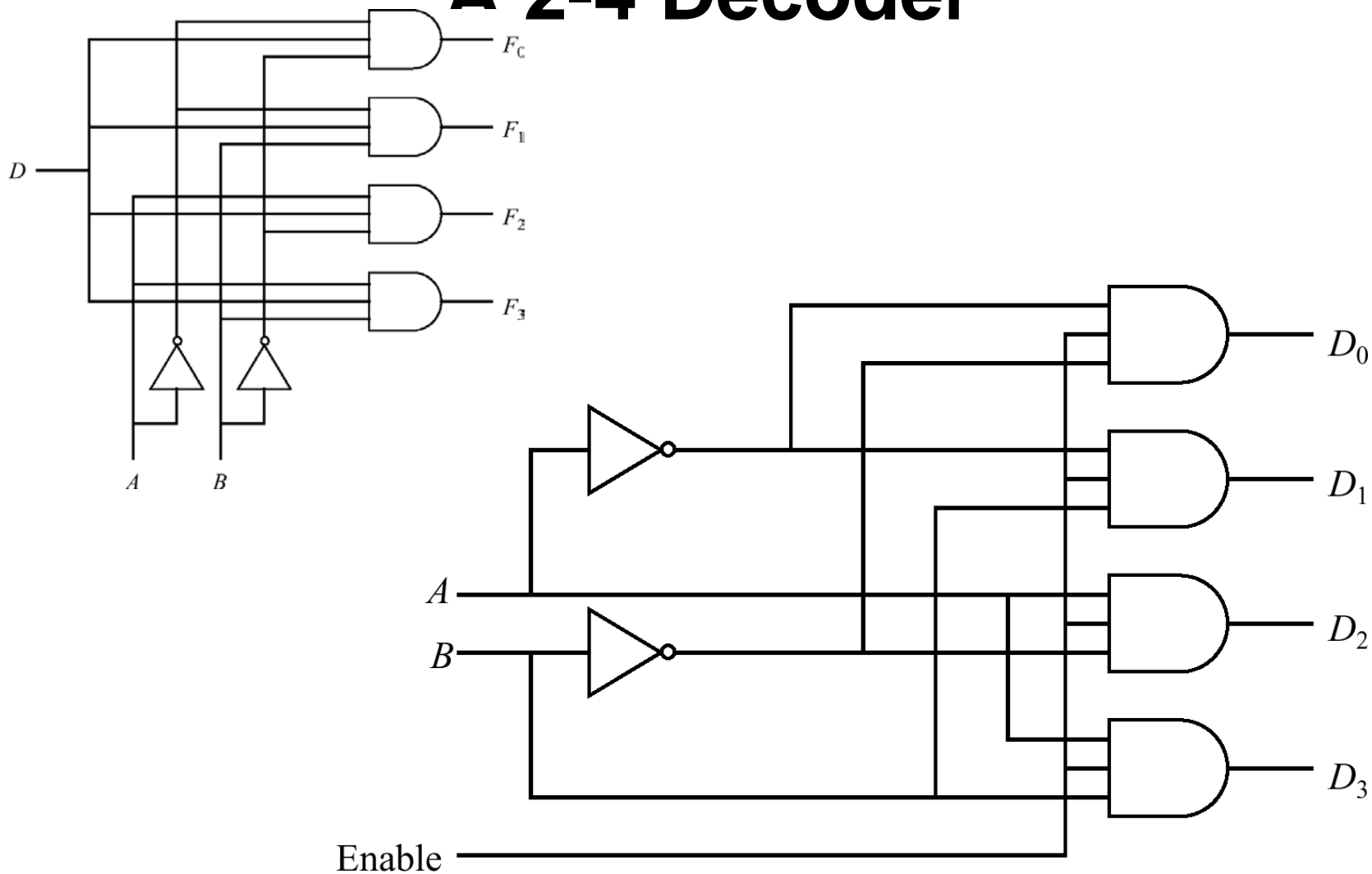

 Using a Decoder to Implement the Majority Function




The Priority Encoder

An encoder translates a set of inputs into a binary encoding,

Can be thought of as the converse of a decoder.

A priority encoder imposes an order on the inputs.


A_i has a higher priority than A_{i+1}

 

$$F_0 = \overline{A_0} \overline{A_1} A_3 + \overline{A_0} A_1 \overline{A_2}$$



$$F_1 = \overline{A_0} A_2 A_3 + \overline{A_0} A_1$$

A_0	A_1	A_2	A_3	F_0	F_1
0	0	0	0	0	0
0	0	0	1	1	1
0	0	1	0	1	0
0	0	1	1	1	0
0	1	0	0	0	1
0	1	0	1	0	1
0	1	1	0	0	1
0	1	1	1	0	1
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	0	0

 


Programmable Logic Arrays (PLAs)

  
A PLA is a customizable AND matrix followed by a customizable OR matrix:



 
Using a PLA to Implement the Majority Function




Using PLAs to Implement an Adder

 


Example:

 


A_i	B_i	C_i	S_i	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

A Multi-Bit Ripple-Carry Adder

 

PLA Realization of a Full Adder

 

Objectives Completed

- Differentiated logic gates from components
- Described the function of the Multiplexer (MUX), Demultiplexer (DEMUX), Decoder, Priority Encoder, Programmable Logic Array
- Designed a ripple carry adder using the different components described

Next time

- **Making smaller circuits with logic reduction techniques**
- **Characterizing propagation delay in gates**
- **OR gate and MUX decomposition methods of logic reduction**

SSI : small scale integrated circuit