

Making Finite State Machines Simpler

~~~~~

## FSM State Reduction

# Review of Objectives

After this lecture, you should be able to...

- **Declare the 2 conditions necessary for states in an FSM to be EQUIVALENT**
- **Use a state reduction to lower the number of required FSM states so that the design flow takes the form shown:-**
- **STEPS IN REDUCED FSM DESIGN**
  - **Draw a state transition diagram**
  - **Reduce number of states if possible**
  - **Derive a state table from the state transition diagram**
  - **Assign states, determine number, type of FF's required**
  - **Draw up a truth table**
  - **Design logic for combinational logic unit**
  - **Draw the complete schematic**
- **Write D, RS, T and JK FF excitation tables**
- **Employ FF excitation tables to use any kind of FF in an FSM designs**

# Definitions for FSM State Reduction

- **Condition #1** : The outputs associated with 2 states are the SAME
- **Condition #2** : Corresponding Next States are the SAME or EQUIVALENT
- With these 2 conditions satisfied, we can **COMBINE** the 2 states into 1 newly named state

# State Reduction

- Description of state machine  $M_0$  to be reduced.

| Present state \ Input | $X$ |     |
|-----------------------|-----|-----|
|                       | 0   | 1   |
| $A$                   | C/0 | E/1 |
| $B$                   | D/0 | E/1 |
| $C$                   | C/1 | B/0 |
| $D$                   | C/1 | A/0 |
| $E$                   | A/0 | C/1 |

# State Reduction – Step 1

- Look for output compatible transitions: Note that {A,B and E} and {C,D} transition to **OUTPUT compatible** states

| Present state \ Input | $X$ |     |
|-----------------------|-----|-----|
|                       | 0   | 1   |
| $A$                   | C/0 | E/1 |
| $B$                   | D/0 | E/1 |
| $C$                   | C/1 | B/0 |
| $D$                   | C/1 | A/0 |
| $E$                   | A/0 | C/1 |

## State Reduction – Step 2

- Take each collection of states and examine each pair within the set for possibly equivalent states with the different inputs  $X=0$  and  $X=1$

| Possibly Equivalent Pairs | Next State pairing with $X=0$<br>[output incompatible] = [!] | Next State pairing with $X=1$<br>[output incompatible] = [!] |
|---------------------------|--------------------------------------------------------------|--------------------------------------------------------------|
| (A,B)                     | (C,D)                                                        |                                                              |
| (A,E)                     | (A,C) [!]                                                    | (C,E) [!]                                                    |
| (B,E)                     | (A,D) [!]                                                    | (C,E) [!]                                                    |

| Possibly Equivalent Pairs | Next State pairing with $X=0$<br>[output incompatible] = [!] | Next State pairing with $X=1$<br>[output incompatible] = [!] |
|---------------------------|--------------------------------------------------------------|--------------------------------------------------------------|
| (C,D)                     |                                                              | (A,B)                                                        |

# State Reduction – Step 3

- **Eliminate pairs that are not output compatible:**
- **We see that E is not compatible with A or B or by implication with (C,D) which are already seen to be output incompatible. So E cannot be eliminated nor combined with other states.**

**So we have pairs {A,B}, {C,D} and {E} which represent 3 states which allow the FSM definition to remain unchanged.**

# Reduced State Table – Step 4

- We have  $\{A,B\}$ ,  $\{C,D\}$  and  $\{E\}$  as the new set of states, which we will rename as  $A'$   $B'$  and  $C'$  for the reduced FSM's internal states.
- We now write the “reduced state” state table for machine  $M_1$ .

| Current state \ Input | $X$    |        |
|-----------------------|--------|--------|
|                       | 0      | 1      |
| $AB: A'$              | $B'/0$ | $C'/1$ |
| $CD: B'$              | $B'/1$ | $A'/0$ |
| $E: C'$               | $A'/0$ | $B'/1$ |



# The State Assignment Problem

- Two state assignments for machine  $M_2$ .

| Input<br>P.S. | $X$   |       |
|---------------|-------|-------|
|               | 0     | 1     |
| $A$           | $B/1$ | $A/1$ |
| $B$           | $C/0$ | $D/1$ |
| $C$           | $C/0$ | $D/0$ |
| $D$           | $B/1$ | $A/0$ |

Machine  $M_2$ 

| Input<br>$S_0S_1$ | $X$    |        |
|-------------------|--------|--------|
|                   | 0      | 1      |
| $A: 00$           | $01/1$ | $00/1$ |
| $B: 01$           | $10/0$ | $11/1$ |
| $C: 10$           | $10/0$ | $11/0$ |
| $D: 11$           | $01/1$ | $00/0$ |

State assignment  $SA_0$ 

| Input<br>$S_0S_1$ | $X$    |        |
|-------------------|--------|--------|
|                   | 0      | 1      |
| $A: 00$           | $01/1$ | $00/1$ |
| $B: 01$           | $11/0$ | $10/1$ |
| $C: 11$           | $11/0$ | $10/0$ |
| $D: 10$           | $01/1$ | $00/0$ |

State assignment  $SA_1$

# State Assignment SA<sub>0</sub>

- Boolean equations for machine  $M_2$  using state assignment SA<sub>0</sub>.

|          |    | $X$ |   |
|----------|----|-----|---|
|          |    | 0   | 1 |
| $S_0S_1$ | 00 |     |   |
|          | 01 | 1   | 1 |
| 11       |    |     |   |
| 10       | 1  | 1   |   |

$$S_0 = \bar{S}_0S_1 + S_0\bar{S}_1$$

|          |    | $X$ |   |
|----------|----|-----|---|
|          |    | 0   | 1 |
| $S_0S_1$ | 00 | 1   |   |
|          | 01 |     | 1 |
| 11       | 1  |     |   |
| 10       |    | 1   |   |

$$S_1 = \bar{S}_0\bar{S}_1\bar{X} + \bar{S}_0S_1X + S_0S_1\bar{X} + S_0\bar{S}_1X$$

|          |    | $X$ |   |
|----------|----|-----|---|
|          |    | 0   | 1 |
| $S_0S_1$ | 00 | 1   | 1 |
|          | 01 |     | 1 |
| 11       | 1  |     |   |
| 10       |    |     |   |

$$Z = \bar{S}_0\bar{S}_1 + \bar{S}_0X + S_0S_1\bar{X}$$

# State Assignment SA<sub>1</sub>

- Boolean equations for machine  $M_2$  using state assignment SA<sub>1</sub>.

|          |    |     |   |
|----------|----|-----|---|
|          |    | $X$ |   |
|          |    | 0   | 1 |
| $S_0S_1$ | 00 |     |   |
|          | 01 | 1   | 1 |
|          | 11 | 1   | 1 |
|          | 10 |     |   |

$$S_0 = S_1$$


|          |    |     |   |
|----------|----|-----|---|
|          |    | $X$ |   |
|          |    | 0   | 1 |
| $S_0S_1$ | 00 | 1   |   |
|          | 01 | 1   |   |
|          | 11 | 1   |   |
|          | 10 | 1   |   |

$$S_1 = \bar{X}$$

|          |    |     |   |
|----------|----|-----|---|
|          |    | $X$ |   |
|          |    | 0   | 1 |
| $S_0S_1$ | 00 | 1   | 1 |
|          | 01 |     | 1 |
|          | 11 |     |   |
|          | 10 | 1   |   |

$$Z = \bar{S}_1\bar{X} + \bar{S}_0X$$
 
# Sequence Detector State Transition Diagram



Input: 0 1 1 0 1 1 1 0 0

Output: 0 0 1 1 1 1 0 1 0

Time: 0 1 2 3 4 5 6 7 8

# Sequence Detector State Table

| Present state \ Input | $X$   |       |
|-----------------------|-------|-------|
|                       | 0     | 1     |
| $A$                   | $B/0$ | $C/0$ |
| $B$                   | $D/0$ | $E/0$ |
| $C$                   | $F/0$ | $G/0$ |
| $D$                   | $D/0$ | $E/0$ |
| $E$                   | $F/0$ | $G/1$ |
| $F$                   | $D/0$ | $E/1$ |
| $G$                   | $F/1$ | $G/0$ |

# Sequence Detector Reduced State Table

| Present state \ Input | $X$   |       |
|-----------------------|-------|-------|
|                       | 0     | 1     |
| $A: A'$               | $B'0$ | $C'0$ |
| $BD: B'$              | $B'0$ | $D'0$ |
| $C: C'$               | $E'0$ | $F'0$ |
| $E: D'$               | $E'0$ | $F'1$ |
| $F: E'$               | $B'0$ | $D'1$ |
| $G: F'$               | $E'1$ | $F'0$ |

# Sequence Detector State Assignment

| Present state \ Input | $X$          |              |
|-----------------------|--------------|--------------|
|                       | 0            | 1            |
| $S_2S_1S_0$           | $S_2S_1S_0Z$ | $S_2S_1S_0Z$ |
| $A': 000$             | 001/0        | 010/0        |
| $B': 001$             | 001/0        | 011/0        |
| $C': 010$             | 100/0        | 101/0        |
| $D': 011$             | 100/0        | 101/1        |
| $E': 100$             | 001/0        | 011/1        |
| $F': 101$             | 100/1        | 101/0        |

# Sequence Detector K-Maps

- K-map reduction of next state and output functions for sequence detector.

|          |    |    |     |     |
|----------|----|----|-----|-----|
| $S_2S_1$ | 00 | 01 | 11  | 10  |
| $S_0X$   | 00 | 1  | $d$ | 1   |
|          | 01 |    | 1   | $d$ |
|          | 11 | 1  | 1   | $d$ |
|          | 10 | 1  |     | $d$ |

$$S_0 = \overline{S_2}\overline{S_1}\overline{X} + S_0X + S_2\overline{S_0} + S_1X$$

|          |    |    |     |     |
|----------|----|----|-----|-----|
| $S_2S_1$ | 00 | 01 | 11  | 10  |
| $S_0X$   | 00 |    | $d$ |     |
|          | 01 | 1  |     | $d$ |
|          | 11 | 1  |     | $d$ |
|          | 10 |    |     | $d$ |

$$S_1 = \overline{S_2}\overline{S_1}X + S_2\overline{S_0}X$$

|          |    |    |    |     |
|----------|----|----|----|-----|
| $S_2S_1$ | 00 | 01 | 11 | 10  |
| $S_0X$   | 00 |    | 1  | $d$ |
|          | 01 |    | 1  | $d$ |
|          | 11 |    | 1  | $d$ |
|          | 10 |    | 1  | $d$ |


$$S_2 = S_2S_0 + S_1$$

|          |    |    |     |     |
|----------|----|----|-----|-----|
| $S_2S_1$ | 00 | 01 | 11  | 10  |
| $S_0X$   | 00 |    | $d$ |     |
|          | 01 |    | $d$ | 1   |
|          | 11 |    | 1   | $d$ |
|          | 10 |    | $d$ | 1   |

$$Z = S_2\overline{S_0}X + S_1S_0X + S_2S_0\overline{X}$$




# Sequence Detector Circuit

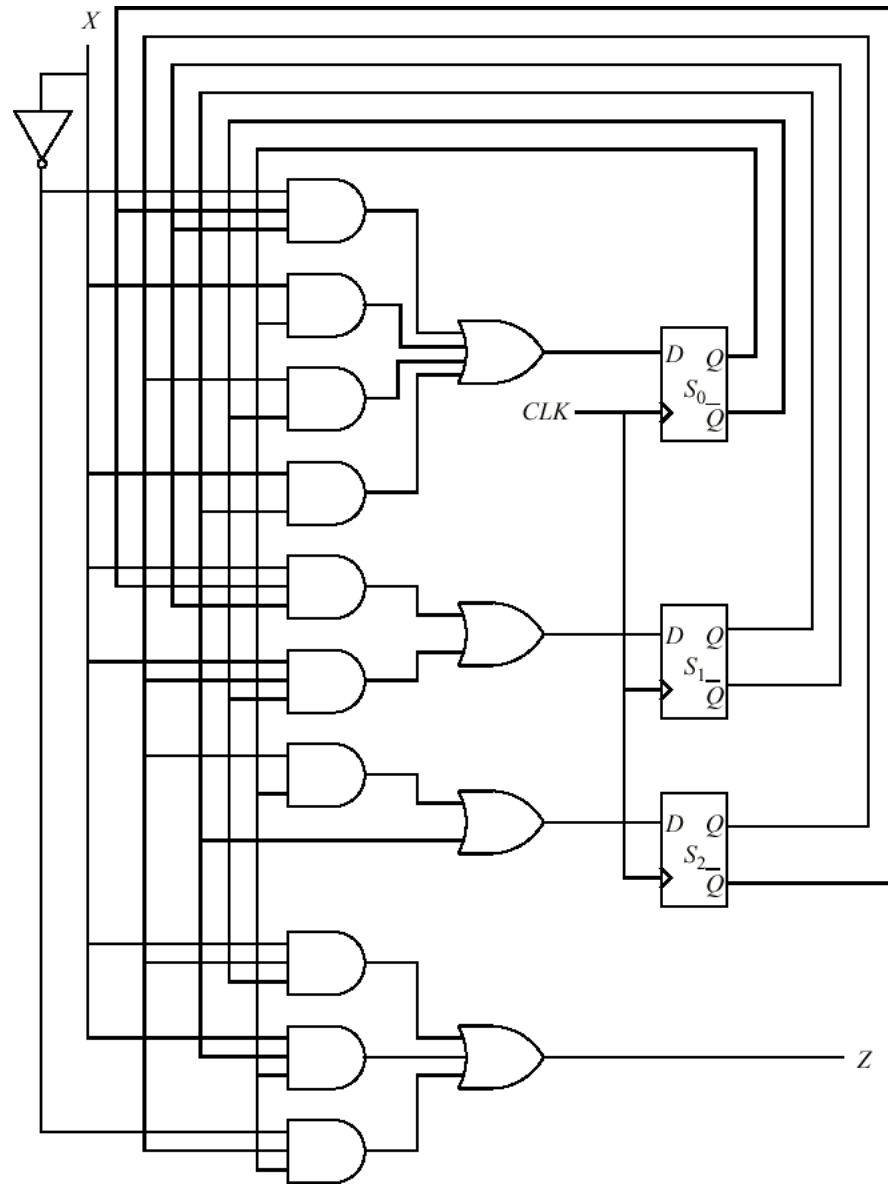

 
# Excitation Tables

- In addition to the D flip-flop, the S-R, J-K, and T flip-flops are used as delay elements in finite state machines.
- A Master-Slave J-K flip-flop is shown below.



 
# Clocked T Flip-Flop

- Logic diagram and symbol for a T flip-flop.



Circuit

 

Symbol

# Excitation Tables

- Each table shows the settings that must be applied at the inputs at time  $t$  in order to change the outputs at time  $t+1$ .

*S-R*  
*flip-flop*

| $Q_t$ | $Q_{t+1}$ | $S$ | $R$ |
|-------|-----------|-----|-----|
| 0     | 0         | 0   | 0   |
| 0     | 1         | 1   | 0   |
| 1     | 0         | 0   | 1   |
| 1     | 1         | 0   | 0   |

*D*  
*flip-flop*

| $Q_t$ | $Q_{t+1}$ | $D$ |
|-------|-----------|-----|
| 0     | 0         | 0   |
| 0     | 1         | 1   |
| 1     | 0         | 0   |
| 1     | 1         | 1   |


*J-K*  
*flip-flop*

| $Q_t$ | $Q_{t+1}$ | $J$ | $K$ |
|-------|-----------|-----|-----|
| 0     | 0         | 0   | $d$ |
| 0     | 1         | 1   | $d$ |
| 1     | 0         | $d$ | 1   |
| 1     | 1         | $d$ | 0   |

*T*  
*flip-flop*

| $Q_t$ | $Q_{t+1}$ | $T$ |
|-------|-----------|-----|
| 0     | 0         | 0   |
| 0     | 1         | 1   |
| 1     | 0         | 1   |
| 1     | 1         | 0   |

# Serial Adder

 

- **State transition diagram, state table, and state assignment for a serial adder.**

| Present state \ Input | Input $XY$ |       |       |       |
|-----------------------|------------|-------|-------|-------|
|                       | 00         | 01    | 10    | 11    |
| $A$                   | $A/0$      | $A/1$ | $A/1$ | $B/0$ |
| $B$                   | $A/1$      | $B/0$ | $B/0$ | $B/1$ |

Next state      Output

| Present state ( $S_i$ ) \ Input | Input $XY$ |     |     |     |
|---------------------------------|------------|-----|-----|-----|
|                                 | 00         | 01  | 10  | 11  |
| $A:0$                           | 0/0        | 0/1 | 0/1 | 1/0 |
| $B:1$                           | 0/1        | 1/0 | 1/0 | 1/1 |

# Serial Adder Next-State Functions

- Truth table showing next-state functions for a serial adder for D, S-R, T, and J-K flip-flops. Shaded functions are used in the example.


| Present State |     |       | (Set) (Reset) |     |     |     |     |     |     |
|---------------|-----|-------|---------------|-----|-----|-----|-----|-----|-----|
| $X$           | $Y$ | $S_t$ | $D$           | $S$ | $R$ | $T$ | $J$ | $K$ | $Z$ |
| 0             | 0   | 0     | 0             | 0   | 0   | 0   | 0   | $d$ | 0   |
| 0             | 0   | 1     | 0             | 0   | 1   | 1   | $d$ | 1   | 1   |
| 0             | 1   | 0     | 0             | 0   | 0   | 0   | 0   | $d$ | 1   |
| 0             | 1   | 1     | 1             | 0   | 0   | 0   | $d$ | 0   | 0   |
| 1             | 0   | 0     | 0             | 0   | 0   | 0   | 0   | $d$ | 1   |
| 1             | 0   | 1     | 1             | 0   | 0   | 0   | $d$ | 0   | 0   |
| 1             | 1   | 0     | 1             | 1   | 0   | 1   | 1   | $d$ | 0   |
| 1             | 1   | 1     | 1             | 0   | 0   | 0   | $d$ | 0   | 1   |

# J-K Flip-Flop Serial Adder Circuit


$$J = XY$$

$$K = \bar{X}\bar{Y}$$
 
$$Z = \bar{X}\bar{Y}S + \bar{X}Y\bar{S} + XY S + X\bar{Y}\bar{S}$$




# D Flip-Flop Serial Adder Circuit

 



# Majority Finite State Machine

 

# Majority FSM State Table

- (a) State table for majority FSM; (b) partitioning; (c) reduced state table.

| P.S. \ Input | X   |     |
|--------------|-----|-----|
|              | 0   | 1   |
| A            | B/0 | C/0 |
| B            | D/0 | E/0 |
| C            | F/0 | G/0 |
| D            | A/0 | A/0 |
| E            | A/0 | A/1 |
| F            | A/0 | A/1 |
| G            | A/1 | A/1 |

(a)

$$\begin{aligned}
 P_0 &= (ABCDEFGG) \\
 P_1 &= (ABCD)(EF)(G) \\
 P_2 &= (AD)(B)(C)(EF)(G) \\
 P_3 &= (A)(B)(C)(D)(EF)(G) \\
 P_4 &= (A)(B)(C)(D)(EF)(G) \checkmark
 \end{aligned}$$

(b)

| P.S. \ Input | X    |      |
|--------------|------|------|
|              | 0    | 1    |
| A: A'        | B'/0 | C'/0 |
| B: B'        | D'/0 | E'/0 |
| C: C'        | E'/0 | F'/0 |
| D: D'        | A'/0 | A'/0 |
| EF: E'       | A'/0 | A'/1 |
| G: F'        | A'/1 | A'/1 |

(c)

# Majority FSM State Assignment

- (a) State assignment for reduced majority FSM using D flip-flops; and (b) using T flip-flops.


| P.S. \ Input | X            |              |
|--------------|--------------|--------------|
|              | 0            | 1            |
| $S_2S_1S_0$  | $S_2S_1S_0Z$ | $S_2S_1S_0Z$ |
| $A': 000$    | 001/0        | 010/0        |
| $B': 001$    | 011/0        | 100/0        |
| $C': 010$    | 100/0        | 101/0        |
| $D': 011$    | 000/0        | 000/0        |
| $E': 100$    | 000/0        | 000/1        |
| $F': 101$    | 000/1        | 000/1        |

(a)

| P.S. \ Input | X            |              |
|--------------|--------------|--------------|
|              | 0            | 1            |
| $S_2S_1S_0$  | $T_2T_1T_0Z$ | $T_2T_1T_0Z$ |
| $A': 000$    | 001/0        | 010/0        |
| $B': 001$    | 000/0        | 010/0        |
| $C': 010$    | 110/0        | 111/0        |
| $D': 011$    | 011/0        | 011/0        |
| $E': 100$    | 100/0        | 100/1        |
| $F': 101$    | 101/1        | 101/1        |

(b)

# Majority FSM Circuit

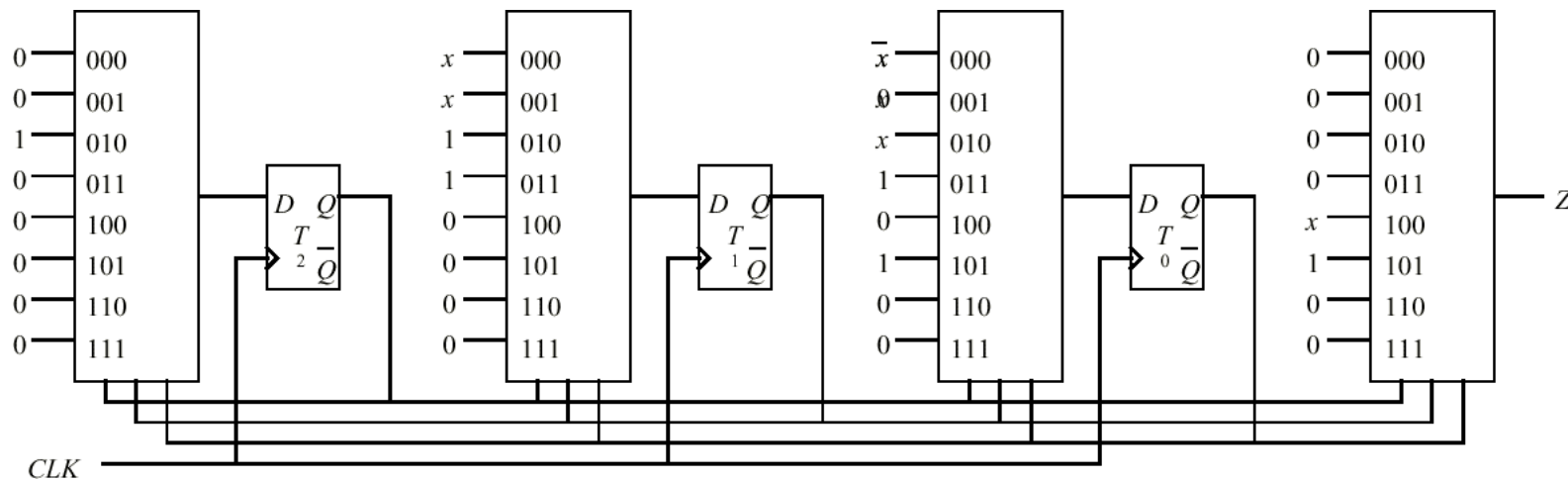

# Review of Objectives

- Declared the 2 conditions necessary for states in an FSM to be EQUIVALENT
- Used a state reduction to lower the number of required FSM states which slightly altered the FSM design flow
- Wrote D, RS, T and JK FF excitation tables
- Employed FF excitation tables to allow the application of any kind of FF in a given FSM design