

MOS: Metal Oxide Semiconductor

Transistors are built on a **Silicon** (semiconductor) substrate.


Pure silicon has no free carriers and conducts poorly.


Dopants are added to increase conductivity: extra electrons (**n-type**) or extra holes (**p-type**)

MOS structure created by superimposing several layers of conducting, insulating and transistor-forming materials.

Metal gate has been replaced by polysilicon or poly in modern technologies.

There are two types of MOS transistors:


nMOS  : Negatively doped silicon, rich in electrons.

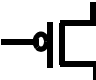pMOS  : Positively doped silicon, rich in holes.

CMOS: Both type of transistors are used to construct any gate.


nMOS and pMOS

 Four terminal devices: Source, Gate, Drain, body (substrate, bulk).




CMOS Inverter Cross-Section

Cadence Layer's for AMI 0.6mm technology

 

CMOS Cadence Layout

 Cadence Layout for the inverter on previous slide




MOS Transistor Switches

We can treat MOS transistors as simple on-off switches with a source (S), gate (G) (controls the state of the switch) and drain (D).


1 represents high voltage, V_{DD} (5V, 3.3V, 1.8V, 1.2V, $\leq 1.0V$ today,

0 represent low voltage - GND or V_{SS} . (0V for digital circuits)


nMOS

 




$g = 0$

 

$g = 1$

 

pMOS

   

Signal Strengths


Signals such as **1** and **0** have strengths, measures ability to sink or source current
 V_{DD} and GND Rails are the strongest 1 and 0



Under the switch abstraction, G has complete control and S and D have no effect.
 In reality, the gate can turn the switch on only if a potential difference of at least V_t exists between the G and S.

We will look at V_t in detail later on in the course.


Thus signal strengths are related to V_t and therefore p and n transistors produce signals with different strengths

 Strong 1: V_{DD} , **Strong 0**: GND, **Weak 1** : $(\sim V_{DD} - V_t)$ and **Weak 0** : $(\sim GND + V_t)$.



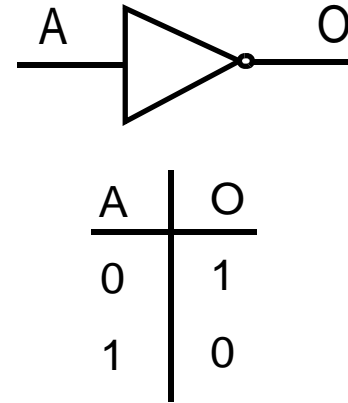
 
CMOS Inverter

 THE CONFIGURATION BELOW FOR A BUFFER IS NOT A GOOD IDEA. WHY?





BAD IDEA

NAND and NOR CMOS Gates

  

| A | B | C |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |








 
 


| A | B | C |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

Pass Transistor


The off-state of a transistor creates a high impedance condition Z at the drain.

         No current flows from source to drain. So transistors can be used as switches.



However, as we previously discussed this will produce degraded outputs, if only one transistor is used as a switch.

Transmission Gates

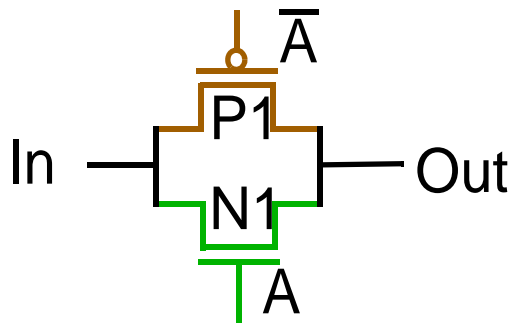


One pMOS and one nMOS in parallel.


Note that neither transistor is connected to V_{DD} or GND.

A and \bar{A} control the transmission of a signal on *In* to *Out*.

 
Transmission gates act as tristate buffers.



$g = 0, gb = 1$

 


$g = 1, gb = 0$

 





Input

Output

$g = 1, gb = 0$

 


$g = 1, gb = 0$

    


Transmission Gate Application: Select Mux

Transmission Gate

 

2-to-1 MUX

 

Truth Table for 2-to-1 MUX





| Select | Out |
|--------|-----|
| 0 | B |
| 1 | A |

$$\text{Out} = A.S + B.\bar{S}$$

How many transistors are required to implement this using CMOS gates?

D Latch





Positive
level-sensitive
latch

    

*If \overline{CLK} is unavailable one extra inverter
needed to generate it using CLK*

D Flip-Flop

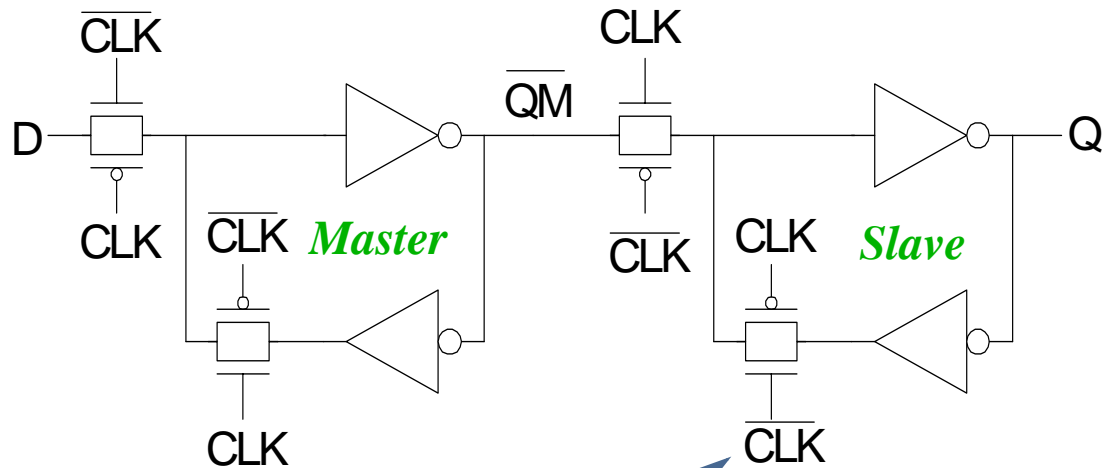   
Positive
edge-triggered
flip-flop
a.k.a
master-slave
flip-flop




If \overline{CLK} is unavailable one extra inverter needed to generate it using CLK

D Flip-Flop Operation


\overline{QM} follows D, Q is latched

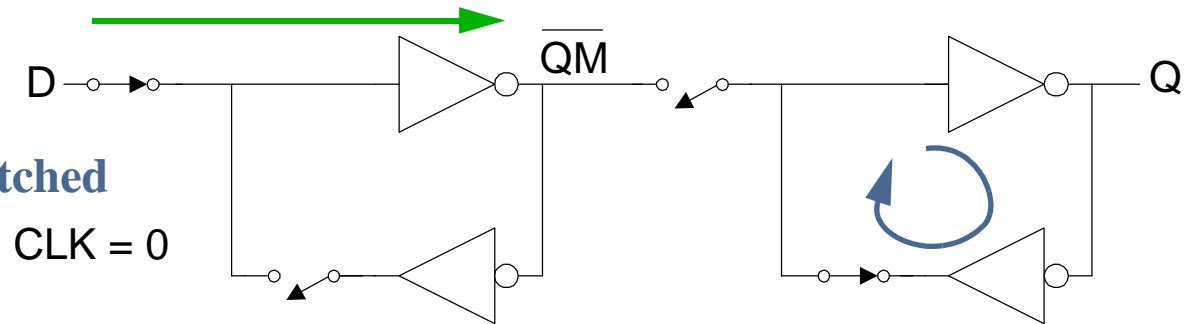

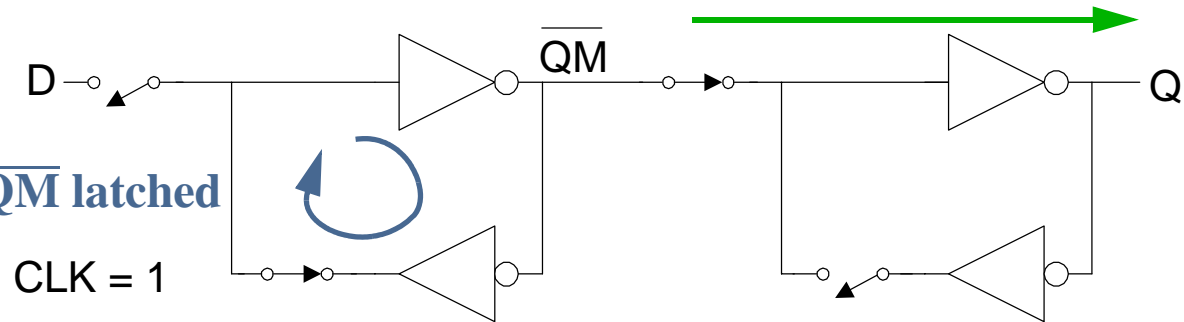
\overline{QM} transferred to Q, \overline{QM} latched




Positive edge-triggered flip-flop

 

More CMOS Gates

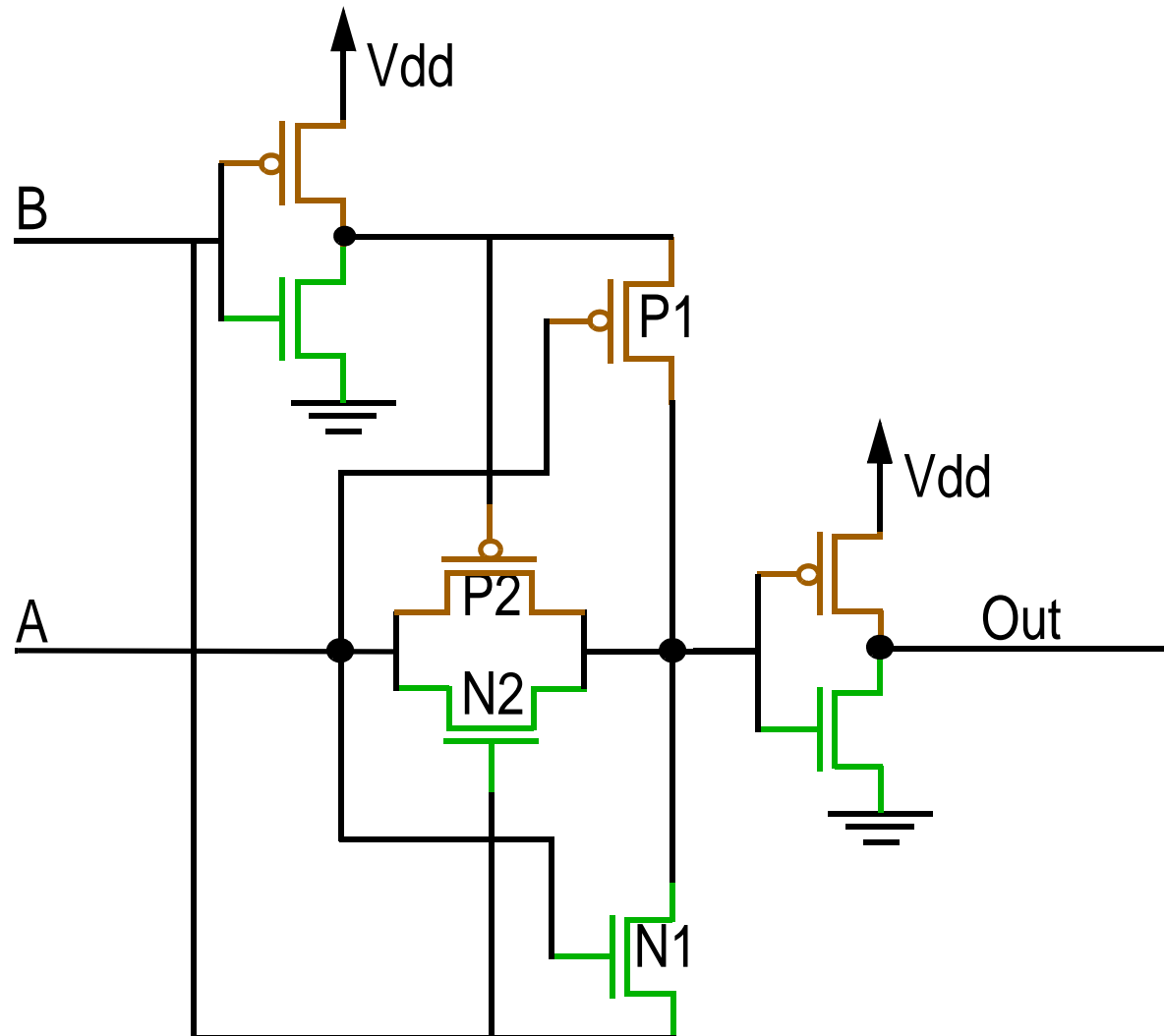

 And More CMOS Gates

And More CMOS Gates

