



Digital Design: An Embedded Systems Approach Using Verilog

Chapter 4 Sequential Basics



Portions of this work are from the book, *Digital Design: An Embedded Systems Approach Using Verilog*, by Peter J. Ashenden, published by Morgan Kaufmann Publishers, Copyright 2007 Elsevier Inc. All rights reserved.

Sequential Basics

- Sequential circuits
 - Outputs depend on current inputs and previous inputs
 - Store *state*: an abstraction of the history of inputs
- Usually governed by a periodic clock signal

D-Flipflops

 
 
- 1-bit storage element
 - We will treat it as a basic component



- Other kinds of flipflops
 - SR (set/reset), JK, T (toggle)

Registers

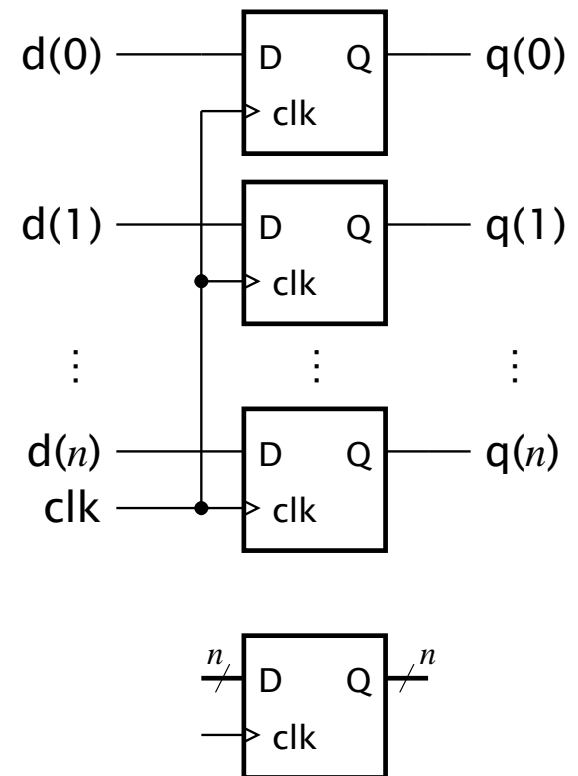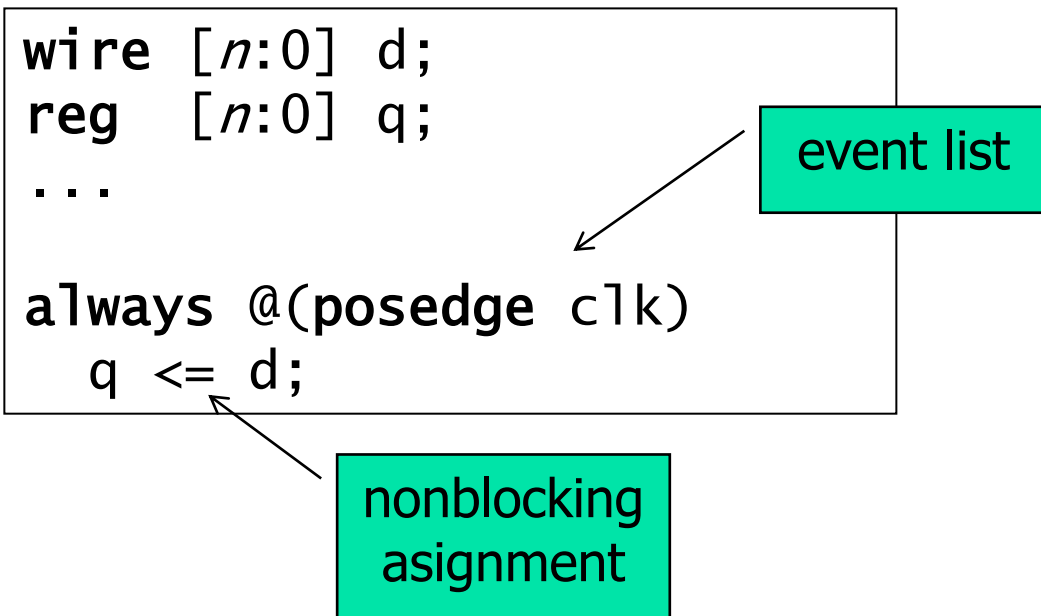- Store a multi-bit encoded value
 - One D-flipflop per bit
 - Stores a new value on each clock cycle




Pipelines Using Registers

Total delay = $\text{Delay}_1 + \text{Delay}_2 + \text{Delay}_3$

Clock period = $\text{Delay}_1 + \text{Delay}_2 + \text{Delay}_3$

Interval between outputs $>$ Total delay

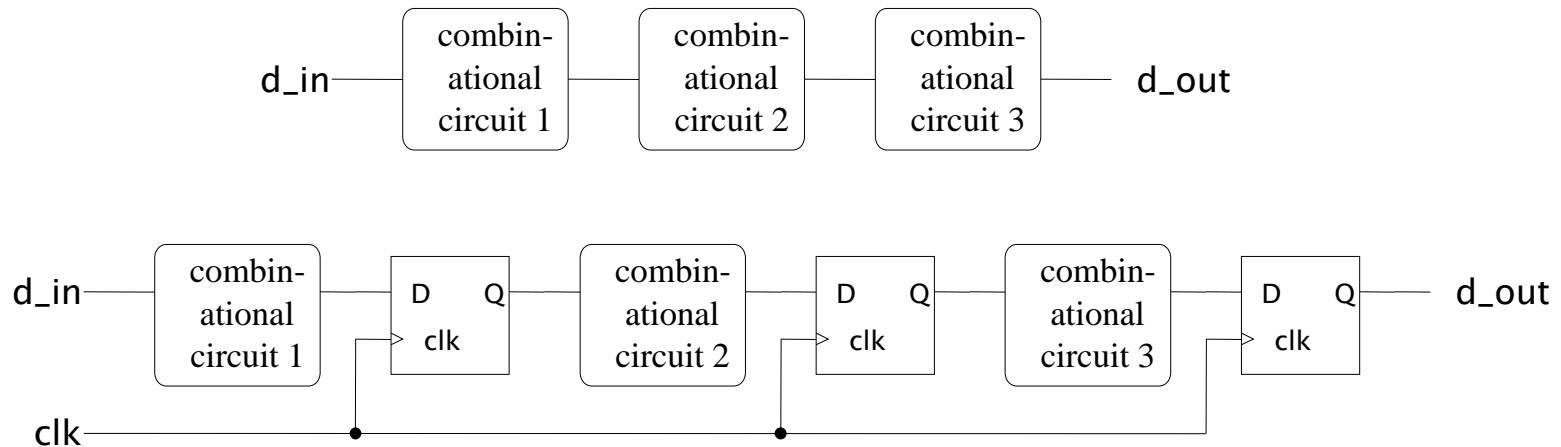

Clock period = $\max(\text{Delay}_1, \text{Delay}_2, \text{Delay}_3)$

Total delay = $3 \times \text{clock period}$

Interval between outputs = 1 clock period

Example: Average Calculator

- Design a module that calculates the average of 3 inputs using 2-input Adder and one divider.
- First design the module in combinational style, assuming you receive one set of inputs.
- Next Pipeline the design to receive stream of inputs.

Example Combinational Module for Average

```
module average(output signed [0:13] avg,  
              input signed [0:13] a,b,c);
```

```
  wire signed [14:0] a_plus_b;
```


```
  wire signed [15:0] sum;
```

```
  assign a_plus_b=a+b;
```

```
  assign sum = a_plus_b + c;
```

```
  assign avg = sum / 3;
```

```
endmodule
```

 

Testbench and results

```
module average_tb();
reg signed [13:0] a,b,c;
wire signed [13:0] avg;
```

```
average uut(.a(a),
            .b(b),
            .c(c),
            .avg(avg));
```

```
initial begin
```

```
a=2;
```

```
b=3;
```

```
c=4;
```

```
end
```


```
endmodule
```

Name	Value	
> a[13:0]	0002	0002
> b[13:0]	0003	0003
> c[13:0]	0004	0004
> avg[13:0]	0003	0003
> a_plus_b[14:0]	0005	0005
> sum[15:0]	0009	0009

Pipeline Example of Average Module

- Compute the average of corresponding numbers in three input streams
 - New values arrive on each clock edge

Block diagram of the Pipeline Example

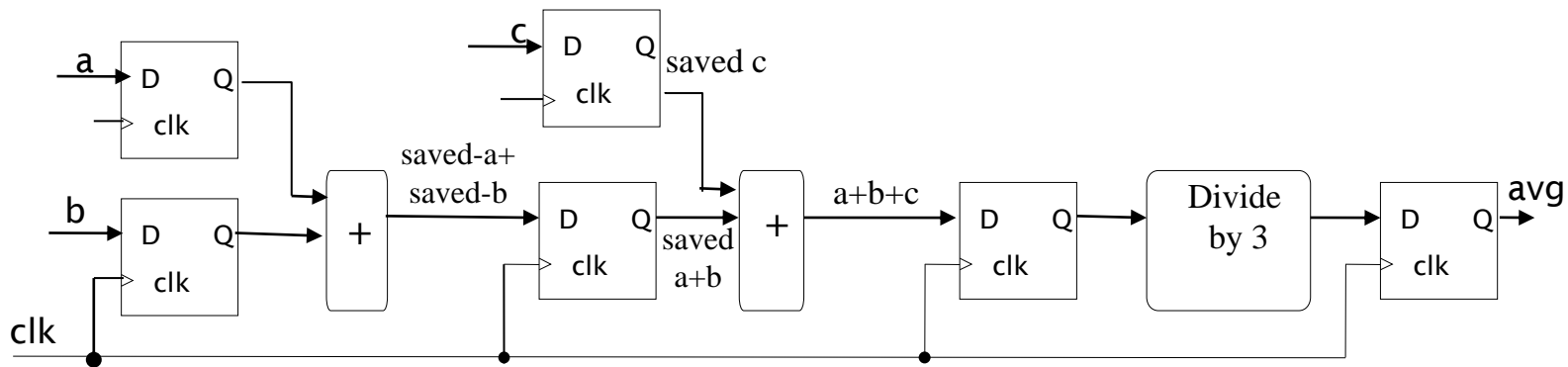

Verilog of the Pipeline Example

```
module pipeline(output reg signed
[0:13] avg,
                input signed [0:13] a,b,c,
                input clk);

reg signed [0:13] saved_a,saved_b;
wire signed [0:14] a_plus_b;
wire signed [0:15] sum;
wire signed [0:22] sum_div_3;
reg signed [0:14] saved_a_plus_b;
reg signed [0:13] saved_c;
reg [0:15] saved_sum;
```

```
always @(posedge clk)begin
    saved_a <= a;
    saved_b <= b;
end
assign a_plus_b = saved_a + saved_b;


always @(posedge clk)begin
    saved_a_plus_b <= a_plus_b;
    saved_c <= c;
end
assign sum = saved_a_plus_b + saved_c;
always @(posedge clk)begin
    saved_sum <= sum;
end
assign sum_div_3 = saved_sum /3;
always @(posedge clk)
    avg <= sum_div_3;
endmodule
```

Testbench for one input set

```
module pipeline_tb();
  reg clk;
  reg signed [13:0] a,b,c;
  wire signed [13:0] avg;
  pipeline uut(.clk(clk),
              .a(a),
              .b(b),
              .c(c),
              .avg(avg));

  always #5 clk = ~clk;
  initial begin
    clk = 0;
    a=2;
    b=3;
    c=4;
  end
endmodule
```

Simulation Results

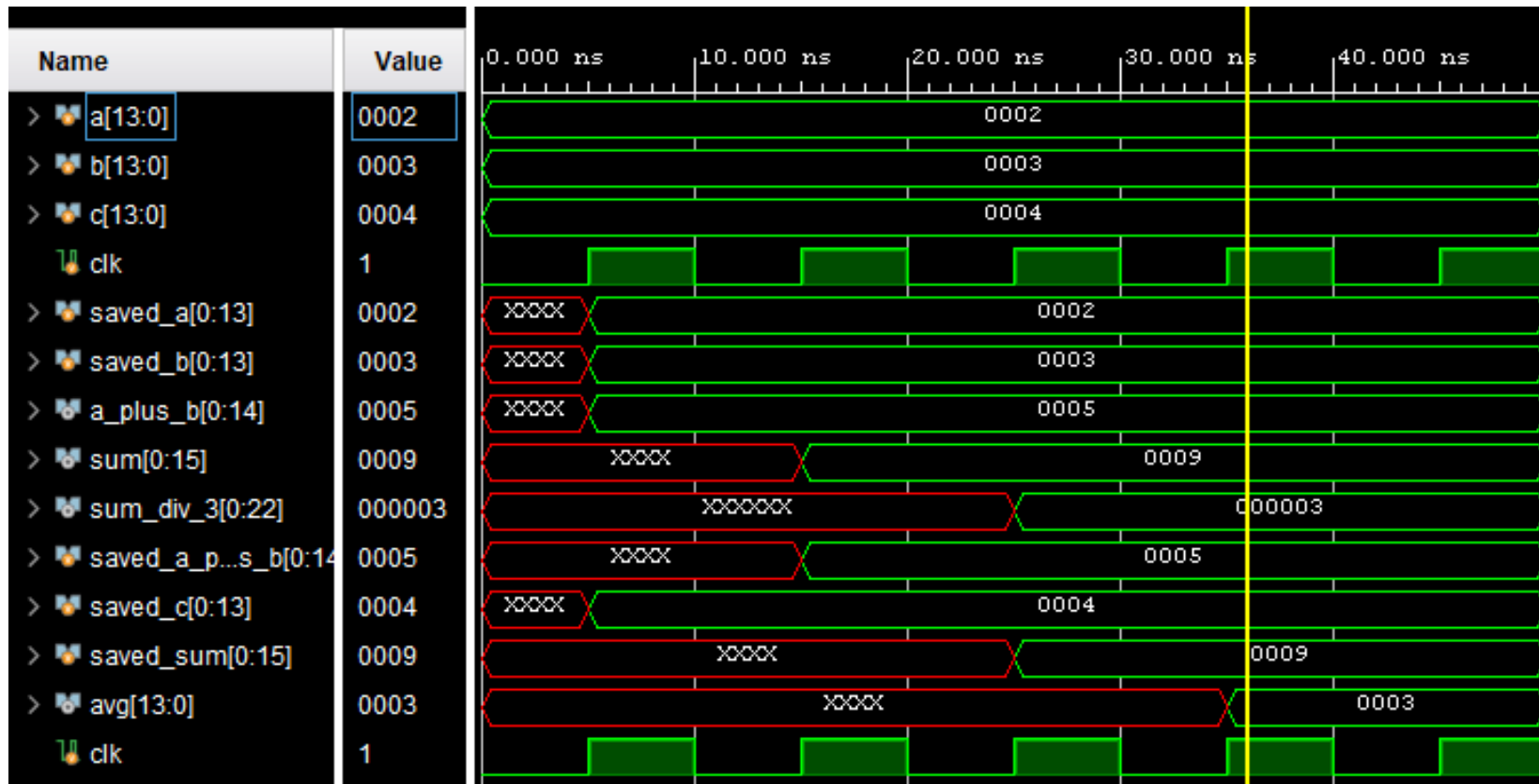

Testbench for streams of input sets

```
module pipeline_tb();  
  reg clk;  
  reg signed [13:0] a,b,c;  
  wire signed [13:0] avg;  
  pipeline uut(.clk(clk),  
              .a(a),  
              .b(b),  
              .c(c),  
              .avg(avg));
```

```
  always #5 clk = ~clk;  
  initial begin  
    clk = 0;  
    a=2;  
    b=3;  
    c=4;
```


```
  #10  
    a=10;  
    b=5;  
    c=3;
```

```
  #10  
    a=10;  
    b=5;  
    c=6;  
  end  
endmodule
```


Expected Results

	cycle 1	cycle 2	cycle 3
a:	2	10	10
b:	3	5	5
c:	4	3	6
sum :	9	18	21
Avg ($\frac{\text{sum}}{3}$):	3	6	7

clk

 

Testbench Results with existing code

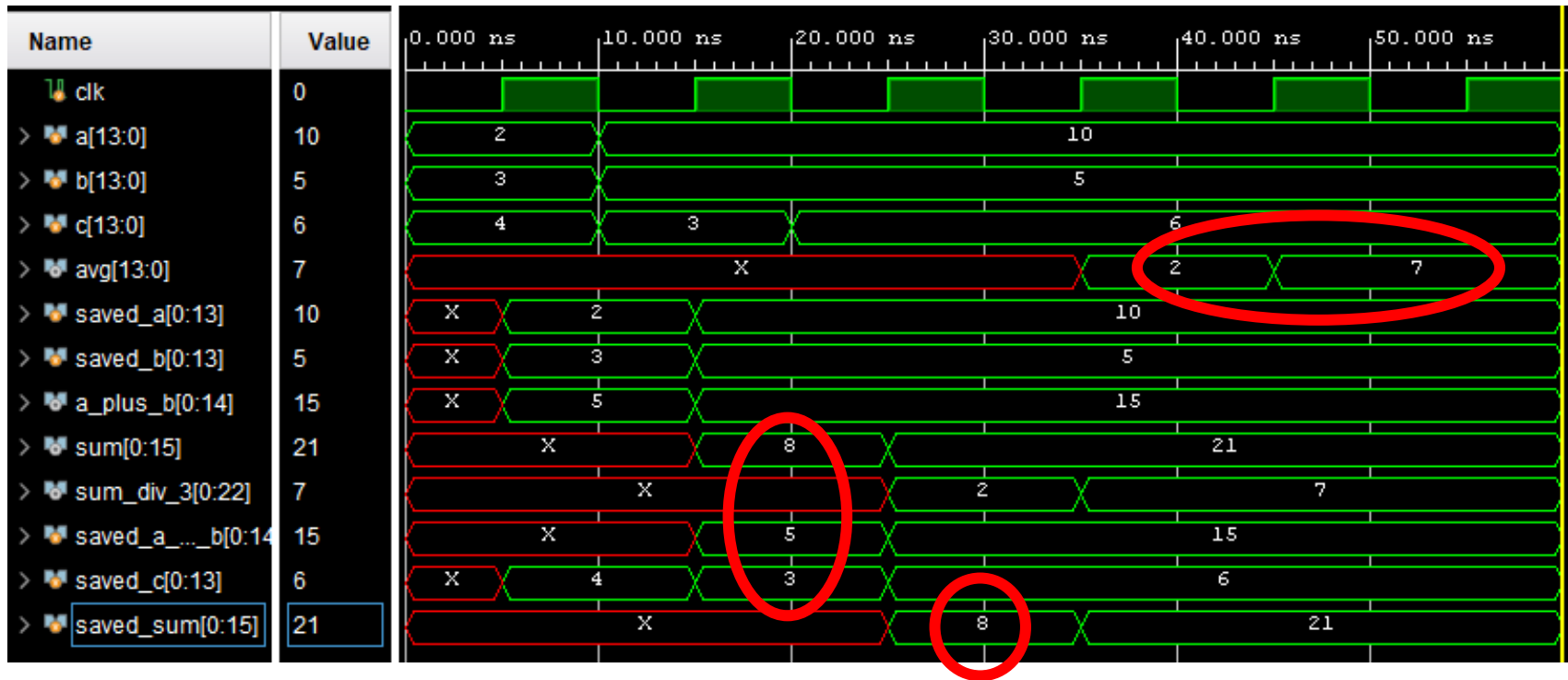

Wrong results! How to solve it?

Solution: Delay C one more cycle

```
module pipeline(output reg signed [0:13] avg,
               input signed [0:13] a,b,c,
               input clk);

reg signed [0:13] saved_a,saved_b;
wire signed [0:14] a_plus_b;
wire signed [0:15] sum;
wire signed [0:22] sum_div_3;
reg signed [0:14] saved_a_plus_b;
reg signed [0:13] saved_c, saved_saved_c;
reg [0:15] saved_sum;

always @(posedge clk)begin
    saved_a <= a;
    saved_b <= b;
end

assign a_plus_b = saved_a + saved_b;

always @(posedge clk)begin
    saved_a_plus_b <= a_plus_b;
    saved_c <= c;
    saved_saved_c <= saved_c;
end

assign sum = saved_a_plus_b + saved_saved_c;

always @(posedge clk)begin
    saved_sum <= sum;
end

assign sum_div_3 = saved_sum /3;

always @(posedge clk)
    avg <= sum_div_3;

endmodule
```

Testbench Results with corrected code

